

21BDS0340

Abhinav Dinesh Srivatsa

Digital Systems Design Lab

Task 4

S. No.	Components	Page No.	Student Check Mark	RA Check Mark
1	Aim	3	✓	
2	Components and Tools Required	3	✓	
3	Procedure	3	✓	
4	Pin Diagram	3	✓	
5	Function Table of 1-bit ALU	3	✓	
6	One Bit ALU Theory	3	✓	
7	Data Path Elements Theory	4	✓	
8	Block diagram /Circuit diagram for implementing 1-bit ALU	4	✓	
9	Block diagram and Circuit diagram for implementing 4-bit ALU	5	✓	
10	Block diagram and Circuit diagram for implementing 8-bit ALU	5	✓	
11	4-bit ALU Theory	5	✓	
12	Verilog code for 1-bit ALU	5	✓	
13	Verilog code for 4-bit ALU	6	✓	
14	Verilog code of 8-bit ALU	7	✓	
15	Test bench	8	✓	
16	Implementation steps for ALU Design	9	✓	
17	Verilog code Output in online circuit simulator/Modelsim tool for 1-bit ALU	9	✓	
18	Verilog code Output in online circuit simulator/Modelsim tool for 4-bit ALU	9	✓	

19	Multisim live / Circuitverse.org Simulation link for 1-bit ALU	9	✓	
20	Multisim live / Circuitverse.org Simulation link for 4-bit ALU	9	✓	
21	IC inter-connection diagram for 1-bit ALU HW connection in breadboard	9	✓	
22	Verilog code: 16-bit ALU	9	✓	
23	Verilog code: 32-bit ALU	10	✓	
24	Result	11	✓	
25	Inference	11	✓	

Aim

1. Design ALU (1, 4, 8 bit) for 8 functions of your choice with a neat circuit diagram. Write Verilog code for (1, 4, 8 bit) ALU. 2.
2. Design the various data path elements of the Arithmetic Logic unit (4 or 8 or 16 bit). Write the suitable Verilog code to implement in Modelsim.

Components Required

- a. AND, OR, NOT, NAND and NOR gates
- b. 5V voltage source
- c. Led indicator

Tools Required

- a. Multisim simulator

Procedure

1. Design 1-bit ALU and implement in Verilog
2. Do the same for higher bit ALUs

Function Table of 1-bit ALU

S_0	S_1	S_2	S_3	F	Operation
0	0	0	0	$F = A + B$	Addition
0	0	0	1	$F = A - B$	Subtraction
0	0	1	0	$F = A \times B$	Multiplication
0	0	1	1	$F = A / B$	Division
0	1	0	0	$F = A + 1$	Increment A
0	1	0	1	$F = A - 1$	Decrement A
0	1	1	0	$F = A \& B$	Logical AND
0	1	1	1	$F = A B$	Logical OR
1	0	0	0	$F = \sim A$	Logical NOT
1	0	0	1	$F = \sim(A \& B)$	Logical NAND
1	0	1	0	$F = \sim(A B)$	Logical NOR
1	0	1	1	$F = A \wedge B$	Logical XOR
1	1	0	0	$F = \sim(A \wedge B)$	Logical XNOR
1	1	0	1	$F = (A > B) ? 1 : 0$	Greater Comparison
1	1	1	0	$F = (A < B) ? 1 : 0$	Lesser Comparison
1	1	1	1	$F = (A == B) ? 1 : 0$	Equal Comparison

One Bit ALU Theory

In computing, an arithmetic logic unit (ALU) is a combinational digital circuit that performs arithmetic and bitwise operations on integer binary numbers. This contrasts with a floating-point unit (FPU), which operates on floating point numbers. It is a fundamental building block of many types of computing circuits, including the central processing unit (CPU) of computers, FPUs, and graphics processing units (GPUs).


The inputs to an ALU are the data to be operated on, called operands, and a code indicating the operation to be performed; the ALU's output is the result of the performed operation. In many designs, the ALU also has status inputs or outputs, or both, which convey information about a previous operation or the current operation, respectively, between the ALU and external status registers.

Data Path Elements Theory

A data path is a collection of functional units such as arithmetic logic units or multipliers that perform data processing operations, registers, and buses. Along with the control unit it composes the central processing unit (CPU). A larger data path can be made by joining more than one data paths using multiplexers.

A data path is the ALU, the set of registers, and the CPU's internal bus(es) that allow data to flow between them.

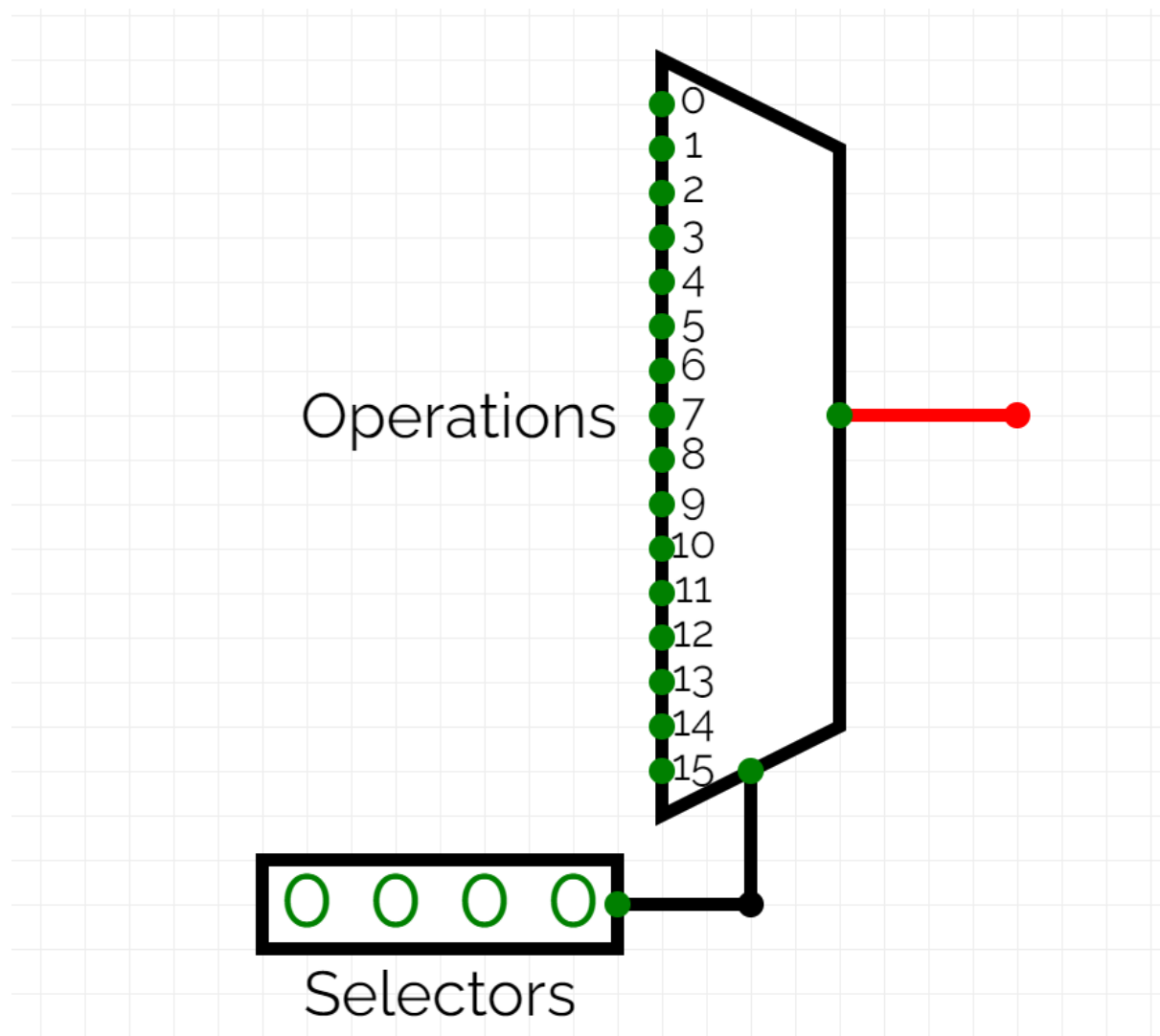Block diagram/Circuit diagram for implementing 1-bit ALU



Block diagram and Circuit diagram for implementing 4-bit and 8-bit ALU

Same as the above diagram just that the bit width for A and B will be 4 and 8 respectively for 4- and 8-bit ALUs

4-bit ALU Theory

Theory is the same as a 1-bit ALU, only difference is that the bit width of the output and the inputs are changed to 4 bits instead of 1 bit.

Verilog code for 1-bit ALU

```
module alu(a, b, sel, carry, out);
  input a, b;
  input [0:3]sel;
  output carry;
  output out;
  reg [0:1]res;

  assign out = res[1];
  assign carry = res[0];
  always @(*)
    begin
      case(sel)
        4'b0000: //addition
          res = a + b;
        4'b0001: //subtraction
          res = a - b;
        4'b0010: //multiplication
          res = a * b;
        4'b0011: //division
          res = a / b;
        4'b0100: //increment
          res = a + 4'b0001;
        4'b0101: //decrement
          res = a - 4'b0001;
        4'b0110: //logical AND
          res = a & b;
        4'b0111: //logical OR
          res = a | b;
        4'b1000: //logical NOT
          res = ~a;
        4'b1001: //logical NAND
          res = ~(a & b);
        4'b1010: //logical NOR
          res = ~(a | b);
        4'b1011: //logical XOR
          res = a ^ b;
      endcase
    end
endmodule
```

```

    4'b1100: //logical XNOR
        res = ~(a ^ b);
    4'b1101: //greater comparision
        res = (a > b) ? 8'd1 : 8'd0;
    4'b1110: //lesser comparision
        res = (a < b) ? 8'd1 : 8'd0;
    4'b1111: //equal comparision
        res = (a == b) ? 8'd1 : 8'd0;
endcase
end
endmodule

```

Verilog code for 4-bit ALU

```

module alu(a, b, sel, carry, out);
    input [0:3]a, b;
    input [0:3]sel;
    output carry;
    output [0:3]out;
    reg [0:4]res;

    assign out = res[1:4];
    assign carry = res[0];
    always @(*)
        begin
            case(sel)
                4'b0000: //addition
                    res = a + b;
                4'b0001: //subtraction
                    res = a - b;
                4'b0010: //multiplication
                    res = a * b;
                4'b0011: //division
                    res = a / b;
                4'b0100: //increment
                    res = a + 4'b0001;
                4'b0101: //decrement
                    res = a - 4'b0001;
                4'b0110: //logical AND
                    res = a & b;
                4'b0111: //logical OR
                    res = a | b;
                4'b1000: //logical NOT
                    res = ~a;
                4'b1001: //logical NAND
                    res = ~(a & b);
                4'b1010: //logical NOR
                    res = ~(a | b);
                4'b1011: //logical XOR

```

```

        res = a ^ b;
4'b1100: //logical XNOR
        res = ~(a ^ b);
4'b1101: //greater comparision
        res = (a > b) ? 8'd1 : 8'd0;
4'b1110: //lesser comparision
        res = (a < b) ? 8'd1 : 8'd0;
4'b1111: //equal comparision
        res = (a == b) ? 8'd1 : 8'd0;
    endcase
end
endmodule

```

Verilog code for 8-bit ALU

```

module alu(a, b, sel, carry, out);
    input [0:7]a, b;
    input [0:3]sel;
    output carry;
    output [0:7]out;
    reg [0:8]res;

    assign out = res[1:8];
    assign carry = res[0];
    always @(*)
    begin
        case(sel)
            4'b0000: //addition
                res = a + b;
            4'b0001: //subtraction
                res = a - b;
            4'b0010: //multiplication
                res = a * b;
            4'b0011: //division
                res = a / b;
            4'b0100: //increment
                res = a + 4'b0001;
            4'b0101: //decrement
                res = a - 4'b0001;
            4'b0110: //logical AND
                res = a & b;
            4'b0111: //logical OR
                res = a | b;
            4'b1000: //logical NOT
                res = ~a;
            4'b1001: //logical NAND
                res = ~(a & b);
            4'b1010: //logical NOR
                res = ~(a | b);

```

```

    4'b1011: //logical XOR
        res = a ^ b;
    4'b1100: //logical XNOR
        res = ~(a ^ b);
    4'b1101: //greater comparision
        res = (a > b) ? 8'd1 : 8'd0;
    4'b1110: //lesser comparision
        res = (a < b) ? 8'd1 : 8'd0;
    4'b1111: //equal comparision
        res = (a == b) ? 8'd1 : 8'd0;
endcase
end
endmodule

```

Test bench

```

module test;
    reg a, b;
    reg [0:3]sel;
    wire carry;
    wire out;


    alu a1(a, b, sel, carry, out);
    initial begin
        a = 1'b1;
        b = 1'b0;
        sel = 4'h0; #100
        sel = 4'h1; #100
        sel = 4'h2; #100
        sel = 4'h3; #100
        sel = 4'h4; #100
        sel = 4'h5; #100
        sel = 4'h6; #100
        sel = 4'h7; #100
        sel = 4'h8; #100
        sel = 4'h9; #100
        sel = 4'hA; #100
        sel = 4'hB; #100
        sel = 4'hC; #100
        sel = 4'hD; #100
        sel = 4'hE; #100
        sel = 4'hF;
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
    end
end

```



endmodule

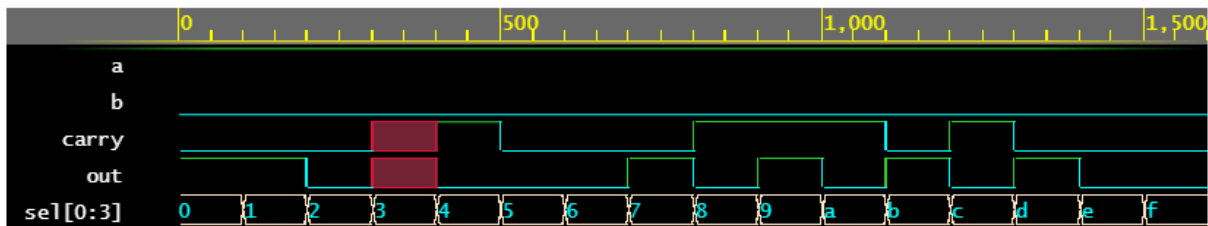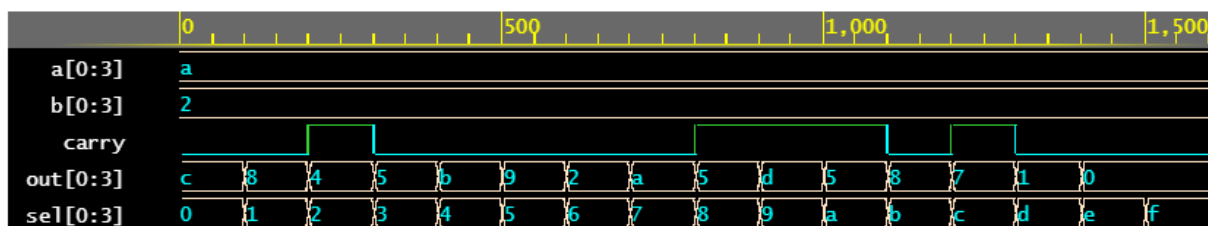Verilog code Output in online circuit simulator/Modelsim tool for 1-bit ALU



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Verilog code Output in online circuit simulator/Modelsim tool for 4-bit ALU



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Multisim live / Circuitverse.org Simulation link for 1-bit ALU

<https://www.edaplayground.com/x/rgPw>

Multisim live / Circuitverse.org Simulation link for 4-bit ALU

<https://www.edaplayground.com/x/As73>

Verilog code: 16-bit ALU

```
module alu(a, b, sel, carry, out);
  input [0:15]a, b;
  input [0:3]sel;
  output carry;
  output [0:15]out;
  reg [0:16]res;

  assign out = res[1:16];
  assign carry = res[0];
  always @(*)
  begin
    case(sel)
      4'b0000: //addition
        res = a + b;
      4'b0001: //subtraction
        res = a - b;
```

```

    4'b0010: //multiplication
        res = a * b;
    4'b0011: //division
        res = a / b;
    4'b0100: //increment
        res = a + 4'b0001;
    4'b0101: //decrement
        res = a - 4'b0001;
    4'b0110: //logical AND
        res = a & b;
    4'b0111: //logical OR
        res = a | b;
    4'b1000: //logical NOT
        res = ~a;
    4'b1001: //logical NAND
        res = ~(a & b);
    4'b1010: //logical NOR
        res = ~(a | b);
    4'b1011: //logical XOR
        res = a ^ b;
    4'b1100: //logical XNOR
        res = ~(a ^ b);
    4'b1101: //greater comparision
        res = (a > b) ? 8'd1 : 8'd0;
    4'b1110: //lesser comparision
        res = (a < b) ? 8'd1 : 8'd0;
    4'b1111: //equal comparision
        res = (a == b) ? 8'd1 : 8'd0;
endcase
end
endmodule

```

Verilog code: 32-bit ALU

```

module alu(a, b, sel, carry, out);
    input [0:31]a, b;
    input [0:3]sel;
    output carry;
    output [0:31]out;
    reg [0:32]res;

    assign out = res[1:32];
    assign carry = res[0];
    always @(*)
        begin
            case(sel)
                4'b0000: //addition
                    res = a + b;

```

```

4'b0001: //subtraction
    res = a - b;
4'b0010: //multiplication
    res = a * b;
4'b0011: //division
    res = a / b;
4'b0100: //increment
    res = a + 4'b0001;
4'b0101: //decrement
    res = a - 4'b0001;
4'b0110: //logical AND
    res = a & b;
4'b0111: //logical OR
    res = a | b;
4'b1000: //logical NOT
    res = ~a;
4'b1001: //logical NAND
    res = ~(a & b);
4'b1010: //logical NOR
    res = ~(a | b);
4'b1011: //logical XOR
    res = a ^ b;
4'b1100: //logical XNOR
    res = ~(a ^ b);
4'b1101: //greater comparision
    res = (a > b) ? 8'd1 : 8'd0;
4'b1110: //lesser comparision
    res = (a < b) ? 8'd1 : 8'd0;
4'b1111: //equal comparision
    res = (a == b) ? 8'd1 : 8'd0;
endcase
end
endmodule

```

Result and Inference

The above codes are to implement ALUs with functions of my choice which include addition, subtraction, multiplication, division, increment, decrement, basic gate functions (AND, OR, NOT, NAND, NOR, XOR, XNOR) and comparators (greater than, lesser than, equal to). All these ALUs have been made in 1-bit, 4-bit, 8-bit, 16-bit and 32-bit versions in Verilog.