

21BDS0340

Abhinav Dinesh Srivatsa

Electronics Lab


Task 4

Exercise No.: 1

Date: 16/04/22

RC Phase Shift Oscillator

Circuit Diagram

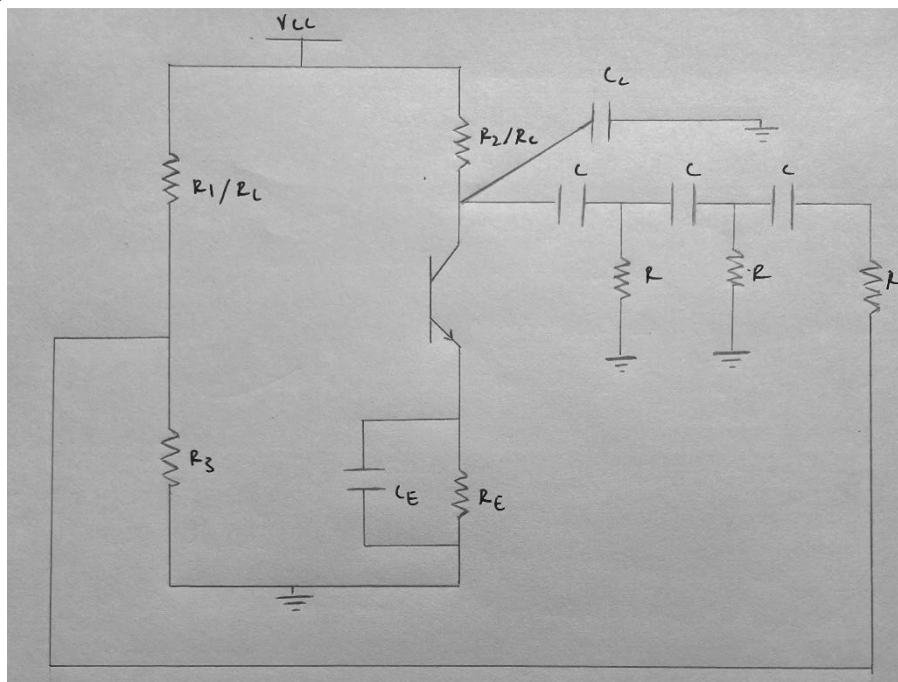

Components Required


Basic – Resistors, Capacitors

Sources – VCC, Ground, AC_Voltage

Transistors – BC547BP


Simulate – Instruments – Oscilloscope

Simulated Circuit Diagram

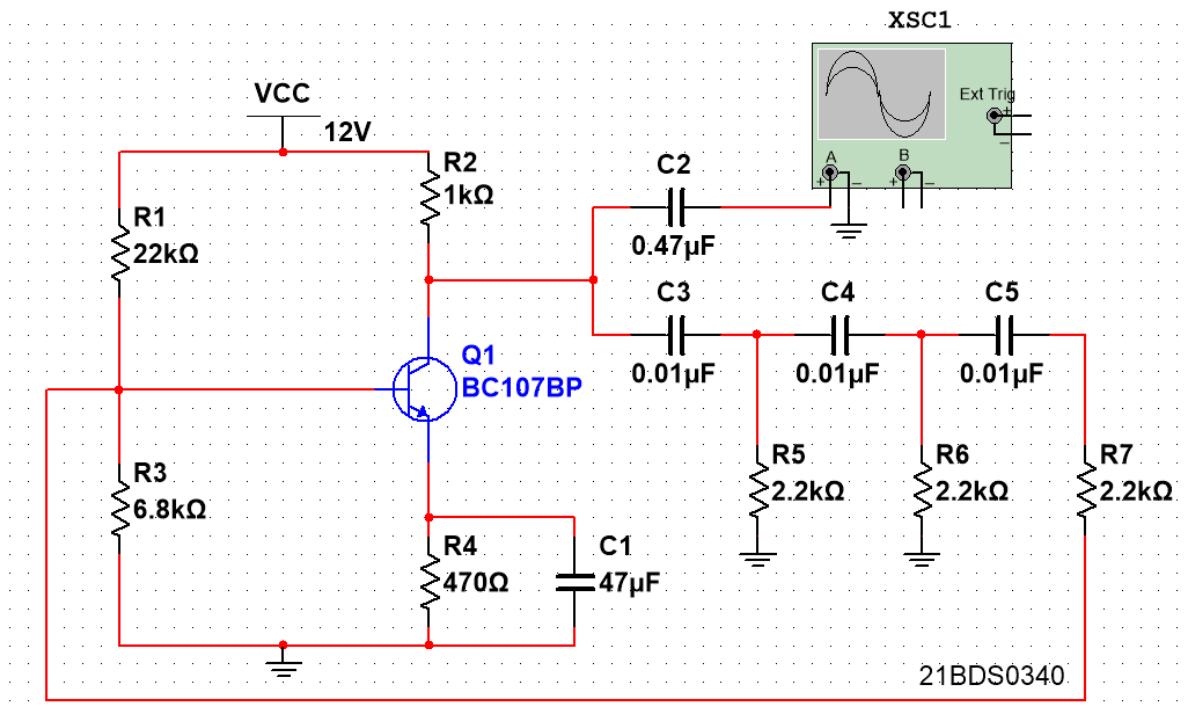

Simulated Output

Oscilloscope-XSC1

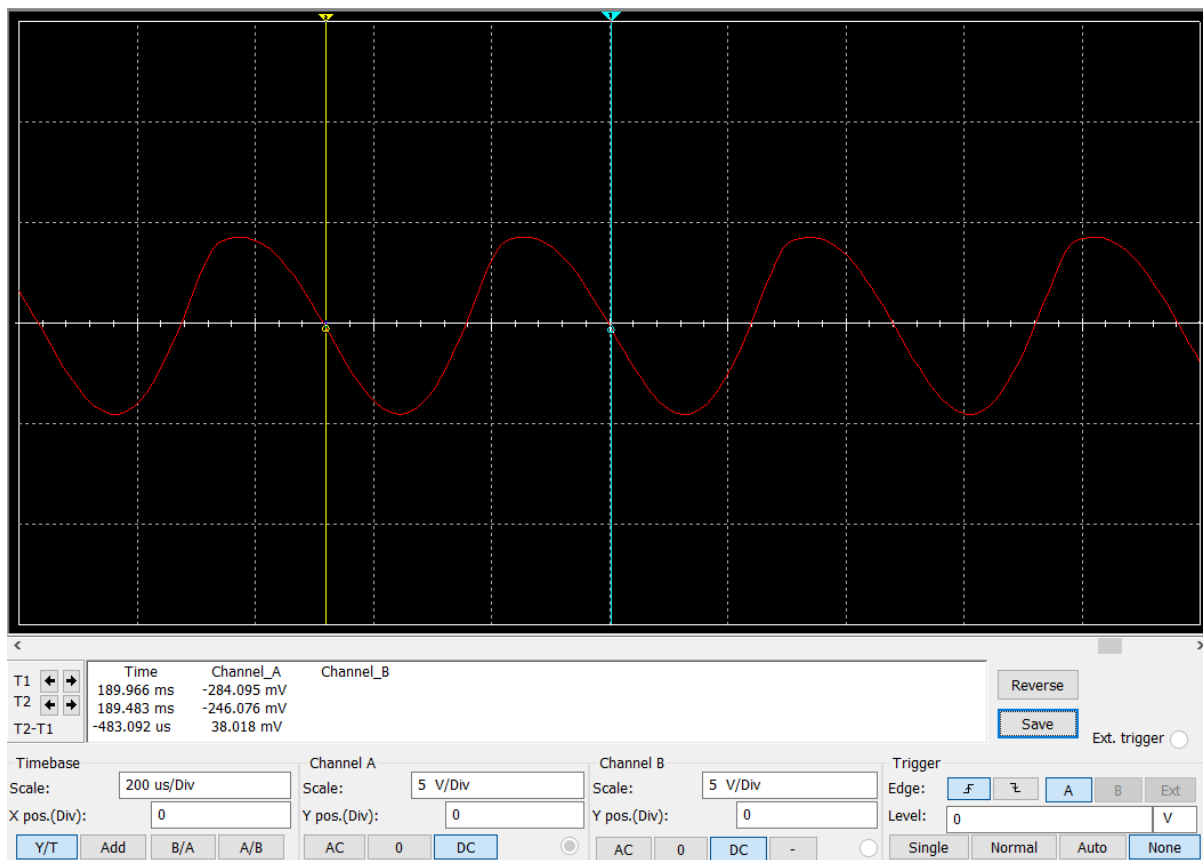

Calculations from Simulated Graph

$$f = \frac{1}{2\pi R C \sqrt{6+4K}}$$

$$R = 2200 \text{ ohms}$$

$$C = 0.015 \mu F$$

$$K = \frac{R_C}{R} = 0.454$$

$$\therefore f = 2000 \text{ Hz}$$

Verification Message



KRISHNA CHAITHANYA MUNTHA 04-05-2022 11:27

21BDS0340-Exp 8 verified

Exercise No.: 2

Date: 19/05/22

Logic Gates

Truth Table

A	B	C	AC	BC	AC + BC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	1	1


Components Required

Basic – Switch – SPDT


Sources – Power Sources – VCC, Ground

TTL – 7408N, 7401N, 7432N


Simulated Circuit Diagram 1

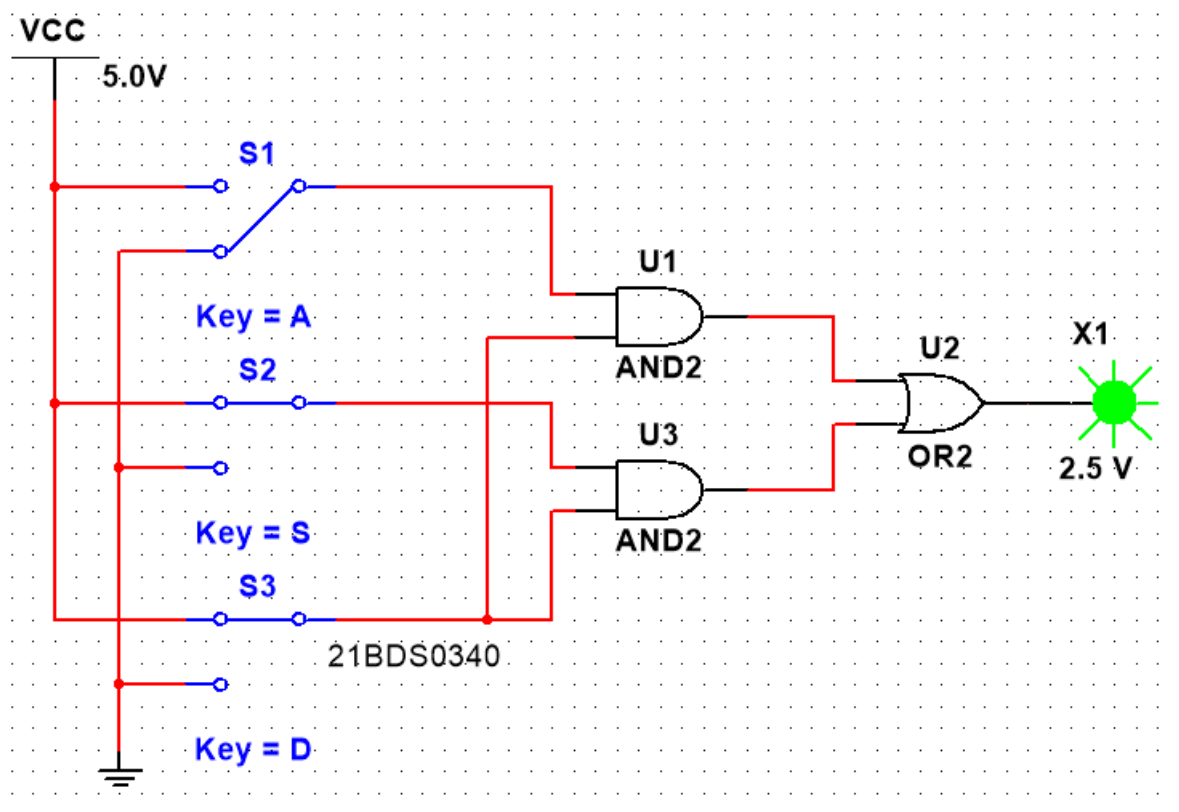


Simulated Circuit Diagram 2

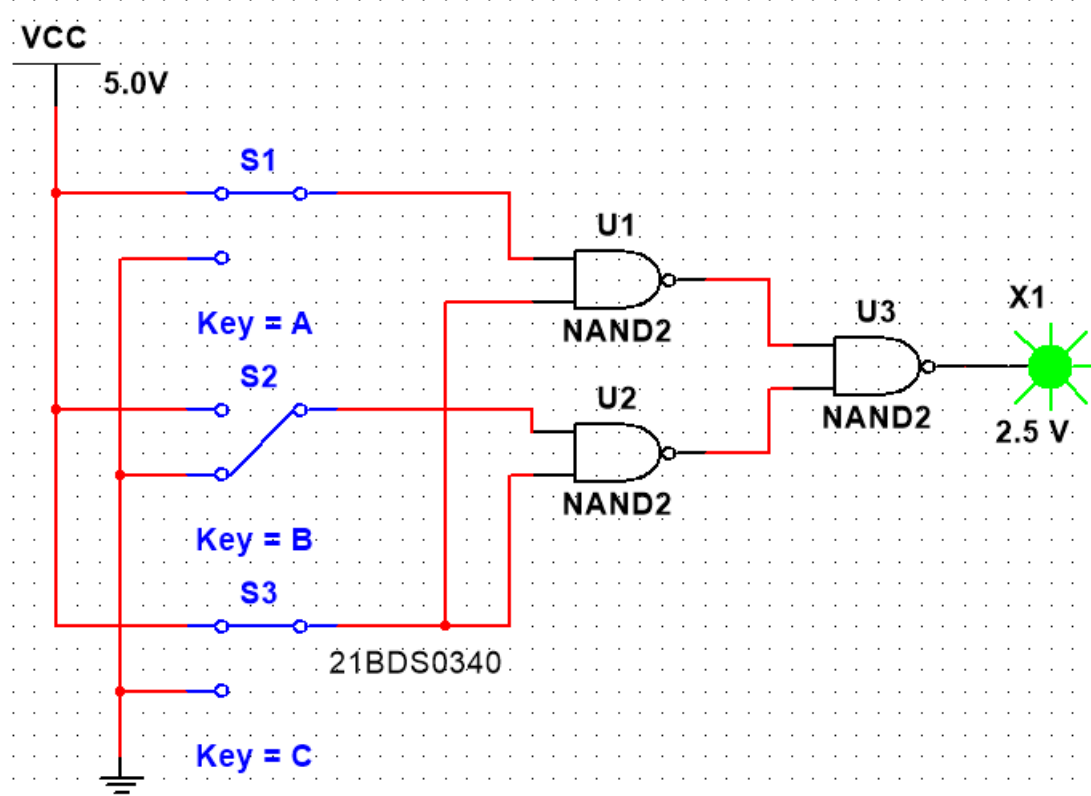

Simulated Circuit Diagram 3

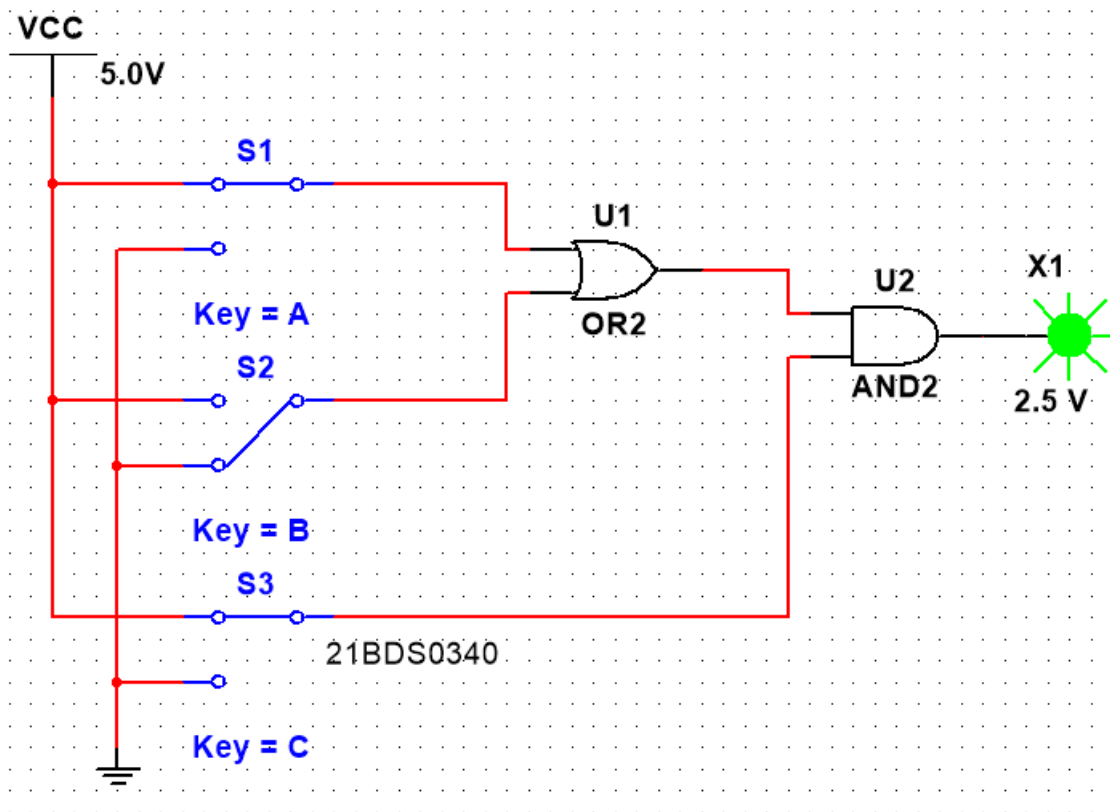

Simulated Circuit Diagram 4

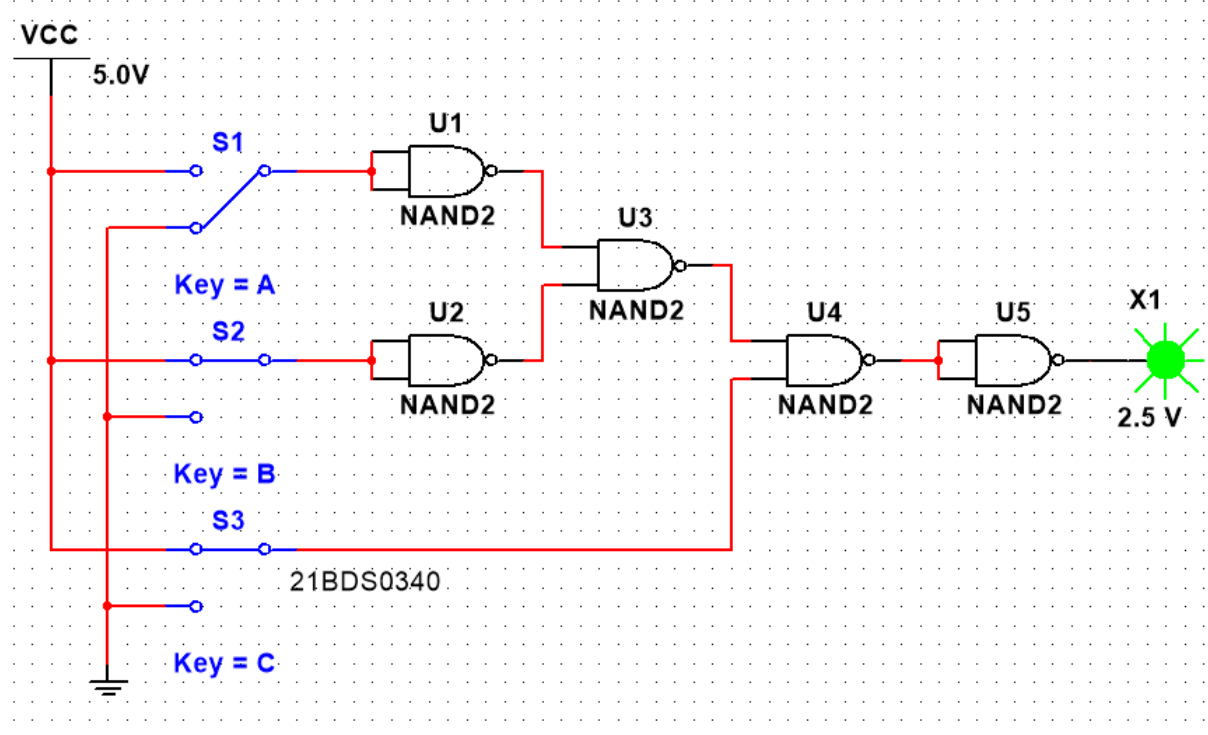

Verification Message

