

21BDS0340

Abhinav Dinesh Srivatsa

Electronics Lab

Task 1

Exercise No.: 1

Date: 24/02/22

Introduction to the Hardware Equipment's, components to be used, Resistor coding , Capacitors , Multimeters, Function Generator and CRO


Part A: Reading Resistor by Colour Coding

No.	Band 1	Band 2	Band 3	Band 4	Nominal Value (ohm)
1	orange	orange	black	gold	$33 \pm 5\%$
2	orange	white	red	gold	$3.9 k \pm 5\%$
3	brown	green	orange	gold	$15 k \pm 5\%$
4	red	violet	orange	gold	$27 k \pm 5\%$
5	orange	white	orange	gold	$39 k \pm 5\%$
6	brown	black	gold	none	$1 \pm 20\%$
7	red	violet	orange	gold	$27 k \pm 5\%$
8	brown	black	red	gold	$1 k \pm 5\%$
9	blue	grey	brown	gold	$680 \pm 5\%$
10	yellow	violet	red	gold	$4.7 k \pm 5\%$
11	red	red	red	gold	$2.2 k \pm 5\%$

Part B: Using Multimeter to Measure Resistance, Voltage and Current

Exercise 1

Circuit Diagram

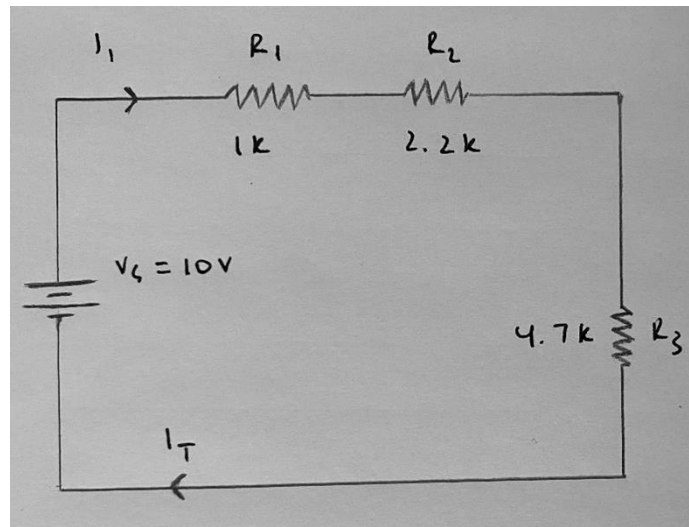

Components Required

Basic – Resistors

Sources – Power Sources – DC_Power, Ground

Manual Workings

$$V = 10V$$

$$R_{eq} = (1 + 2.2 + 4.7) \times 10^3$$

$$= 7900 \text{ ohms}$$

1. $I_1 = I_T$ because the resistors are in series

$$I_1 = I_T = \frac{V}{R_{eq}}$$

$$= \frac{10}{7900}$$

$$= \underline{1.26 \text{ mA}}$$

$$2. V_{R1} = I_1 R_1$$

$$= 1.26 \times 10^{-3} \times 10^3$$

$$= \underline{1.26 \text{ V}}$$


$$3. V_{R2R3} = V_S - V_{R1}$$

$$= 10 - 1.26$$


$$= \underline{8.74 \text{ V}}$$

$$4. R_{eq} = \underline{7900 \text{ ohms}}$$

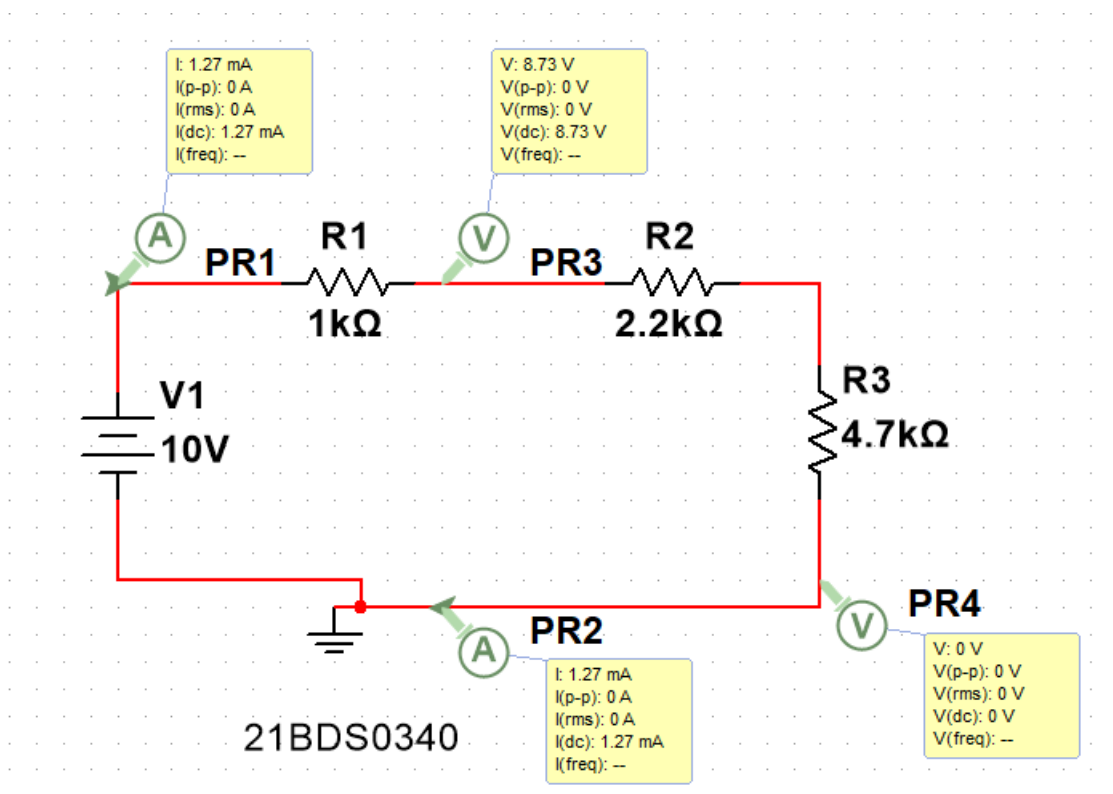Simulated Circuit Diagram for Finding Current and Voltage



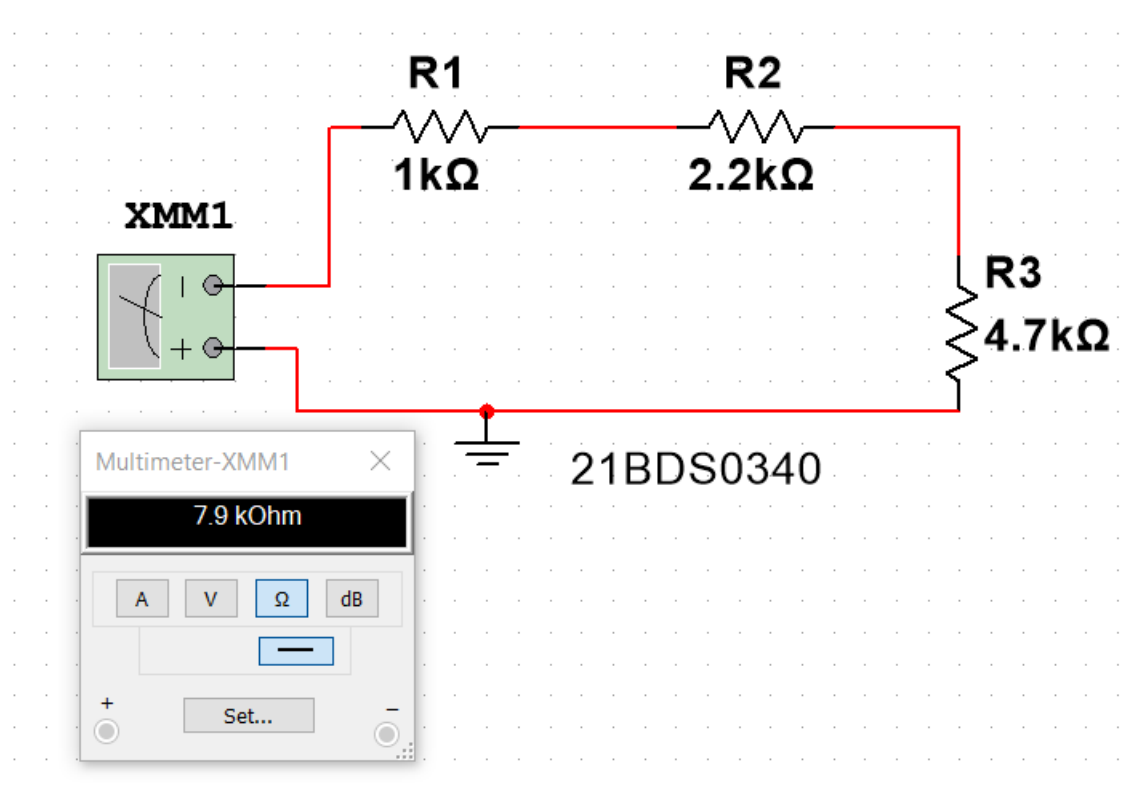Simulated Circuit Diagram for Finding Resistance




Results

NOTATION	MANUAL CALCULATIONS	SIMULATED RESULT
I_1	1.26 mA	1.27 mA
I_T	1.26 mA	1.27 mA
V_{R1}	1.26 V	1.27 V
V_{R2R3}	8.74 V	8.73 V
R_{eq}	7900 ohms	7900 ohms

Exercise 2

Circuit Diagram

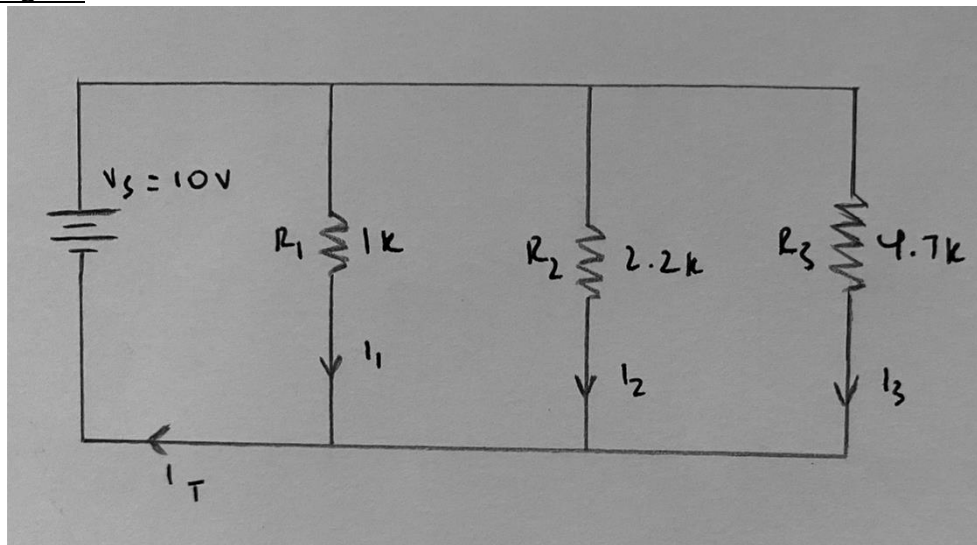

Components Required

Basic – Resistors

Sources – Power Sources – DC_Power, Ground

Manual Workings

$$V_S = 10 \text{ V}$$

$$1. \quad I_1 = \frac{V_S}{R_1}$$

$$= \frac{10}{1000}$$

$$= \underline{10 \text{ mA}}$$

$$I_2 = \frac{V_S}{R_2}$$

$$= \frac{10}{2200}$$

$$= \underline{4.5 \text{ mA}}$$

$$I_3 = \frac{V_S}{R_3}$$

$$= \frac{10}{4700}$$

$$= \underline{2.1 \text{ mA}}$$

$$2. \quad I_T = I_1 + I_2 + I_3 \quad \text{because they are in parallel.}$$

$$= 10 + 4.5 + 2.1$$

$$= \underline{16.6 \text{ mA}}$$


$$3. \quad R_{eq} = \frac{V_S}{I_T}$$

$$= \frac{10}{16.6 \times 10^{-3}}$$


$$= \underline{599.78 \text{ ohms}}$$

$$4. \quad V_{R1} = V_{R2} = V_{R3} = V_S = \underline{10 \text{ V}}$$

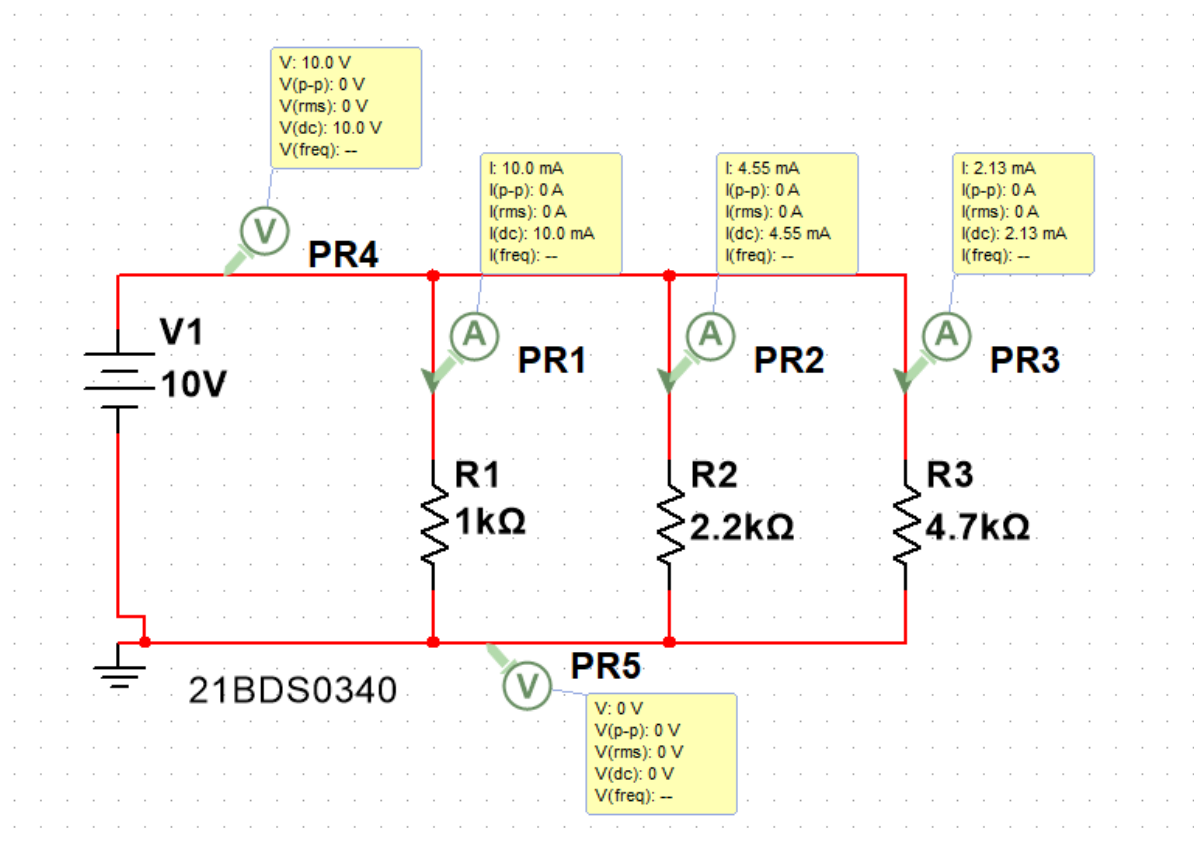Simulated Circuit Diagram for Finding Current and Voltage



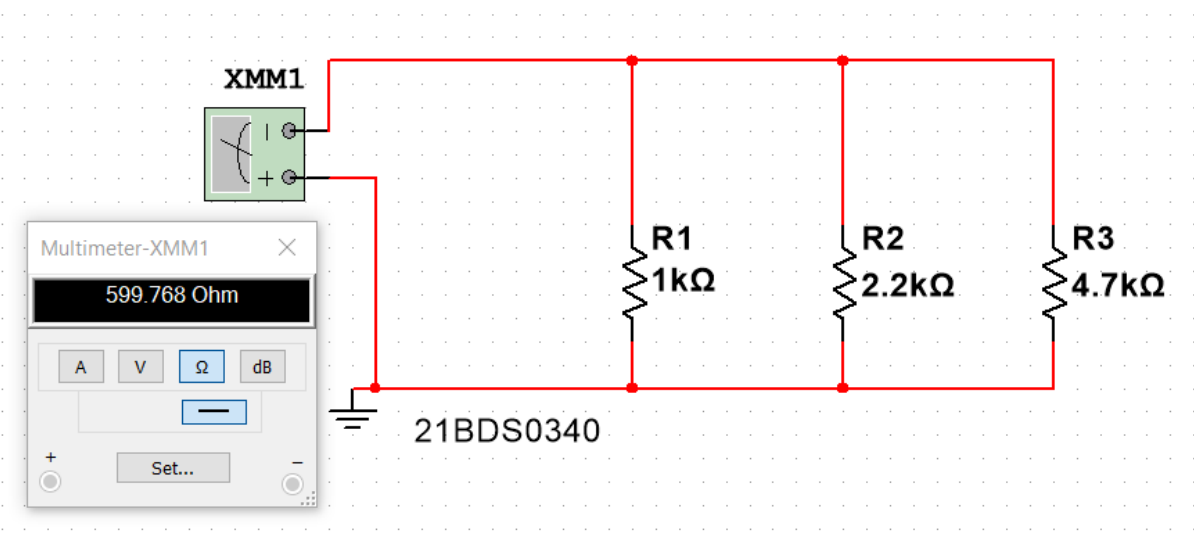Simulated Circuit Diagram for Finding Resistance




Results

NOTATION	MANUAL CALCULATIONS	SIMULATED RESULT
I_1	10 mA	10 mA
I_2	4.5 mA	4.5 mA
I_3	2.1 mA	2.1 mA
I_T	16.6 mA	16.6 mA
R_{eq}	599.78 ohms	599.78 ohms
V_{R1}	10 V	10 V
V_{R2}	10 V	10 V
V_{R3}	10 V	10 V

Exercise 3

Circuit Diagram

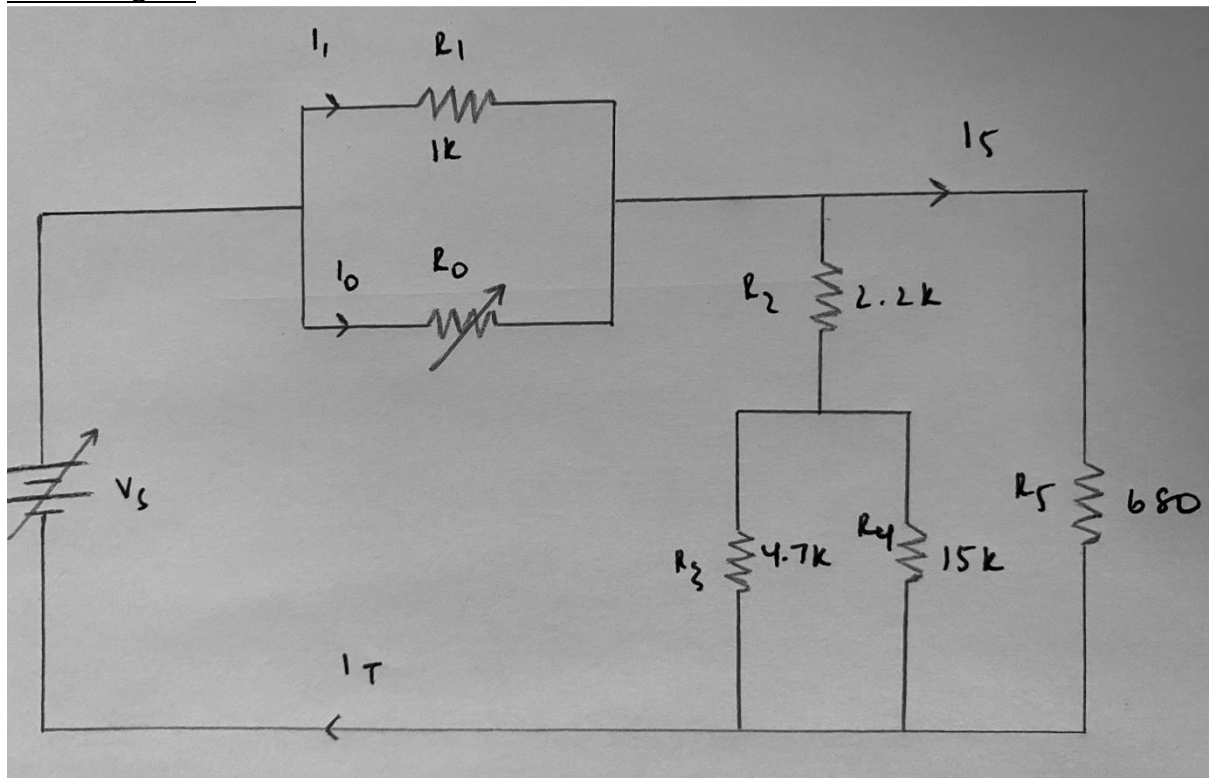

Components Required

Basic – Resistors

Sources – Power Sources – DC_Power, Ground

Manual Workings

$$1. V_s = 15V$$

$$R_0 = 500 \text{ ohms}$$

$$2. R_{xy} = \left(600^{-1} + \left(2200 + \left(4700^{-1} + 15000^{-1} \right)^{-1} \right)^{-1} \right)^{-1}$$
$$= \underline{608.41 \text{ ohms}}$$

$$I_T = \frac{V_s}{\left(\frac{1}{1000} + \frac{1}{500} \right) + 608.41}$$
$$= 15.93 \text{ mA}$$

$$I_1 = \frac{I_T R_0}{R_0 + R_1} = \underline{5.31 \text{ mA}} \text{ when } R_0 = 500$$

$$I_2 = \frac{I_T R_1}{R_0 + R_1} = \underline{10.62 \text{ mA}} \text{ when } R_0 = 500$$

$$I_T = \frac{V_s}{\left(\frac{1}{1000} + \frac{1}{5000} \right) + 608.41}$$
$$= 10.4 \text{ mA}$$

$$I_1 = \frac{I_T R_0}{R_0 + R_1} = \underline{8.67 \text{ mA}} \text{ when } R_0 = 5000$$

$$I_0 = \frac{I_T R_1}{R_0 + R_1} = \underline{1.73 \text{ mA}} \text{ when } R_0 = 5000$$

$$3. \quad V_{x4} = 15 - V_{R2}$$

$$= 15 - I_T \left(\frac{1}{1000} + \frac{1}{5000} \right)^{-1}$$

$$= 15 - 8.67$$

$$= \underline{6.33 \text{ V}}$$

$$I_{R2} = 1.09 \text{ mA}$$

$$V_{R4} = V_{x4} - V_{R2}$$

$$= 6.33 - 1.09 \times 2200 \times 10^{-3}$$

$$= \underline{3.93 \text{ V}}$$

$$V_{R5} = V_{x4}$$

$$= \underline{6.33 \text{ V}}$$

$$4 \text{ and } 5. \quad R_{x4} = 608.41 \text{ ohm}$$

$$R_{12} = 833.33 \text{ ohm}$$

$$V_{x4} = V_s - V_{12}$$

$$\Rightarrow V_{x4} = V_s - 833.33 \times I_{12}$$

$$\Rightarrow V_{x4} = V_s - 833.33 \times \frac{V_s}{R_{x4} + R_{12}}$$

$$\Rightarrow 8.5 = V_s - \frac{833.33 V_s}{1441.74}$$

$$\Rightarrow V_s = \underline{20.142 \text{ V}} \quad \text{if } V_{xy} = 8.5 \text{ V}$$

$$6. \quad I_0 = \frac{I_T R_1}{R_0 + R_1} \quad - (1)$$

$$\text{and } I_T = \frac{V_S}{\left(\frac{1}{R_1} + \frac{1}{R_0}\right)^{-1} + 608.41} \quad - (2)$$

$$(1) \quad I_T = \frac{I_0 (R_0 + R_1)}{R_1}$$

$$(2) \quad \frac{I_0 (R_0 + R_1)}{R_1} = \frac{V_S}{\left(\frac{1}{R_1} + \frac{1}{R_0}\right)^{-1} + 608.41}$$

$$\Rightarrow \frac{I_0 (R_0 + R_1)}{R_1} = \frac{V_S (R_1 + R_0)}{R_1 R_0 + 608.41 (R_1 + R_0)}$$

$$\Rightarrow R_1 R_0 + 608.41 (R_1 + R_0) = \frac{V_S R_1}{I_0}$$

$$\Rightarrow R_0 (R_1 + 608.41) = \frac{V_S R_1}{I_0} - 608.41 R_1$$

$$\Rightarrow R_0 = \frac{\frac{V_S R_1}{I_0} - 608.41 R_1}{R_1 + 608.41}$$

Putting values:


$$R_0 = \underline{1486.93 \text{ ohms}} \quad \text{for } I_0 \text{ to be } 5 \text{ mA}$$

$$\therefore I_S = \frac{I_T \times 5778.68}{5778.68 + 680} \quad \text{and } I_T = 12.4 \text{ mA}$$

$$= \underline{11.09 \text{ mA}}$$


$$I_T = \underline{12.4 \text{ mA}}$$

Simulated Circuit Diagram

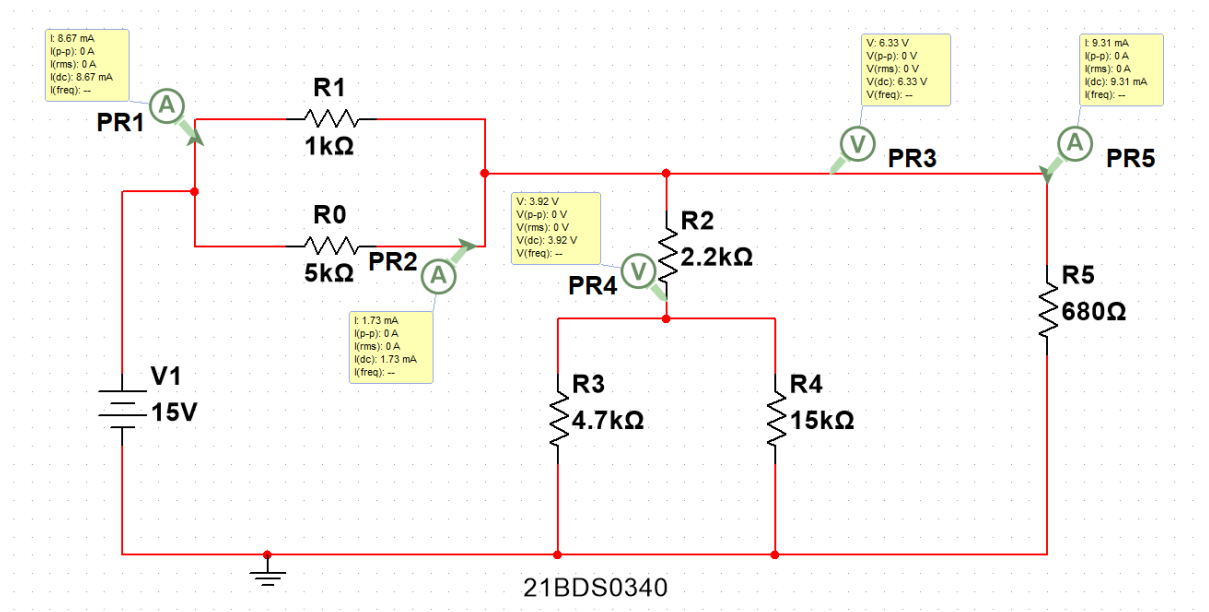


Part C: Study of Function Generator and CRO

Simulated Circuit Diagram

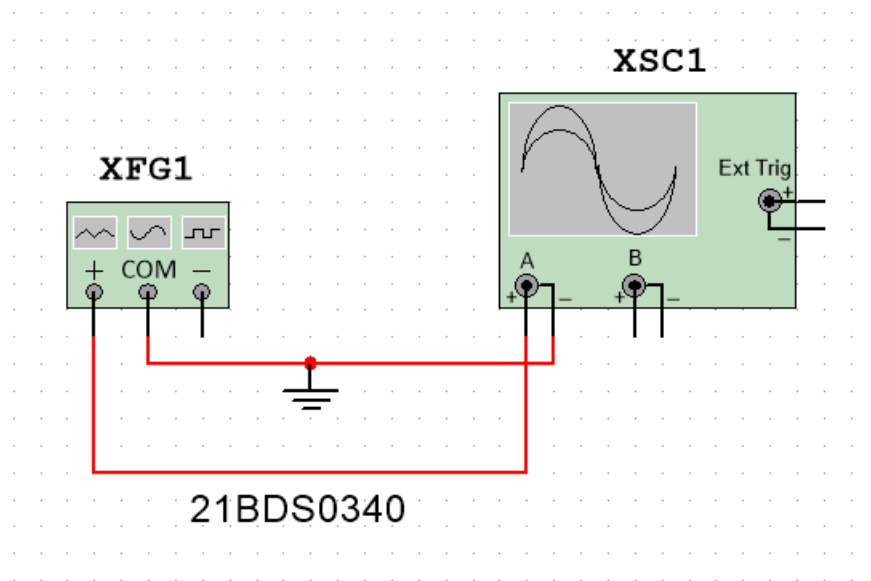

Simulated Sin Wave Output

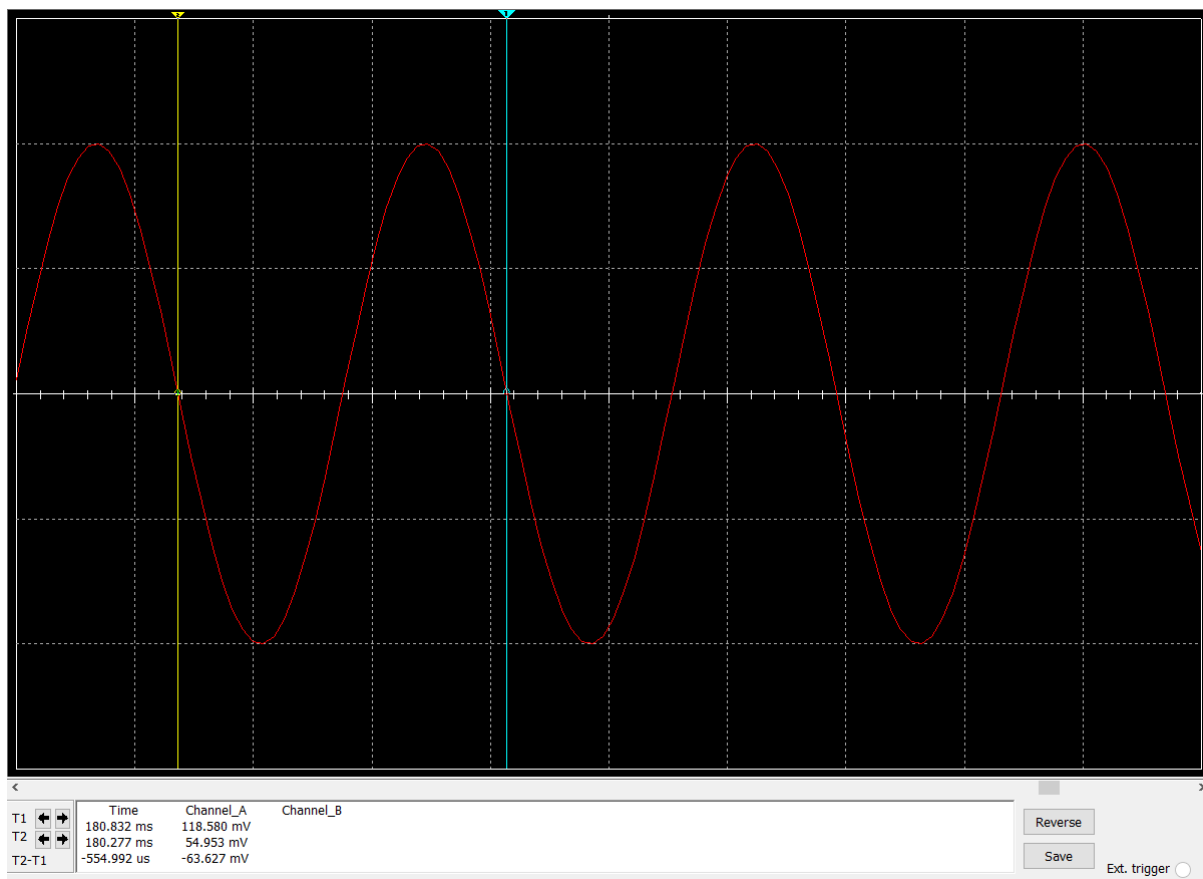

Components Required

Simulate – Instruments – Oscilloscope, Function Generator

Result

S. No.	Function Generator			CRO		
	Waveform Type	Amp (V)	Freq (Hz)	Amp (V)	Time Period (s)	Freq (Hz)
1	Sin	10	1.8k	10	554.82u	1.8k
2	Triangle	34	95M	34	10.482n	95M
3	Square	20	28	20	71.344m	14

Verification Message



KRISHNA CHAITHANYA MUNTHA 12:50

21BDS0340-EXPERIMENT 1 VERIFIED


Exercise No.: 2

Date: 24/02/22

VI Characteristics of PN Junction Diode

Forward Bias

Circuit Diagram

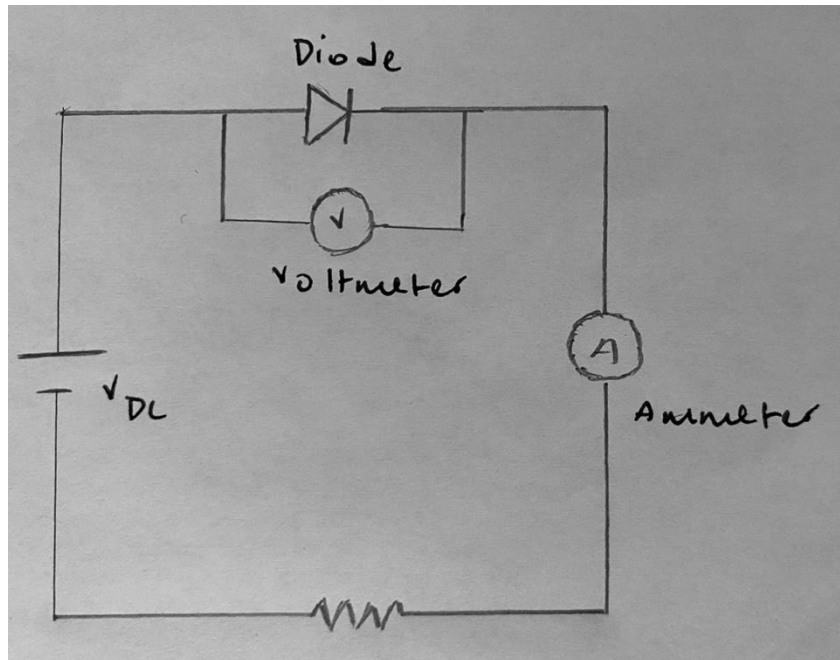

Components Required


Basic – Resistors

Sources – Power Sources – DC_Power, Ground

Diodes – 1N4007G

Toolbars – Measurement Components – Ammeter, Voltmeter


Simulated Circuit Diagram

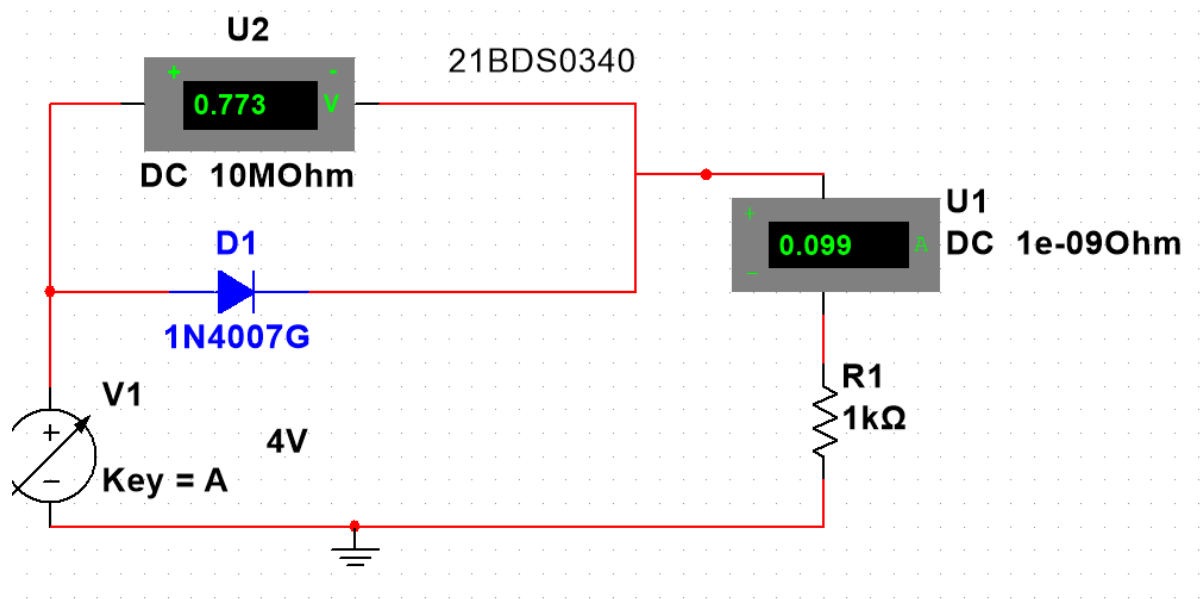

Readings


S. No.	Supply voltage (v)	Diode voltage (v)	Circuit current (A)
1	0.2	0.199	5.31×10^{-7}
2	0.4	0.377	2.3×10^{-5}
3	0.6	0.462	1.38×10^{-4}
4	0.8	0.499	3.01×10^{-4}
5	1	0.521	4.8×10^{-4}
6	2	0.572	1.43×10^{-3}
7	3	0.596	2.4×10^{-3}
8	4	0.612	3.39×10^{-3}
9	5	0.624	4.38×10^{-3}
10	6	0.634	5.37×10^{-3}
11	7	0.642	6.36×10^{-3}
12	8	0.648	7.35×10^{-3}
13	9	0.654	8.35×10^{-3}
14	10	0.66	9.34×10^{-3}

Graph

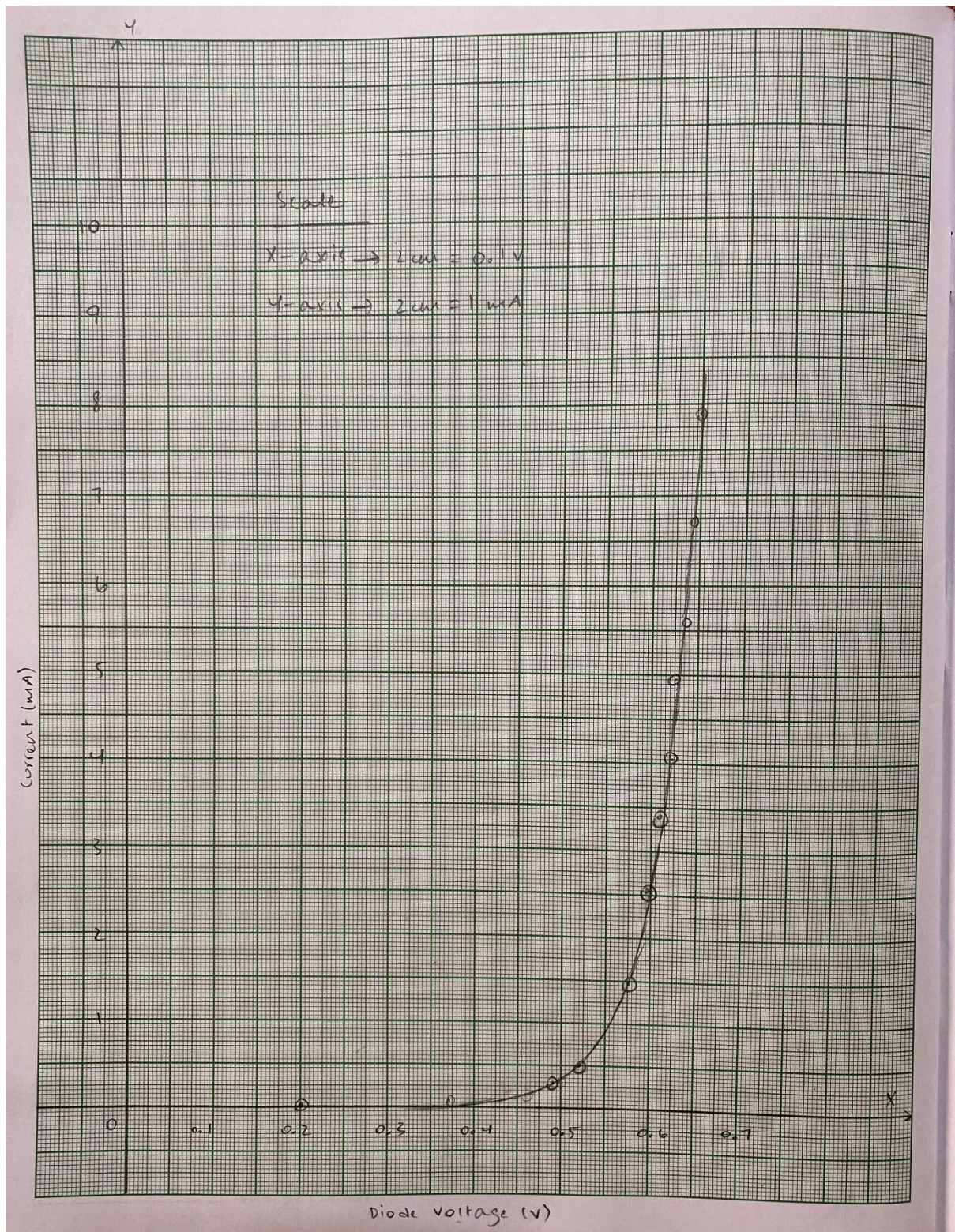

Reverse Bias

Circuit Diagram

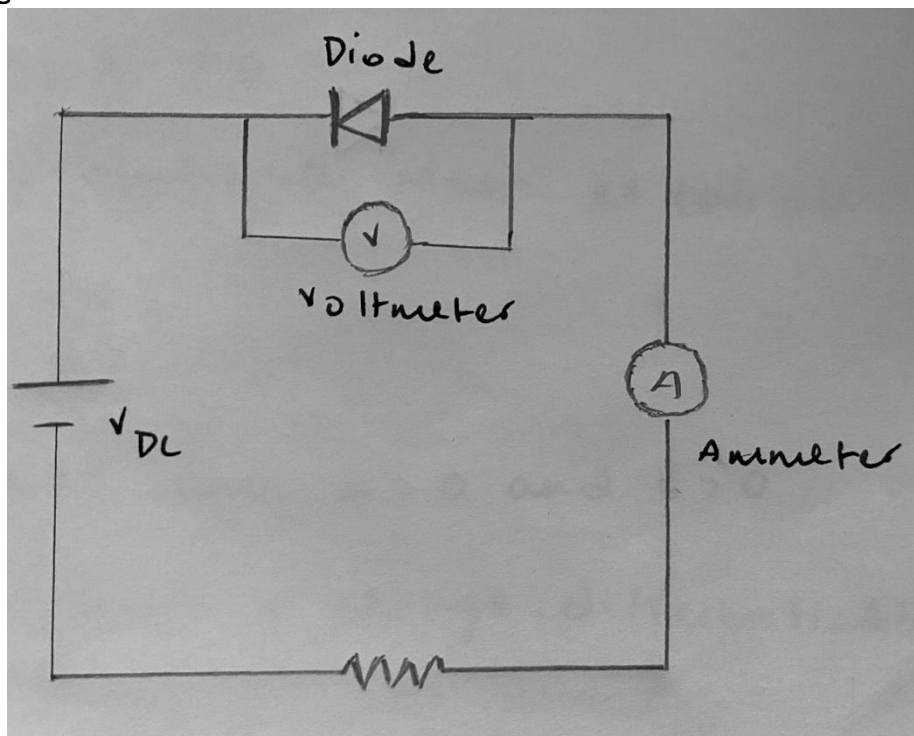

Components Required


Basic – Resistors

Sources – Power Sources – DC_Power, Ground

Diodes – 1N4007G

Toolbars – Measurement Components – Ammeter, Voltmeter


Simulated Circuit Diagram

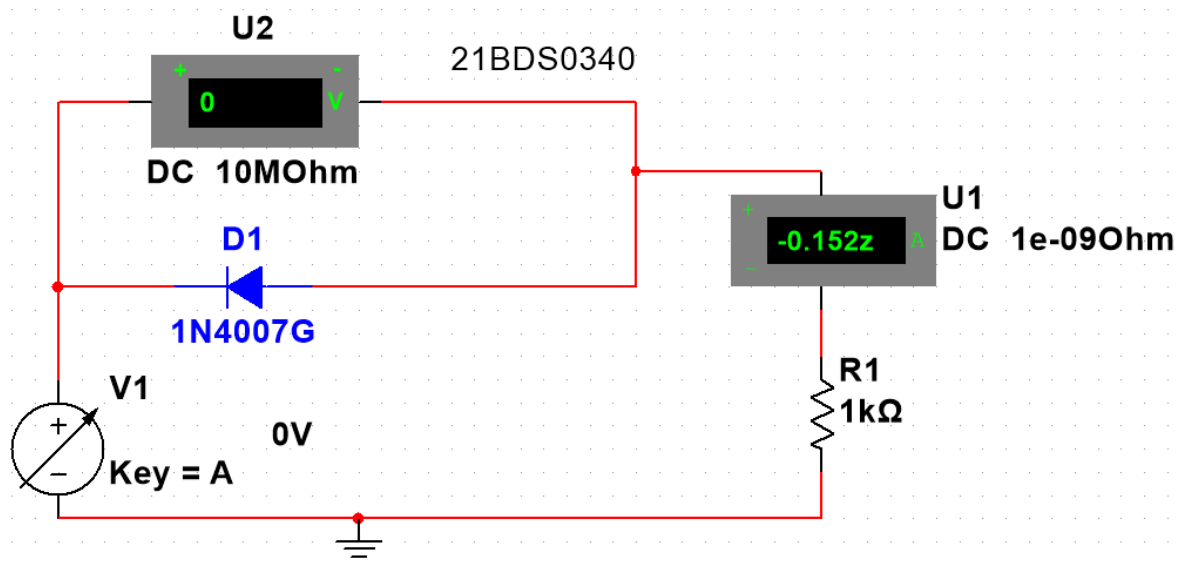


Readings

S. No.	Supply Voltage (V)	Diode Voltage (-V)	Diode/circuit current (A)
1	0.2	0.2	2.7×10^{-8}
2	0.4	0.4	4.7×10^{-8}
3	0.6	0.6	6.7×10^{-8}
4	0.8	0.8	8.7×10^{-8}
5	1	1	1.07×10^{-7}
6	3	3	3.07×10^{-7}
7	6	5.999	6.07×10^{-7}
8	9	8.999	9.07×10^{-7}
9	12	11.999	1.21×10^{-6}
10	15	14.998	1.51×10^{-6}
11	18	17.998	1.81×10^{-6}
12	21	20.998	2.11×10^{-6}
13	24	23.998	2.41×10^{-6}
14	27	26.997	2.71×10^{-6}
15	30	29.997	3.01×10^{-6}

Graph

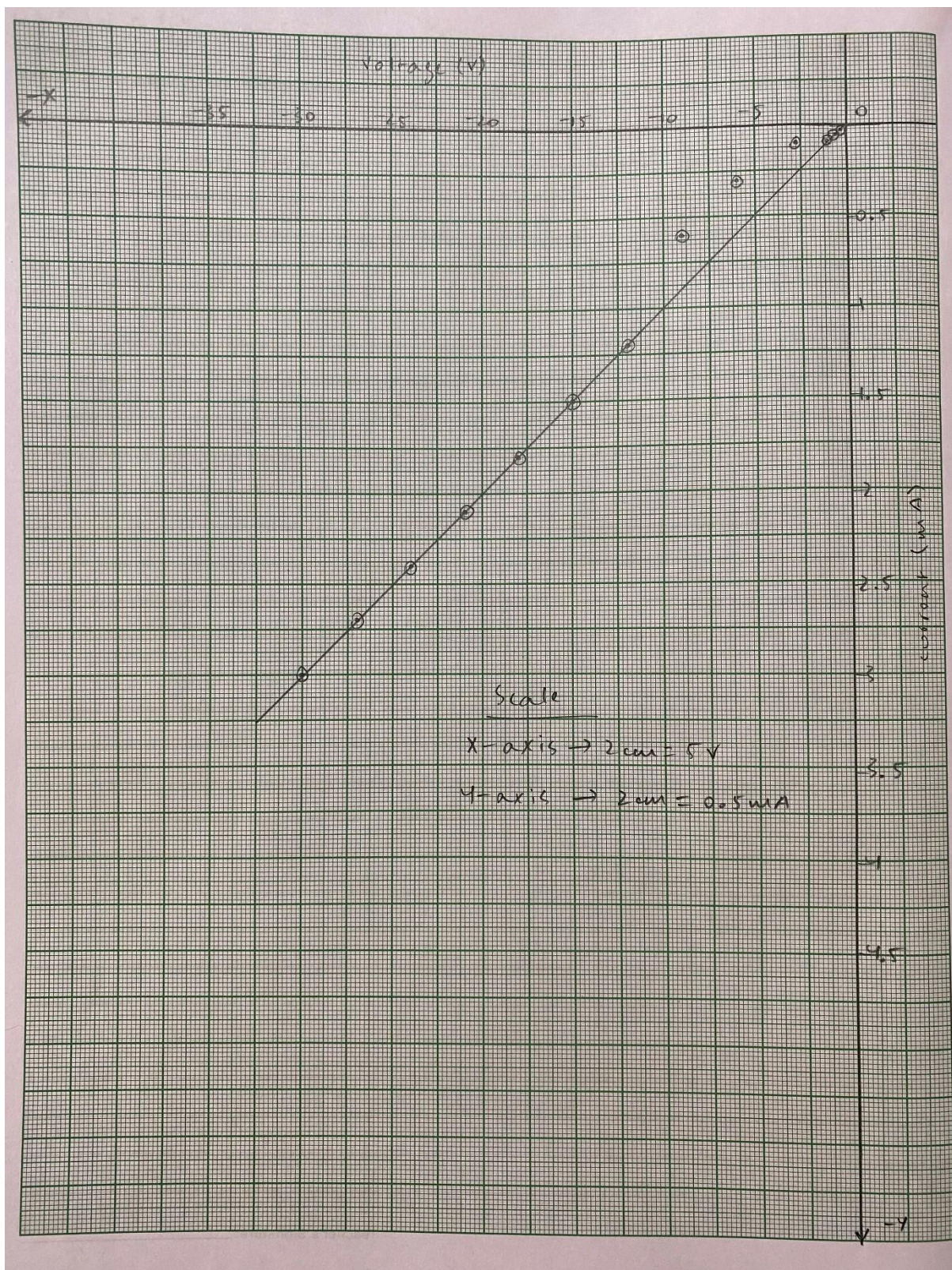

Verification Message

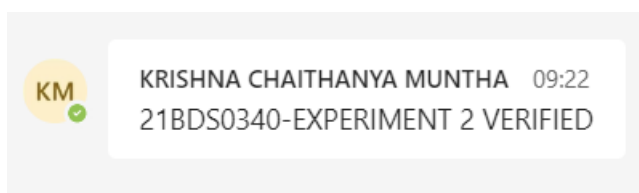

Reg. No: 21BDS0340

Name: Abhinav Dinesh Srivatsa

Date: 27/09/2021