

21BDS0340

Abhinav Dinesh Srivatsa

Digital Systems Design Lab

Task 2

S. No.	Components	Page No.	Student Check Mark	RA Check Mark
1	Aim	2	✓	
2	Components required and tools required	2	✓	
3	Half adder diagram with truth table	2	✓	
4	Half adder with gate level in Verilog	3	✓	
5	Half adder with dataflow in Verilog	3	✓	
6	Half adder with behavioural in Verilog	3	✓	
7	Test bench for half adder and snip of output waveform	4	✓	
8	Full adder diagram with truth table	5	✓	
9	Full adder with gate level in Verilog	5	✓	
10	Full adder with dataflow in Verilog	6	✓	
11	Full adder with behavioural in Verilog	6	✓	
12	Test Bench for full adder and snip of output waveform	6	✓	
13	Full subtractor diagram with two half subtractors	7	✓	
14	Full subtractor with structural modelling in Verilog	8	✓	
15	Test bench for full subtractor and snip of output waveform	8	✓	

Aim

1. Design half adder and implement in gate-level, dataflow, behavioural, testbench using Verilog.
2. Design full adder with basic gates and implement in gate-level, dataflow, behavioural, testbench using Verilog.
3. Design full subtractor with two half subtractors and implement in any one of the levels, testbench using Verilog.

Components Required

- a. AND, OR, NOT and XOR gates
- b. 5V voltage source
- c. Led indicator


Tools Required

- a. Multisim simulator
- b. Truth table display
 - <http://www.32x8.com/>
- c. Modelsim

Half Adder Diagram with Truth Table

Submit			SUM		
	A	B	0	1	x
0	0	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
1	0	1	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
2	1	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
3	1	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
Submit					

Submit			CARRY		
	A	B	0	1	x
0	0	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
1	0	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	1	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	1	1	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
Submit					

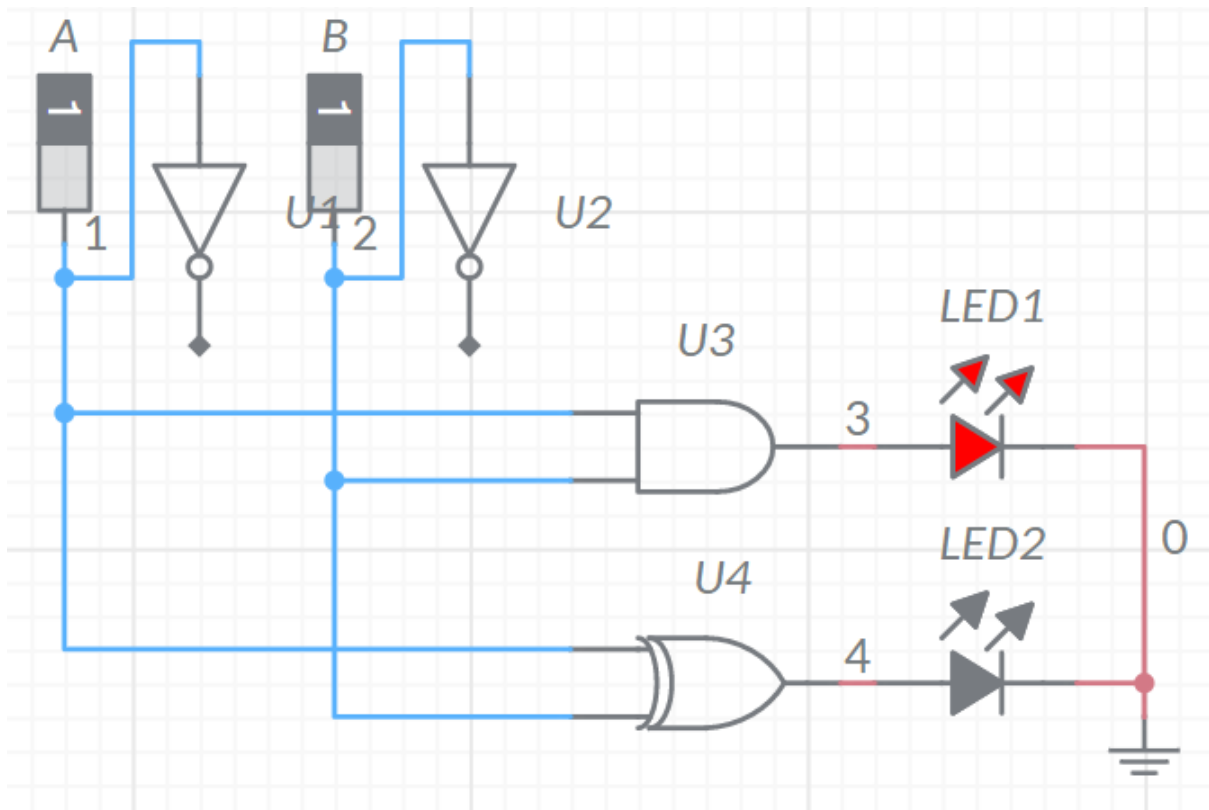

Half Adder with Gate Level in Verilog

```
// Gate Level
module halfadder(a, b, sum, carry);
    input a, b;
    output sum, carry;
    xor g1(sum, a, b);
    and g2(carry, a, b);
endmodule
```

Half Adder with Dataflow in Verilog

```
// Dataflow
module halfadder(a, b, sum, carry);
    input a, b;
    output sum, carry;
    assign sum = a ^ b;
    assign carry = a & b;
endmodule
```

Half Adder with Behavioural in Verilog

```
// Behavioural
module halfadder(a, b, sum, carry);
    input a, b;
    output reg sum, carry;
```

```

always @(a,b);
begin
    sum = a ^ b;
    carry = a & b;
end
endmodule


```

Test Bench for Half Adder and Snip of Output Waveform

```

module test;
    reg a, b;
    wire sum, carry;
    halfadder ha1(a, b, sum, carry);
    initial
    begin
        a = 0; b = 0;
        #100
        a = 0; b = 1;
        #100
        a = 1; b = 0;
        #100
        a = 1; b = 1;
    end
endmodule

```

 


Note: To revert to EPWave opening in a new browser window, set that option on your user page.

Full Adder Diagram with Truth Table

Submit				SUM		
	A	B	C	0	1	x
0	0	0	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
1	0	0	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
2	0	1	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
3	0	1	1	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
4	1	0	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
5	1	0	1	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
6	1	1	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
7	1	1	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
Submit						

Submit				CARRY		
	A	B	C	0	1	x
0	0	0	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
1	0	0	1	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
2	0	1	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
3	0	1	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
4	1	0	0	<input type="radio"/>	<input checked="" type="radio"/>	<input type="radio"/>
5	1	0	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
6	1	1	0	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
7	1	1	1	<input checked="" type="radio"/>	<input type="radio"/>	<input type="radio"/>
Submit						

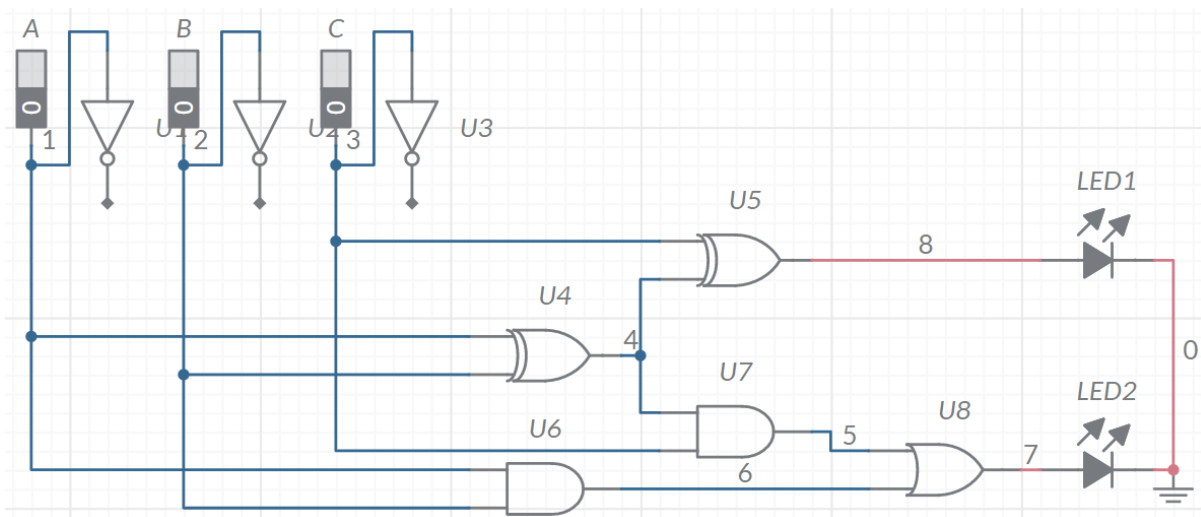**Full Adder with Gate Level in Verilog**

```
// Gate Level
module fulladder(a, b, c, sum, carry);
    input a, b, c;
    output sum, carry;

    xor(xor1, a, b);
```

```

    and(prod1, a, b);
    and(prod2, xor1, c);
    or(carry, prod1, prod2);

    xor(sum, xor1, c);
endmodule

```

Full Adder with Dataflow in Verilog

```

// Dataflow
module fulladder(a, b, c, sum, carry);
    input a, b, c;
    output sum, carry;

    assign xor1 = a ^ b;
    assign prod1 = a & b;
    assign prod2 = xor1 & c;
    assign carry = prod1 & prod2;

    assign sum = xor1 ^ c;
endmodule

```

Full Adder with Behavioural in Verilog

```

// Dataflow
module fulladder(a, b, c, sum, carry);
    input a, b, c;
    output reg sum, carry;
    always @(*);

    begin
        xor1 = a ^ b;
        prod1 = a & b;
        prod2 = xor1 & c;
        carry = prod1 & prod2;

        sum = xor1 ^ c;
    end
endmodule

```

Test Bench for Full Adder and Snip of Output Waveform

```


module test;
    reg a, b, c;
    wire sum, carry;
    fulladder fa1(a, b, c, sum, carry);
    initial

```

```


begin
a = 0; b = 0; c = 0;
#100
a = 0; b = 0; c = 1;
#100
a = 0; b = 1; c = 0;
#100
a = 0; b = 1; c = 1;
#100
a = 1; b = 0; c = 0;
#100
a = 1; b = 0; c = 1;
#100
a = 1; b = 1; c = 0;
#100
a = 1; b = 1; c = 1;
end
endmodule

```

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

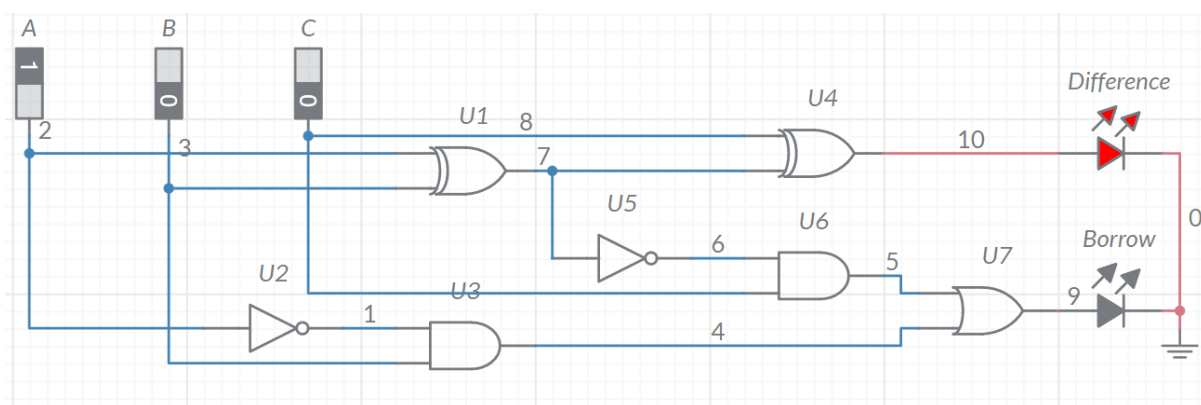Full Subtractor Diagram with Two Half Subtractors



Full Subtractor with Structural Modelling in Verilog

```

module halfsubtractor(x, y, b, d);
    input x, y;
    output b, d;
    xor(d, x, y);
    not(notx, x);
    and(b, notx, y);
endmodule

module fullsubtractor(x, y, z, b, d);
    input x, y, z;
    output b, d;

    wire b1, d1, b2;

    halfsubtractor hs1(x, y, b1, d1);
    halfsubtractor hs2(d1, z, b2, d);
    or(b, b1, b2);
endmodule


```

Test Bench for Full Subtractor and Snip of Output Waveform

```

module test;
    reg a, b, c;
    wire borrow, diff;
    fullsubtractor ha1(a, b, c, borrow, diff);
    initial
    begin
        a = 0; b = 0; c = 0;
        #100
        a = 0; b = 0; c = 1;
        #100
        a = 0; b = 1; c = 0;
        #100
        a = 0; b = 1; c = 1;
        #100
        a = 1; b = 0; c = 0;
        #100
        a = 1; b = 0; c = 1;
        #100
        a = 1; b = 1; c = 0;
        #100
        a = 1; b = 1; c = 1;
    end
endmodule

```

 Note: To revert to EPWave opening in a new browser window, set that option on your user page.