

MEASUREMENT OF ELECTRICAL POWER AND ENERGY

Ex. No. : 8

Date: 6/12/2021

Aim

To measure the power and energy consumed by a single-phase load.

Materials Required

S. No.	Name of the Apparatus	Range / Type	Quantity
1	Ammeter	(0 – 10 A) MI	1 No.
2	Voltmeter	(0 – 300 V) MI	1 No.
3	Wattmeter	300 V, 10 A, UPF	1 No.
4	Energy meter	1-phase, digital	1 No.
5	Resistive load	5 kW	1 No.
6	Stop clock	-----	1 No.
7	Wires	1 sq. mm"	As required

Theory

The watt-hour meter is an instrument used for measuring energy. As energy is the product of power and time; the watt-hour meter must take into consideration both of these factors. Induction type of energy meters are universally used for measurement of energy in domestic and industrial AC circuits. The term testing includes the checking of the actual registration of the meter as well as the adjustments done to bring the errors of the meters within the prescribed limits.

Direct loading method is similar to the one explained in the calibration of wattmeter. Here a standard wattmeter is used for comparing the values. When the capacity of a meter under test is high, a test with the ordinary loading arrangements would involve a considerable waste of power. To avoid this "phantom or fictitious" loading arrangements are employed. These consist in supplying the pressure circuit from a circuit of the required normal voltage, and the current circuit from a separate low voltage supply. This means that the total power supplied for the test is that due to the small pressure coil current at normal voltage plus that due to the load current at a low voltage and the total power is therefore only a comparatively small amount.

FORMULAE USED

1. Actual power = $W \times \text{Multiplication factor}$
Where W – Observed wattmeter reading
2. Apparent power = VI watts
Where V – Voltmeter reading
i. I – Ammeter reading
3. Power Factor, $\cos\phi = \text{Actual Power} / \text{Apparent Power}$
4. True energy = $(\text{wattmeter reading} \times \text{time}) / 60 \times 60 \times 1000$ Kwh
5. Recorded energy = $(\text{No of Rev}) / \text{energy meter constant}$ Kwh
6. % Energy = $(\text{recorded energy} - \text{true energy}) \times 100 / \text{True energy}$

Procedure

1. Collect the materials required for this experiment.
2. Make the connections as shown in circuit diagram.
3. After closing the DPST switch adjust the auto-transformer to the specified voltage of the energy meter.
4. Switch 'ON' some specific load. Note down Ammeter, Voltmeter and wattmeter readings. Also note down the time taken by energy meter disc to complete a specified number of revolutions using stop clock. This is repeated for different load condition.
5. True energy is calculated by multiplying the wattmeter reading and the time.
6. Recorded energy is obtained using energy meter constant and no. of revolution.
7. Result are tabulated (Refer Table) and a graph between percentage error and True energy is drawn.

Precautions

1. Energize the circuit with the presence of Lab instructor / Faculty.
 2. Auto transformer should be in minimum voltage position.
 3. All the loads should be in 'OFF' position.
 4. No part of a live circuit should be touched by the bare hand.
 5. Keep the body, or any part of it, out of the circuit.
 6. Keep the work area and workbench clear of items not used in the experiment.
 7. When disassembling a circuit, first remove the source of power.
-


Sample Calculations

$$\text{True Energy} = \frac{\text{wattmeter reading} * \text{time}}{60 * 60 * 1000} \text{ KWH}$$

$$\text{Recorded Energy} = \frac{\text{No of Revolutions}}{\text{Energy meter constant}} = 1200 \text{ rev/kwh}$$

$$\% \text{Error} = \frac{RE - TE}{TE} * 100$$

Circuit Diagram

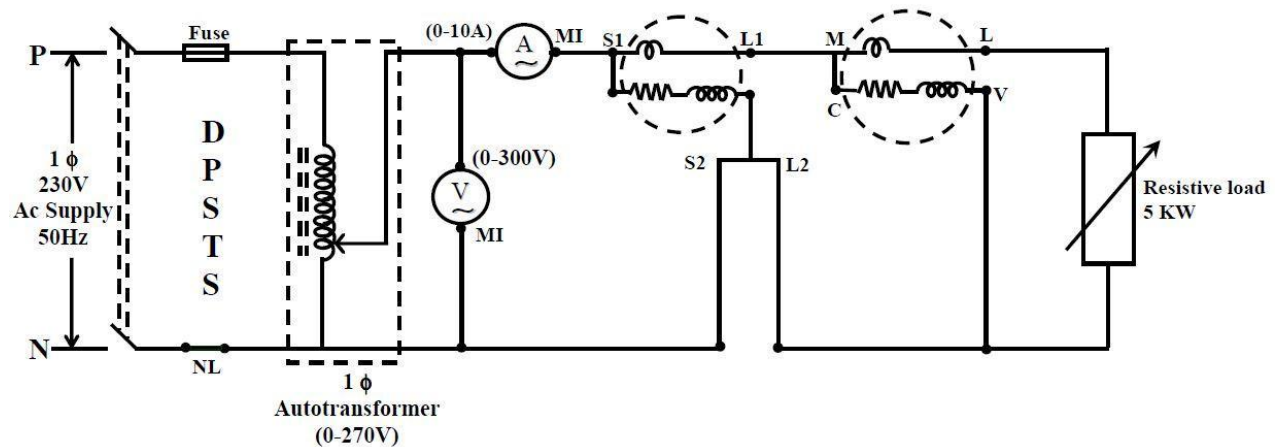

Tabulations

Load(W)	S. No.	Voltmeter reading (V)	Ammeter reading (I)	Wattmeter reading (W)	No. of revolutions	Time taken by Disc (T)	Recorded energy	True energy	Error
		Volts	Amps	Watts		Seconds			
250	1	230	0.96	120*2	5	64	0.00426	0.00416	2.4
500	2	230	1.93	255*2	5	30.7	0.00434	0.00416	4.32
750	3	230	2.7	350*2	5	22.4	0.00434	0.00416	4.32
1000	4	230	3.63	470*2	5	16.6	0.00432	0.00416	3.84
1250	5	230	4.44	570*2	5	13.6	0.00430	0.00416	3.33
	6								

Name of Laboratory : Basic Electrical Engineering Lab

Lab Subject Code : EEE101L

Name of School : SELECT

Result

Net Power Consumed is 416 watt.

Power factor =1

