

Ex. No.: 4

Date: 08/11/2021

## Verification of Maximum Power Transfer Theorem

---

Aim:

To verify the maximum power transfer theorem using Thevenin's theorem with manual calculations and an ORCAD simulation

Apparatus:


ORCAD / Capture CIS: Analog Library – R

Source Library – Vdc, Idc

Ground (GND) – 0 (zero)

Simulation Settings: Analysis Type – DC Sweep

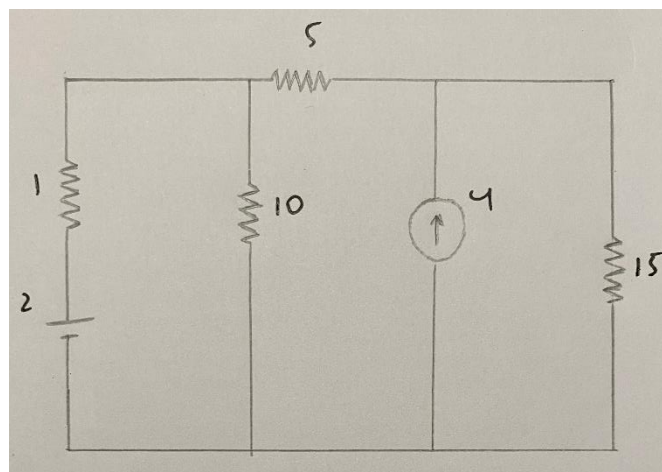Circuit Diagram for Maximum Power Transfer Theorem:




Statement:

Maximum power transfer theorem states that the DC voltage source will deliver maximum power to the variable load when it is equal to the thevenin resistance.

## Manual Calculations:

Finding Thevenin Voltage ( $V_{th}$ ):

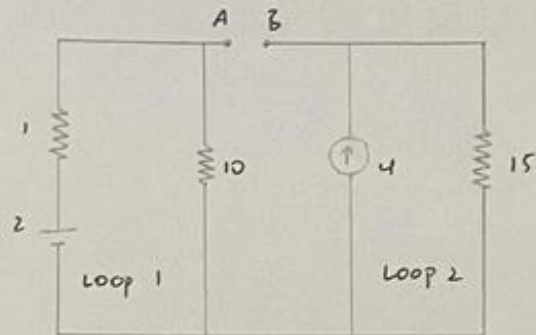

Loop 1:

$$I = \frac{2}{1 + 10}$$

$$\Rightarrow I = 2/11 = 0.182$$

$$A = 2 - I \cdot (1)$$

$$\Rightarrow A = 2 - 0.182$$

$$\Rightarrow A = 1.82 \text{ V}$$

Loop 2

$$V = IR$$

$$\Rightarrow V = 4 \times 15$$


$$\Rightarrow V = 60 \text{ V}$$

$$V_{th} = V_B - V_A$$

$$\Rightarrow V_{th} = 60 - 1.82$$


$$\Rightarrow V_{th} = 58.18 \text{ V}$$

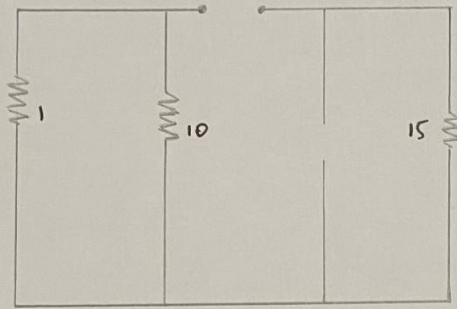Finding Thevenin Resistance ( $R_{th}$ ):



$$R_{th} = \frac{1 \times 10}{1 + 10} + 15 = \frac{10}{11} + 15 = \frac{175}{11} = 15.91 \text{ ohm}$$

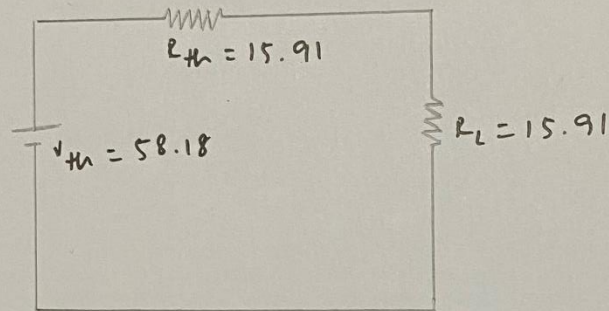Finding Thevenin Current ( $I_{th}$ ) and Maximum Power:




$$I_{th} = \frac{V_{th}}{R_{th} + R_L} = \frac{V_{th}}{2R_{th}} = \frac{58.18}{31.81} = 1.83 \text{ A}$$

$$\therefore \text{Maximum power} = I_{th}^2 \cdot R_{th}$$

$$= 1.83^2 \times 15.91$$

$$P_{max} = 53.19 \text{ W}$$

## Simulation Circuit:

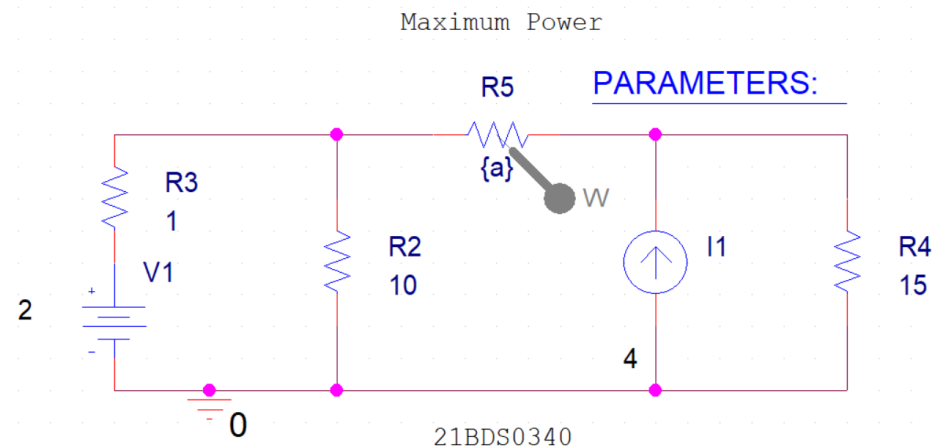

## Procedure:


1. Press 'P' to place a part
2. Press 'R' to filter for a resistor
3. Click analog resistor and place 4 referring to the circuit diagram
4. Search for 'vdc' and 'ldc' like resistors and place 1 of each
5. Search for params next and place it anywhere
6. Add a new property called 'a' with a value 1
7. change the load resistance in the circuit diagram to  $\{a\}$ , a variable in params
8. Run the simulation by creating a new DC sweep
9. set to global parameter, put in the name as 'a'
10. set start as 1, end as 200 and increment as 0.5, lower increments result in a smoother graph
11. Run the simulation and find the maximum power and its corresponding resistance.

Result:

Power vs Resistance Graph:



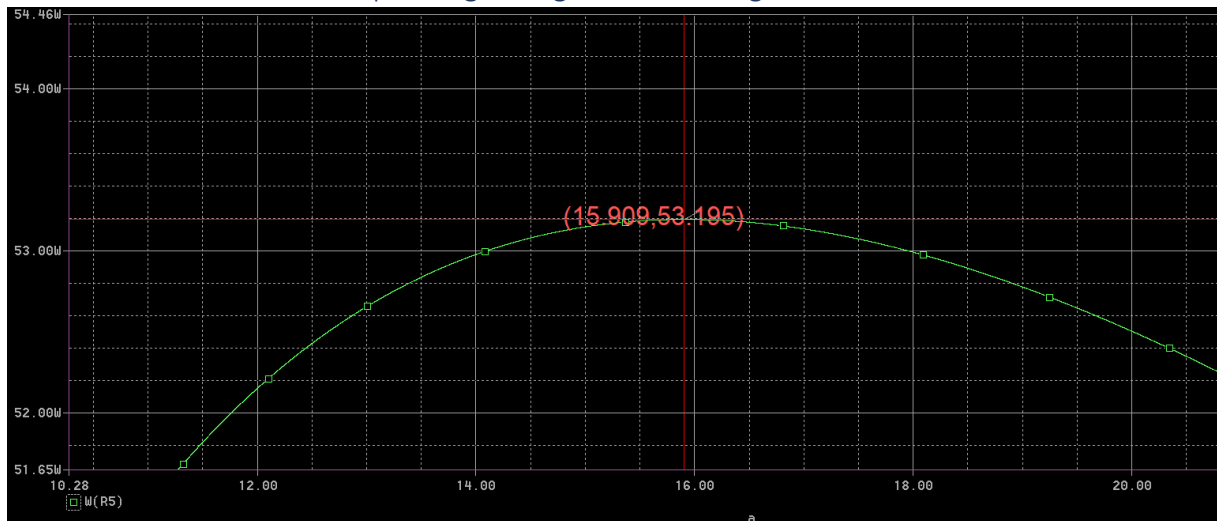Maximum Power and Corresponding Voltage Values Enlarged:



### Maximum Power Transfer Theorem

NOTATION	MANUAL CALCULATIONS	SIMULATED RESULT
$R_{TH}$	15.91	15.909
$P_{MAX}$	53.19	53.195

Inference:

By comparing our manual result to the simulation, we can see that the maximum power transfer theorem works in this circuit.