

21BDS0340

Abhinav Dinesh Srivatsa

Digital Systems Design Lab

## Task 3

S. No.	Components	Page No.	Student Check Mark	RA Check Mark
	PART I-Multiplexer based Design	4	✓	
1	Aim	4	✓	
2	Components Required and Tools Required	4	✓	
3	Procedure	4	✓	
4	Pin diagram	4	✓	
5	Truth Table and Boolean expression of Multiplexer, Demultiplexer.	5	✓	
6	Multiplexer Theory	7	✓	
7	Demultiplexer Theory	7	✓	
8	Block diagram/Circuit diagram for implementing 16:1 MUX using 8:1 MUX	7	✓	
9	Block diagram and Circuit diagram for implementing 8:1 MUX using 4:1 MUX	7	✓	
10	Block diagram and Circuit diagram for implementing 4:1 MUX using 2:1 MUX	8	✓	
11	SOP canonical expression of MUX and circuit implemented in MUX	8	✓	
12	POS canonical expression of MUX and circuit implemented in MUX	8	✓	
13	Circuit diagram of 2:1 MUX Circuit using SOP Equation --- AOI circuit	9	✓	
14	Circuit diagram of 2:1 MUX Circuit using POS Equation --- OAI circuit	9	✓	
15	Circuit diagram of 2:1 MUX Circuit using SOP	10	✓	

	Equation --- NAND circuit			
16	Circuit diagram of 2:1 MUX Circuit using POS Equation --- NOR circuit	10	✓	
17	Implementation steps for Task I and II using 4:1 Multiplexer	11	✓	
18	Implementation steps for Task I and II using 8:1 Multiplexer	11	✓	
19	Multisim live / Circuitverse.org Simulation link for Multiplexer based circuit implemented using 8:1 Multiplexer	12	✓	
20	Multisim live / Circuitverse.org Simulation link for Multiplexer based circuit implemented using 4:1 Multiplexer	13	✓	
21	Verilog code: SL	13	✓	
22	Verilog code: BL	14	✓	
23	Verilog code: DFL	15	✓	
24	Verilog code: Conditional Operator	16	✓	
25	Test Bench	17	✓	
26	Snip of Output waveform with respective code	18	✓	
27	Online Verilog code Simulation links	18	✓	
28	Result	18	✓	
29	Inference	18	✓	
	PART II - Demultiplexer / Decoder based Design			
1	Aim	19	✓	
2	Components Required and Tools Required	19	✓	
3	Procedure	19	✓	
4	Pin diagram	19	✓	
5	Truth Table and Boolean expression of Encoder (4:2, 8:3), Decoder (2:4, 3:8) with active low and active high logic.	19	✓	

6	Block diagram for implementing 3:8 Decoder using 2:4 Decoder	✓	20	
7	Block diagram for implementing 2: 4 Decoder using 1:2 Decoder	✓	20	
8	Decoder theory	✓	20	
9	Encoder and Priority Encoder Theory	✓	20	
10	AOI logic circuit of 2:4 Decoder	✓	21	
11	NAND logic circuit of 2:4 Decoder	✓	21	
12	AOI logic circuit of 4:2 encoder	✓	22	
13	NAND logic circuit of 4:2 encoder	✓	22	
14	Implementation steps for Task I & II using Decoder	✓	23	
15	Proof of Task I (SOP) implemented using Decoder Active Low logic in simulator using snipping tool	✓	24	
16	Proof of Task I (SOP) implemented using Decoder Active High logic in simulator using snipping tool	✓	25	
17	Proof of Task I (POS) implemented using Decoder Active Low logic in simulator using snipping tool	✓	24	
18	Proof of Task I (POS) implemented using Decoder Active High logic in simulator using snipping tool	✓	25	
19	Verilog code for 2:4 Decoder (BL, DFL)	✓	26	
20	Verilog code of 3:8 Decoder (BL, DFL)	✓	26	
21	Verilog code for 2:4 and 3:8 Decoder (SL)	✓	26	
22	Verilog Test Bench of Decoder	✓	27	
23	Snip of Verilog code output with links	✓	27	
24	Result	✓	27	
25	Inference	✓	27	

## Part I – Multiplexer Based Design

### Aim

Using Reg.no. formulate expressions in SOP and POS for F and F'. Implement the circuits using only

- Design 16:1 Multiplexer using 8:1 Multiplexer constructed using 4:1 Multiplexer constructed using 2:1 Multiplexer.
- Give the Internal structure of 2:1 Multiplexer using SOP, POS, NAND, NOR logic design, CMOS, and transmission gates.
- Implement a Combinational circuit framed by your registration number using only
  - 16:1 Multiplexer.
  - 8:1 Multiplexer.
- Write the Verilog code for Multiplexer in different styles and verify the results using the truth table and show the output waveform.
- Show the steps and procedure in the tool used.

### Components Required

- AND, OR, NOT, NAND and NOR gates
- 5V voltage source
- Led indicator


### Tools Required


- Multisim simulator

### Procedure

- Draw circuit diagrams to convert X:1 mux to X/2:1 mux till 2:1
- Write SOP and POS canonical forms of mux equation
- Simplify registration number using implementation table and represent with mux

### Pin Diagram

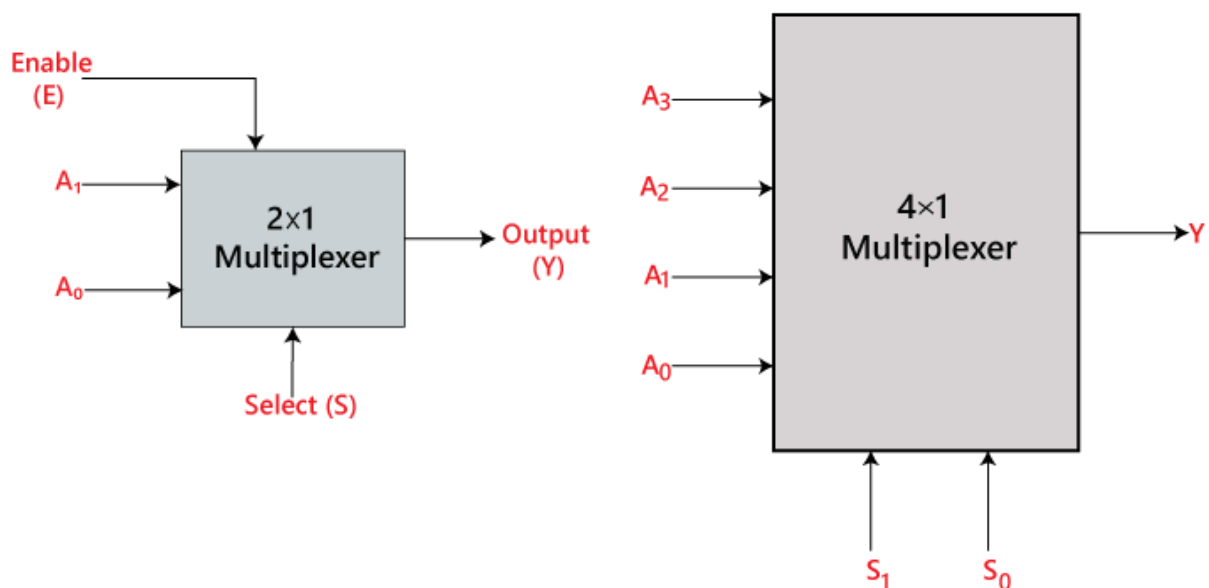

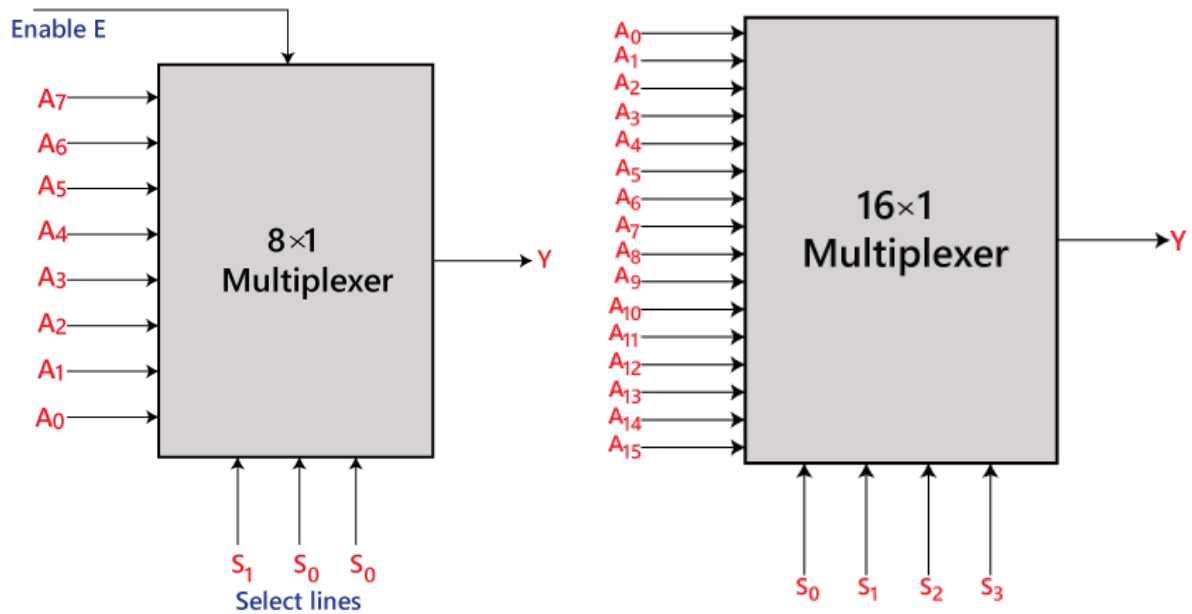

### Truth Table and Boolean expression of Multiplexer, Demultiplexer

Multiplexer:

Binary Equivalent	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	Y
0	0	0	0	0	A <sub>0</sub>
1	0	0	0	1	A <sub>1</sub>
2	0	0	1	0	A <sub>2</sub>
3	0	0	1	1	A <sub>3</sub>
4	0	1	0	0	A <sub>4</sub>
5	0	1	0	1	A <sub>5</sub>
6	0	1	1	0	A <sub>6</sub>
7	0	1	1	1	A <sub>7</sub>
8	1	0	0	0	A <sub>8</sub>
9	1	0	0	1	A <sub>9</sub>
10	1	0	1	0	A <sub>10</sub>
11	1	0	1	1	A <sub>11</sub>
12	1	1	0	0	A <sub>12</sub>
13	1	1	0	1	A <sub>13</sub>
14	1	1	1	0	A <sub>14</sub>
15	1	1	1	1	A <sub>15</sub>

$$Y = A_0.S_0'S_1'S_2'S_3' + A_1.S_0'S_1'S_2'S_3 + A_2.S_0'S_1'S_2S_3' + A_3.S_0'S_1'S_2S_3 + A_4.S_0'S_1S_2'S_3' + A_5.S_0'S_1S_2'S_3 + A_6.S_0'S_1S_2S_3' + A_7.S_0'S_1S_2S_3 + A_8.S_0S_1'S_2'S_3' + A_9.S_0S_1'S_2'S_3 + A_{10}.S_0S_1'S_2S_3' + A_{11}.S_0S_1'S_2S_3 + A_{12}.S_0S_1S_2'S_3' + A_{13}.S_0S_1S_2'S_3 + A_{14}.S_0S_1S_2S_3' + A_{15}.S_0S_1S_2S_3$$

S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	A <sub>0</sub>	A <sub>1</sub>	A <sub>2</sub>	A <sub>3</sub>	A <sub>4</sub>	A <sub>5</sub>	A <sub>6</sub>	A <sub>7</sub>	A <sub>8</sub>	A <sub>9</sub>	A <sub>10</sub>	A <sub>11</sub>	A <sub>12</sub>	A <sub>13</sub>	A <sub>14</sub>	A <sub>15</sub>
0	0	0	0	A	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	A	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	A	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	A	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	A	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	A	0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	A	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	A	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	A	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	A	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	A	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	A	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	A	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	A	0	0
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	A	0
1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	A

$$A_0 = S_0'S_1'S_2'S_3'$$

$$A_1 = S_0'S_1'S_2'S_3$$

$$A_2 = S_0'S_1'S_2S_3'$$

$$A_3 = S_0'S_1'S_2S_3$$

$$A_4 = S_0'S_1S_2'S_3'$$

$$A_5 = S_0'S_1S_2'S_3$$

$$A_6 = S_0'S_1S_2S_3'$$

$$A_7 = S_0'S_1S_2S_3$$

$$A_8 = S_0S_1'S_2'S_3'$$

$$A_9 = S_0S_1'S_2'S_3$$

$$A_{10} = S_0S_1'S_2S_3'$$

$$A_{11} = S_0S_1'S_2S_3$$

$$A_{12} = S_0S_1S_2'S_3'$$

$$A_{13} = S_0S_1S_2'S_3$$

$$A_{14} = S_0S_1S_2S_3'$$



$$A_{15} = S_0S_1S_2S_3$$


**Multiplexer Theory**

The *multiplexer*, shortened to “MUX” or “MPX”, is a combinational logic circuit designed to switch one of several input lines through to a single common output line by the application of a control signal. Multiplexers operate like very fast acting multiple position rotary switches connecting or controlling multiple input lines called “channels” one at a time to the output.

**Demultiplexer Theory**

The *demultiplexer* takes one single input data line and then switches it to any one of several individual output lines one at a time. The demultiplexer converts a serial data signal at the input to a parallel data at its output lines as shown below.

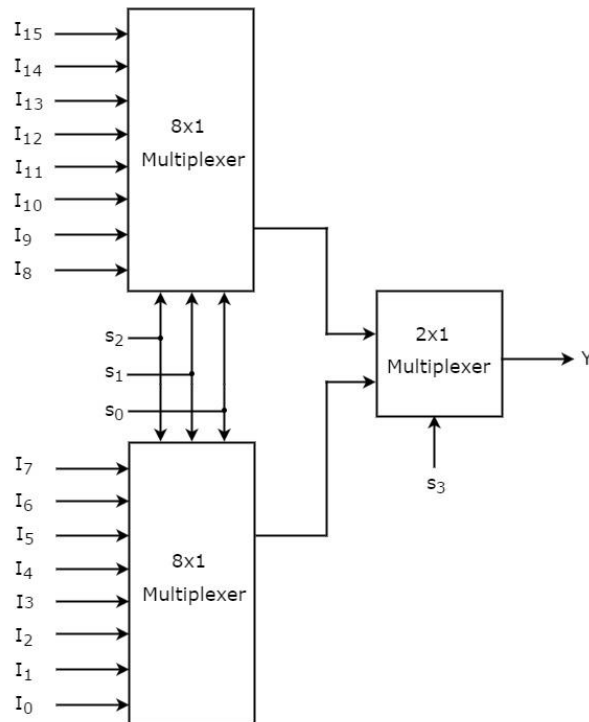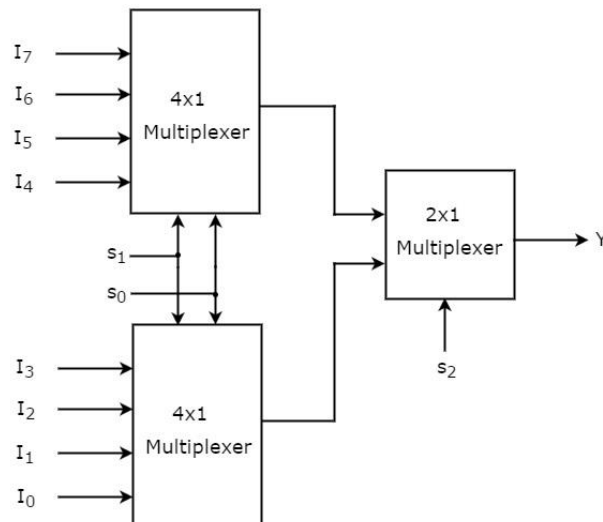**Block diagram/Circuit diagram for implementing 16:1 MUX using 8:1 MUX****Block diagram and Circuit diagram for implementing 8:1 MUX using 4:1 MUX**

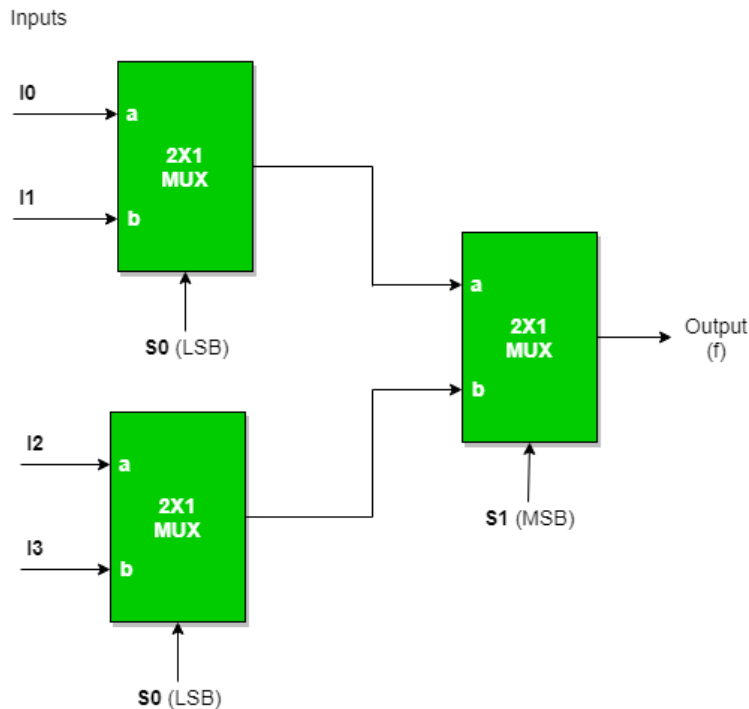**Block diagram and Circuit diagram for implementing 4:1 MUX using 2:1 MUX****SOP canonical expression of MUX and circuit implemented in MUX**

$$F = S_0'S_1'S_2'S_3' + S_0'S_1'S_2'S_3 + S_0'S_1'S_2S_3' + S_0'S_1'S_2S_3 + S_0'S_1S_2'S_3' + A_{11}.S_0S_1'S_2S_3 + A_{13}.S_0S_1S_2'S_3$$



$$F' = S_0'S_1S_2'S_3 + S_0'S_1S_2S_3' + S_0'S_1S_2S_3 + S_0S_1'S_2'S_3' + S_0S_1'S_2'S_3 + S_0S_1'S_2S_3' + S_0S_1S_2'S_3' + S_0S_1S_2S_3' + S_0S_1S_2S_3$$

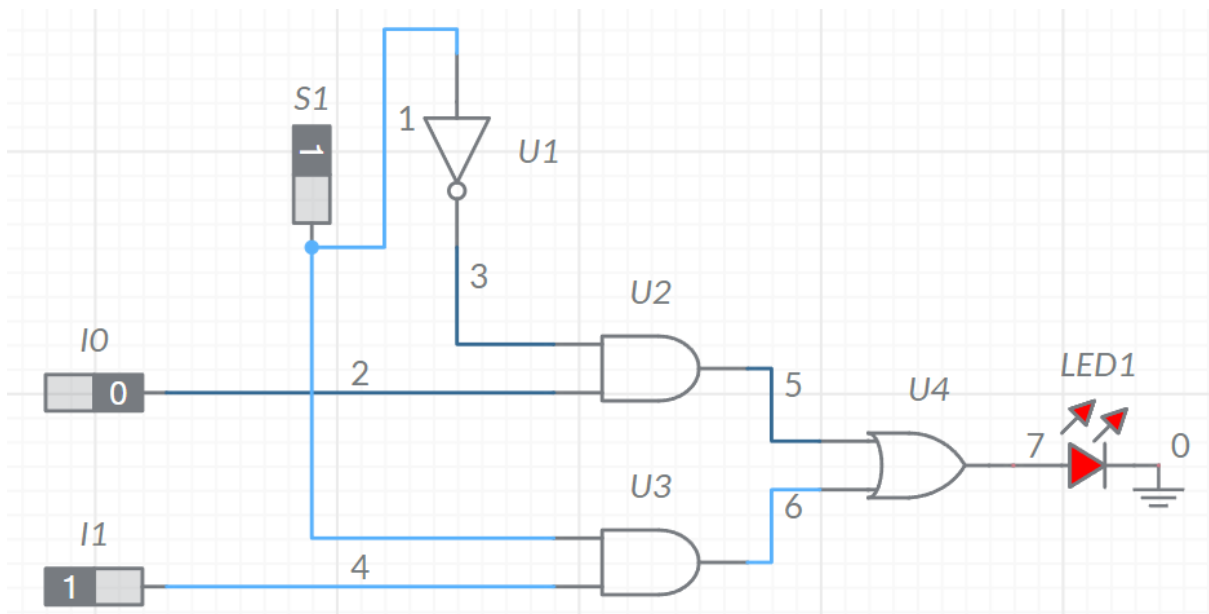
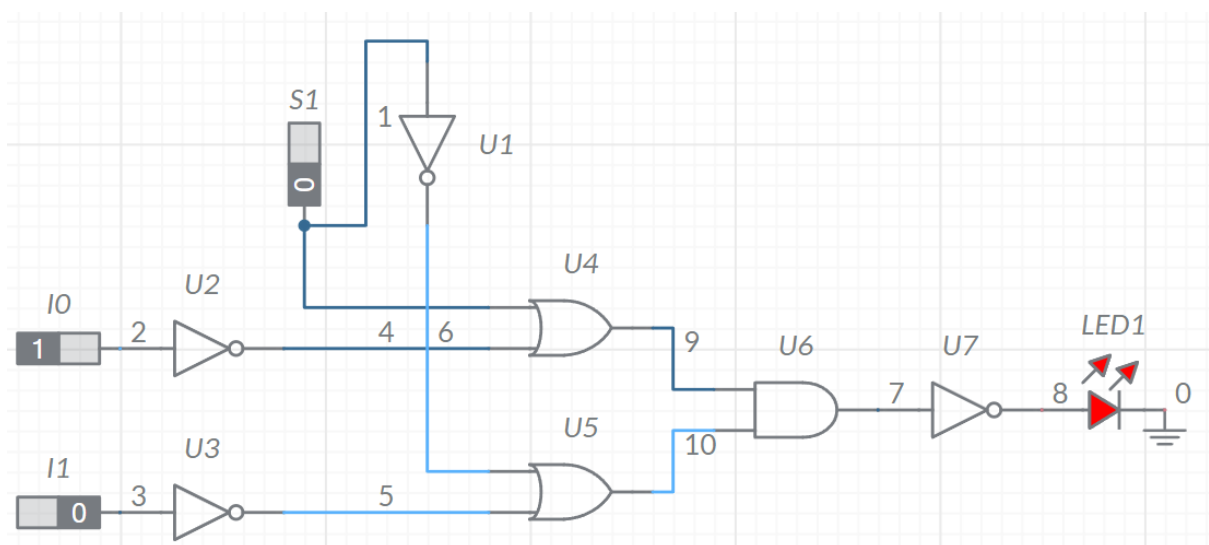
**POS canonical expression of MUX and circuit implemented in MUX**

$$F = (S_0+S_1+S_2+S_3) (S_0+S_1+S_2+S_3') (S_0+S_1+S_2'+S_3) (S_0+S_1+S_2'+S_3') (S_0+S_1'+S_2+S_3) (S_0'+S_1+S_2'+S_3') (S_0'+S_1'+S_2+S_3')$$

$$F' = (S_0+S_1'+S_2+S_3') (S_0+S_1'+S_2'+S_3) (S_0+S_1'+S_2'+S_3') (S_0'+S_1+S_2+S_3) (S_0'+S_1+S_2+S_3') (S_0'+S_1+S_2'+S_3) (S_0'+S_1'+S_2+S_3) (S_0'+S_1'+S_2'+S_3) (S_0'+S_1'+S_2'+S_3')$$



**Circuit diagram of 2:1 MUX Circuit using SOP Equation --- AOI circuit****Circuit diagram of 2:1 MUX Circuit using POS Equation --- OAI circuit**

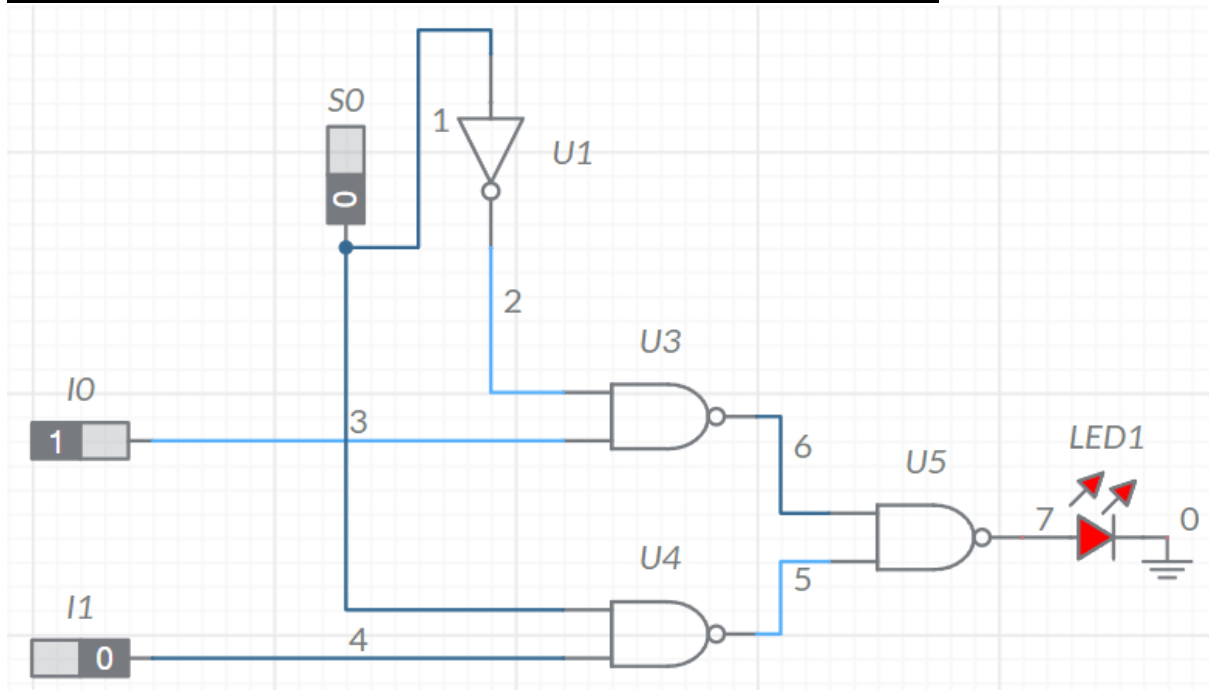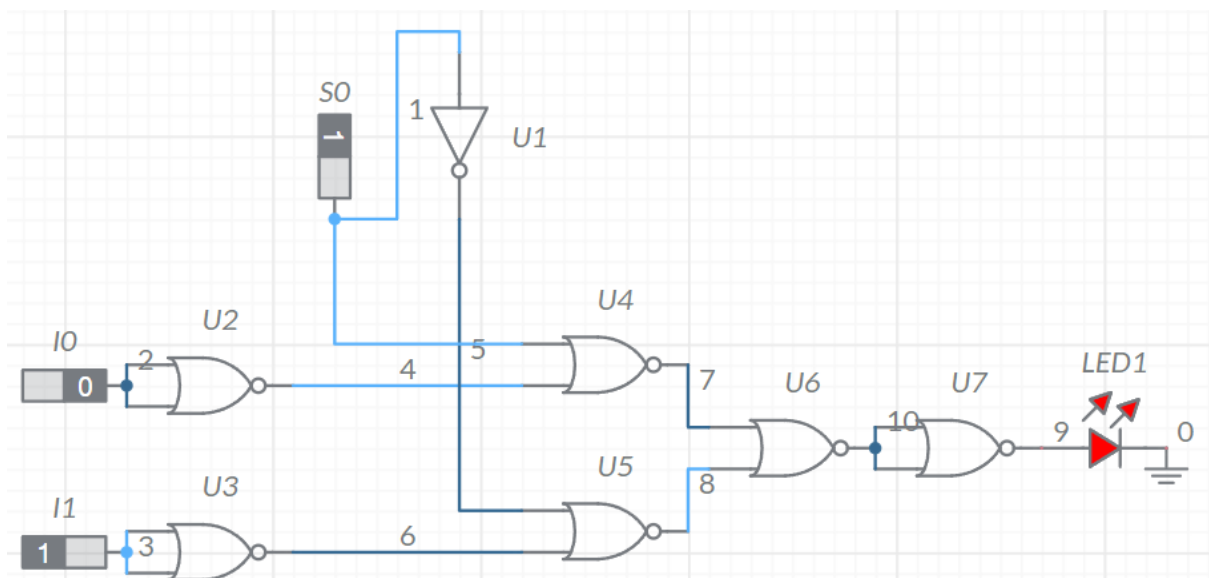**Circuit diagram of 2:1 MUX Circuit using SOP Equation --- NAND circuit****Circuit diagram of 2:1 MUX Circuit using POS Equation --- NOR circuit**

**Implementation steps for Task I and II using 4:1 Multiplexer**

	$C'D'$	$C'D$	$CD'$	$CD$
	$I_0$	$I_1$	$I_2$	$I_3$
$A'B'$	1	1	1	1
$A'B$	1	0	0	0
$AB'$	0	0	0	1
$AB$	0	1	0	0
F:	$A'$	$(A \wedge B)'$	$A'B'$	$B'$
$F'$ :	A	$A \wedge B$	$A+B$	B

F implementation:

$$I_0 = A'$$

$$I_1 = (A \wedge B)'$$

$$I_2 = A'B'$$

$$I_3 = B'$$

F' implementation:

$$I_0 = A$$

$$I_1 = A \wedge B$$

$$I_2 = A + B$$

$$I_3 = B$$

**Implementation steps for Task I and II using 8:1 Multiplexer**

	$B'C'D'$	$B'C'D$	$B'CD'$	$B'CD$	$BC'D'$	$BC'D$	$BCD'$	$BCD$
	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$A'$	1	1	1	1	1	0	0	0
A	0	0	0	1	0	1	0	0
F	$A'$	$A'$	$A'$	1	$A'$	A	0	0
$F'$	A	A	A	0	A	$A'$	1	1

F implementation:

$$I_0 = I_1 = I_2 = I_4 = A'$$

$$I_3 = 1$$

$$I_5 = A$$

$$I_6 = I_7 = 0$$

F' implementation:

$$I_0 = I_1 = I_2 = I_4 = A$$


$$I_3 = 0$$

$$I_5 = A'$$

$$I_6 = I_7 = 1$$

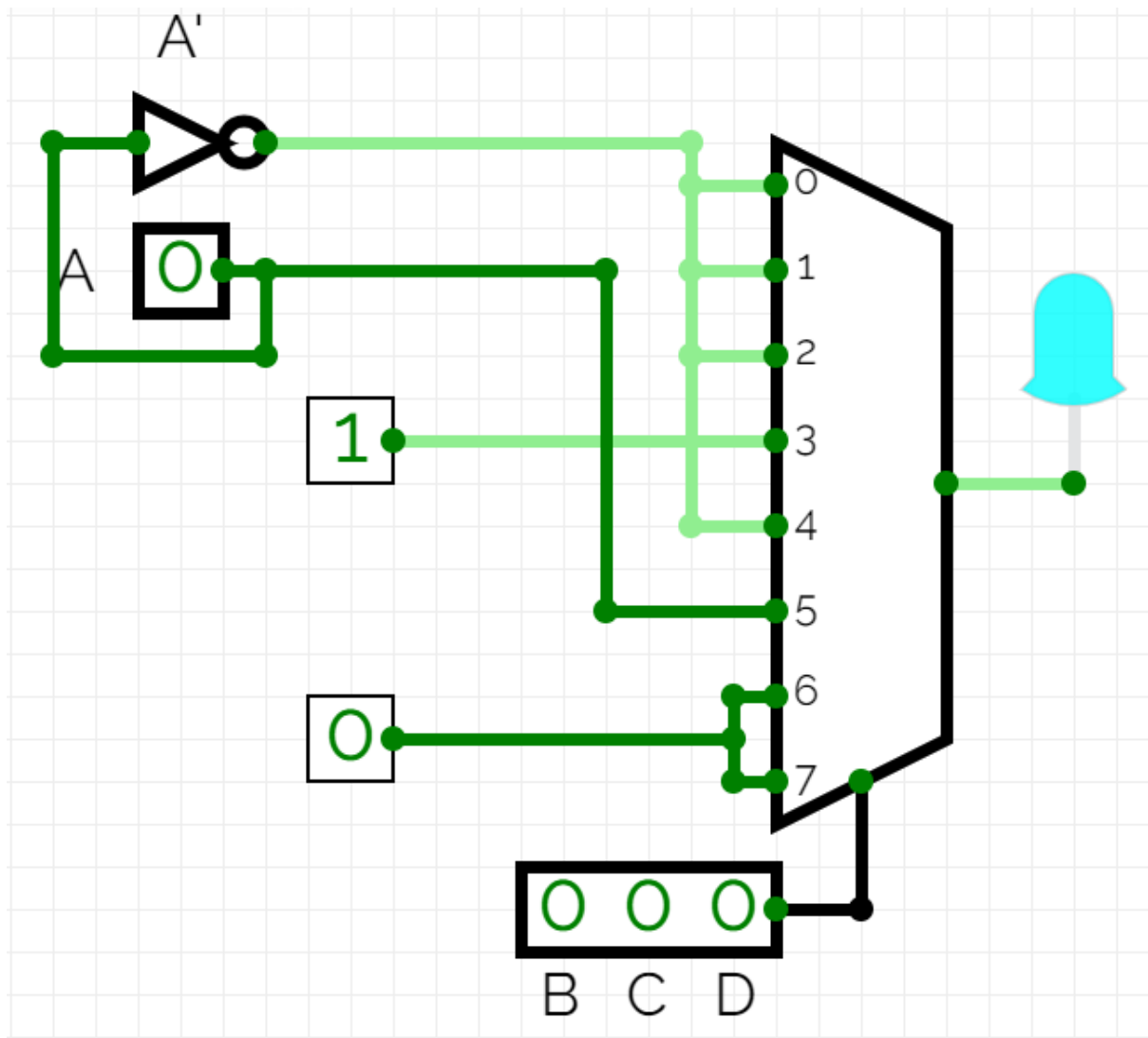
**Multisim live / Circuitverse.org Simulation link for Multiplexer based circuit implemented using 8:1 Multiplexer**

<https://circuitverse.org/simulator/21bds0340-8-1-regno-mux>



 **Multisim live / Circuitverse.org Simulation link for Multiplexer based circuit implemented using 4:1 Multiplexer**

<https://circuitverse.org/simulator/21bds0340-4-1-regno-mux>



### Verilog code: SL

```
module mux2to1(x, s, f);
    input [0:1]x;
    input s;
    output f;
    wire nots, prod1, prod2;
    not(nots, s);
    and(prod1, x[0], nots);
    and(prod2, x[1], s);
    or(f, prod1, prod2);
endmodule

module mux4to1(x, s, f);
    input [0:3]x;
    input [0:1]s;
    output f;
    wire [0:1]farr;
    mux2to1 tto1(x[0:1], s[1], farr[0]);
    mux2to1 tto2(x[2:3], s[1], farr[1]);
endmodule
```

```

    mux2to1 tto3(farr, s[0], f);
endmodule

module mux8to1(x, s, f);
    input [0:7]x;
    input [0:2]s;
    output f;
    wire [0:1]farr;
    mux4to1 fto1(x[0:3], s[1:2], farr[0]);
    mux4to1 fto2(x[4:7], s[1:2], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

module mux16to1(x, s, f);
    input [0:15]x;
    input [0:3]s;
    output f;
    wire [0:1]farr;
    mux8to1 eto1(x[0:7], s[1:3], farr[0]);
    mux8to1 eto2(x[8:15], s[1:3], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

```

### Verilog code: BL

```

module mux2to1(x, s, f);
    input [0:1]x;
    input s;
    output f;
    wire nots, prod1, prod2;
    always @(*);
    begin
        nots = ~s;
        prod1 = x[0] & nots;
        prod2 = x[1] & s;
        f = prod1 | prod2;
    end
endmodule

module mux4to1(x, s, f);
    input [0:3]x;
    input [0:1]s;
    output f;
    wire [0:1]farr;
    mux2to1 tto1(x[0:1], s[1], farr[0]);
    mux2to1 tto2(x[2:3], s[1], farr[1]);
    mux2to1 tto3(farr, s[0], f);
endmodule

```

```

endmodule

module mux8to1(x, s, f);
    input [0:7]x;
    input [0:2]s;
    output f;
    wire [0:1]farr;
    mux4to1 fto1(x[0:3], s[1:2], farr[0]);
    mux4to1 fto2(x[4:7], s[1:2], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

module mux16to1(x, s, f);
    input [0:15]x;
    input [0:3]s;
    output f;
    wire [0:1]farr;
    mux8to1 eto1(x[0:7], s[1:3], farr[0]);
    mux8to1 eto2(x[8:15], s[1:3], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

```

### **Verilog code: DFL**

```

module mux2to1(x, s, f);
    input [0:1]x;
    input s;
    output f;
    wire nots, prod1, prod2;
    assign nots = ~s;
    assign prod1 = x[0] & nots;
    assign prod2 = x[1] & s;
    assign f = prod1 | prod2;
endmodule

module mux4to1(x, s, f);
    input [0:3]x;
    input [0:1]s;
    output f;
    wire [0:1]farr;
    mux2to1 tto1(x[0:1], s[1], farr[0]);
    mux2to1 tto2(x[2:3], s[1], farr[1]);
    mux2to1 tto3(farr, s[0], f);
endmodule

module mux8to1(x, s, f);
    input [0:7]x;
    input [0:2]s;

```

```

    output f;
    wire [0:1]farr;
    mux4to1 fto1(x[0:3], s[1:2], farr[0]);
    mux4to1 fto2(x[4:7], s[1:2], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

module mux16to1(x, s, f);
    input [0:15]x;
    input [0:3]s;
    output f;
    wire [0:1]farr;
    mux8to1 eto1(x[0:7], s[1:3], farr[0]);
    mux8to1 eto2(x[8:15], s[1:3], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

```

### **Verilog code: Conditional Operator**

```

module mux2to1(x, s, f);
    input [0:1]x;
    input s;
    output f;
    assign f = s ? x[0] : x[1];
endmodule

module mux4to1(x, s, f);
    input [0:3]x;
    input [0:1]s;
    output f;
    wire [0:1]farr;
    mux2to1 tto1(x[0:1], s[1], farr[0]);
    mux2to1 tto2(x[2:3], s[1], farr[1]);
    mux2to1 tto3(farr, s[0], f);
endmodule

module mux8to1(x, s, f);
    input [0:7]x;
    input [0:2]s;
    output f;
    wire [0:1]farr;
    mux4to1 fto1(x[0:3], s[1:2], farr[0]);
    mux4to1 fto2(x[4:7], s[1:2], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

module mux16to1(x, s, f);
    input [0:15]x;
    input [0:3]s;

```



```

    output f;
    wire [0:1]farr;
    mux8to1 eto1(x[0:7], s[1:3], farr[0]);
    mux8to1 eto2(x[8:15], s[1:3], farr[1]);
    mux2to1 tto1(farr, s[0], f);
endmodule

```

### **Test Bench**

```

module testbench;
    reg [0:15]x;
    reg [0:3]s;
    wire f;
    mux16to1 sto1(x, s, f);
    initial begin
        x[0] = 1; x[1] = 1; x[2] = 1; x[3] = 1; x[4] = 1; x[5] = 0; x[6] = 0; x[7]
= 0; x[8] = 0; x[9] = 0; x[10] = 0; x[11] = 1; x[12] = 0; x[13] = 1; x[14] =
0; x[15] = 0;
        s[0] = 0; s[1] = 0; s[2] = 0; s[3] = 0;
        #100
        s[0] = 0; s[1] = 0; s[2] = 0; s[3] = 1;
        #100
        s[0] = 0; s[1] = 0; s[2] = 1; s[3] = 0;
        #100
        s[0] = 0; s[1] = 0; s[2] = 1; s[3] = 1;
        #100
        s[0] = 0; s[1] = 1; s[2] = 0; s[3] = 0;
        #100
        s[0] = 0; s[1] = 1; s[2] = 0; s[3] = 1;
        #100
        s[0] = 0; s[1] = 1; s[2] = 1; s[3] = 0;
        #100
        s[0] = 0; s[1] = 1; s[2] = 1; s[3] = 1;
        #100
        s[0] = 1; s[1] = 0; s[2] = 0; s[3] = 0;
        #100
        s[0] = 1; s[1] = 0; s[2] = 0; s[3] = 1;
        #100
        s[0] = 1; s[1] = 0; s[2] = 1; s[3] = 0;
        #100
        s[0] = 1; s[1] = 0; s[2] = 1; s[3] = 1;
        #100
        s[0] = 1; s[1] = 1; s[2] = 0; s[3] = 0;
        #100
        s[0] = 1; s[1] = 1; s[2] = 0; s[3] = 1;
        #100
        s[0] = 1; s[1] = 1; s[2] = 1; s[3] = 0;
        #100
        s[0] = 1; s[1] = 1; s[2] = 1; s[3] = 1;
    end


```

```

#100
s[0] = 0;
end
endmodule

```
 
### Snip of Output waveform with respective code



Note: To revert to EPWave opening in a new browser window, set that option on your user page.

### Online Verilog code Simulation links

<https://www.edaplayground.com/x/Mwqd>

### Result and Inference

The output of the function matches the digits in hexadecimal of my registration number.

## PART II - Demultiplexer / Decoder based Design

### Aim

Using Reg.no. formulate expressions in SOP and POS for F and F'. Implement the circuits using only

- Design 4 to 16 Decoder using 3 to 8 Decoder constructed using 2-4 Decoders.
- Give the internal circuit of 2 to 4 Decoder using SOP, POS, NAND, NOR logic design.
- Implement a Combinational logic circuit obtained from your registration number using Decoder.
- Write the Verilog code for 4:16,3:8 and 2:4 Decoders and Verify the results using the truth table and show the output waveform.
- Implement the Verilog code in ModelSim and verify the results using the truth table and show the output waveform.
- Show the steps and procedure for implementation in the tool used.

### Components Required

- AND, OR, NOT, NAND and NOR gates
- 5V voltage source
- Led indicator


### Tools Required


- Multisim simulator

### Procedure

- Decode registration number with a 4:16 decoder.

### Pin Diagram

 


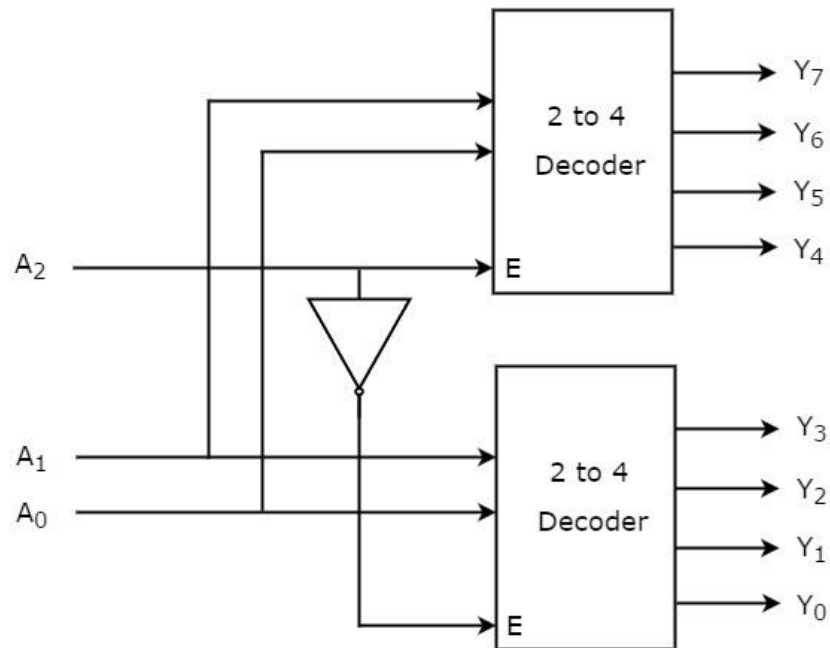
**Block diagram for implementing 3:8 Decoder using 2:4 Decoder****Decoder theory**



A decoder can take the form of a multiple-input, multiple-output logic circuit that converts coded inputs into coded outputs, where the input and output codes are different e.g. n-to- $2^n$ , binary-coded decimal decoders.


**Encoder and Priority Encoder Theory**

An Encoder is a combinational circuit that performs the reverse operation of decoder. It has maximum of  $2^n$  input lines and 'n' output lines, hence it encodes the information from  $2^n$  inputs into an n-bit code. It will produce a binary code equivalent to the input, which is active High. Therefore, the encoder encodes  $2^n$  input lines with 'n' bits.


A priority encoder is a circuit or algorithm that compresses multiple binary inputs into a smaller number of outputs. The output of a priority encoder is the binary representation of the index of the most significant activated line, starting from zero.

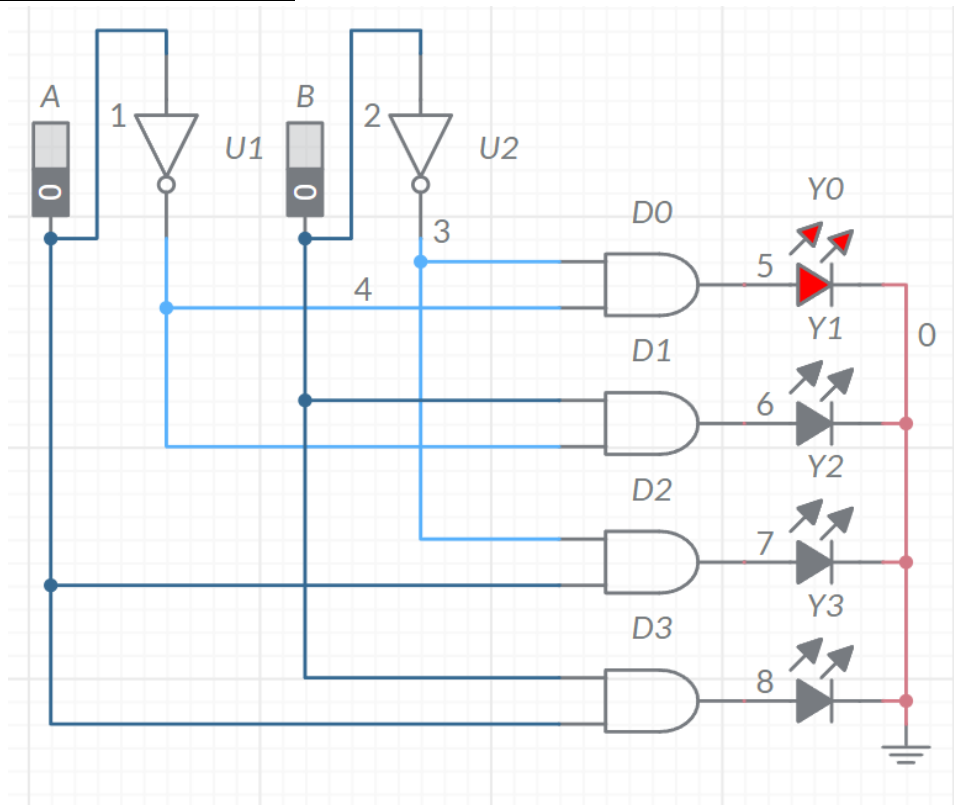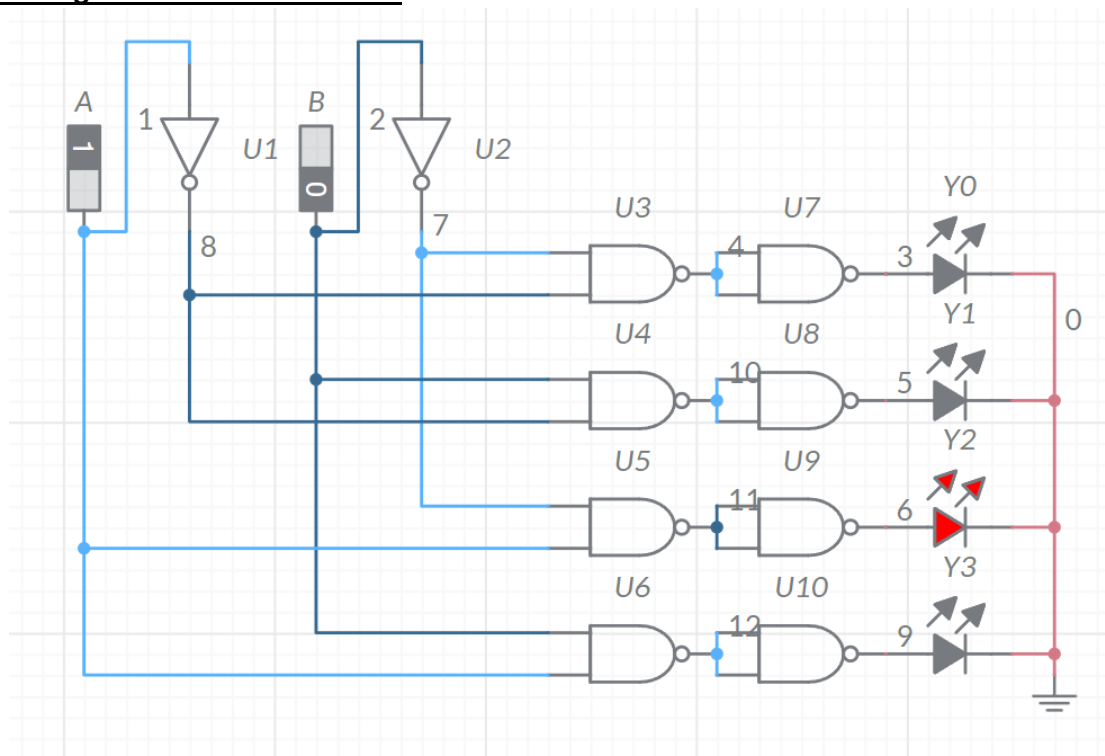**AOI logic circuit of 2:4 Decoder****NAND logic circuit of 2:4 Decoder**

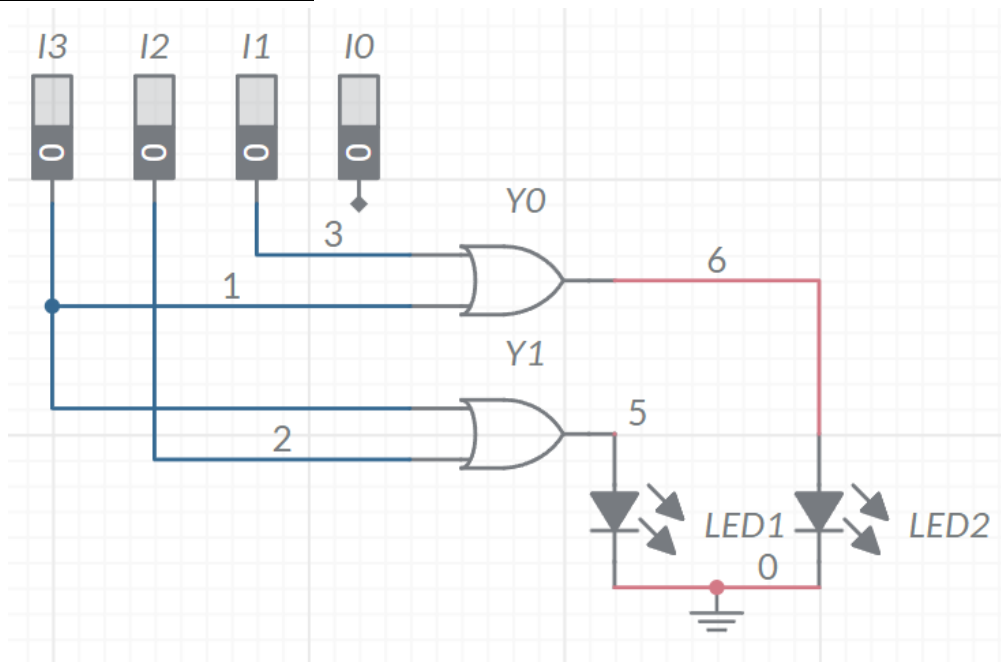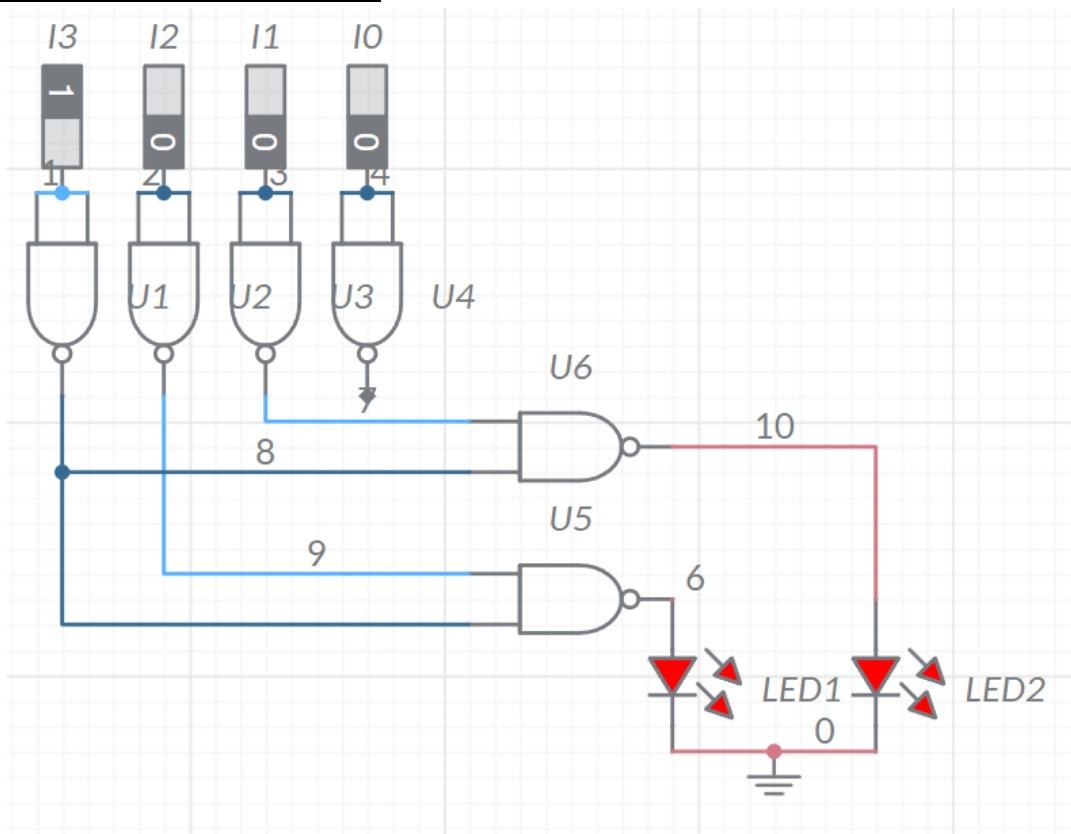**AOI logic circuit of 4:2 encoder****NAND logic circuit of 4:2 encoder**

 
Implementation steps for Task I using Decoder

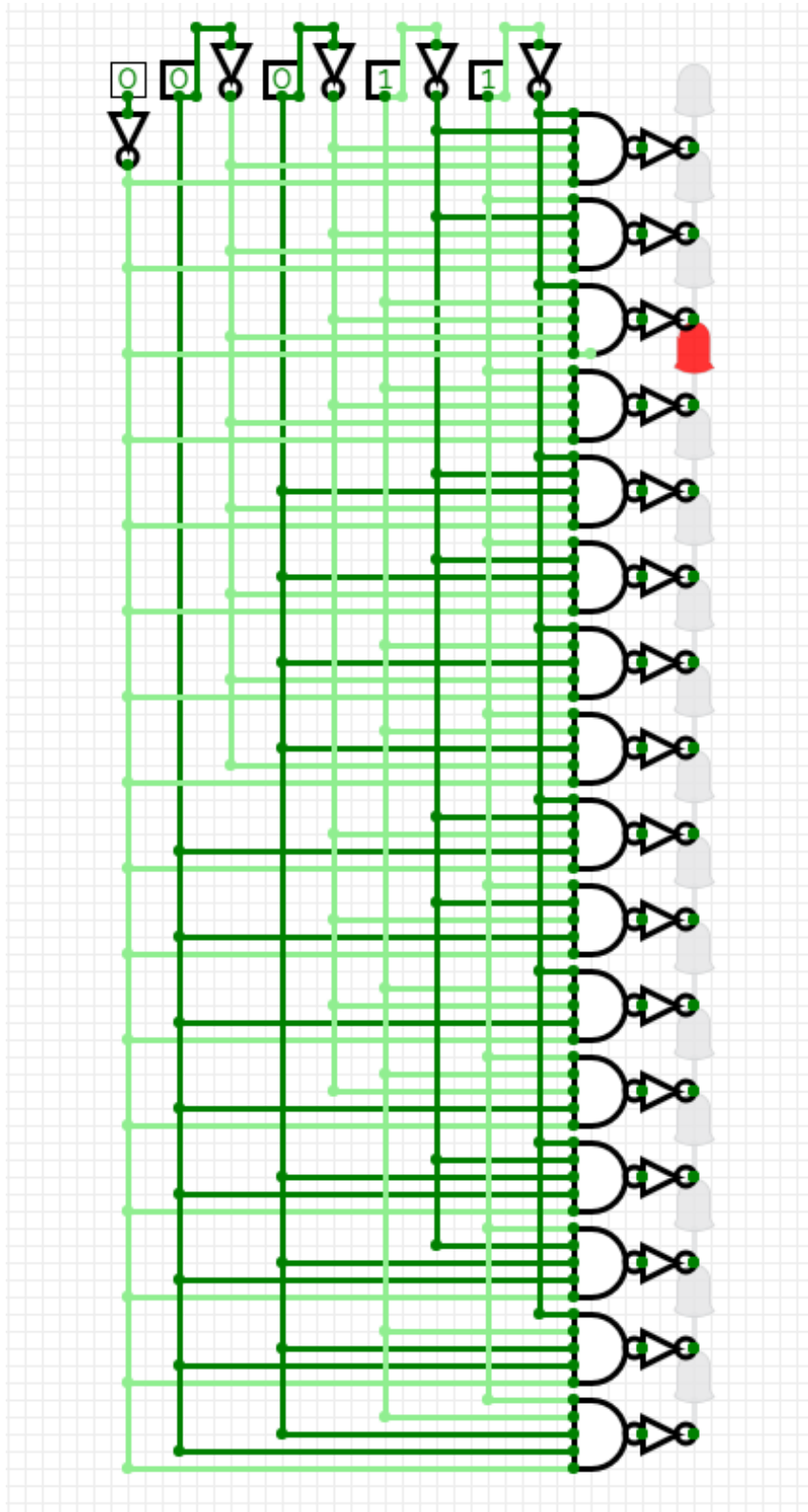**Proof of Task I (SOP) implemented using Decoder Active Low logic in simulator using snipping tool**





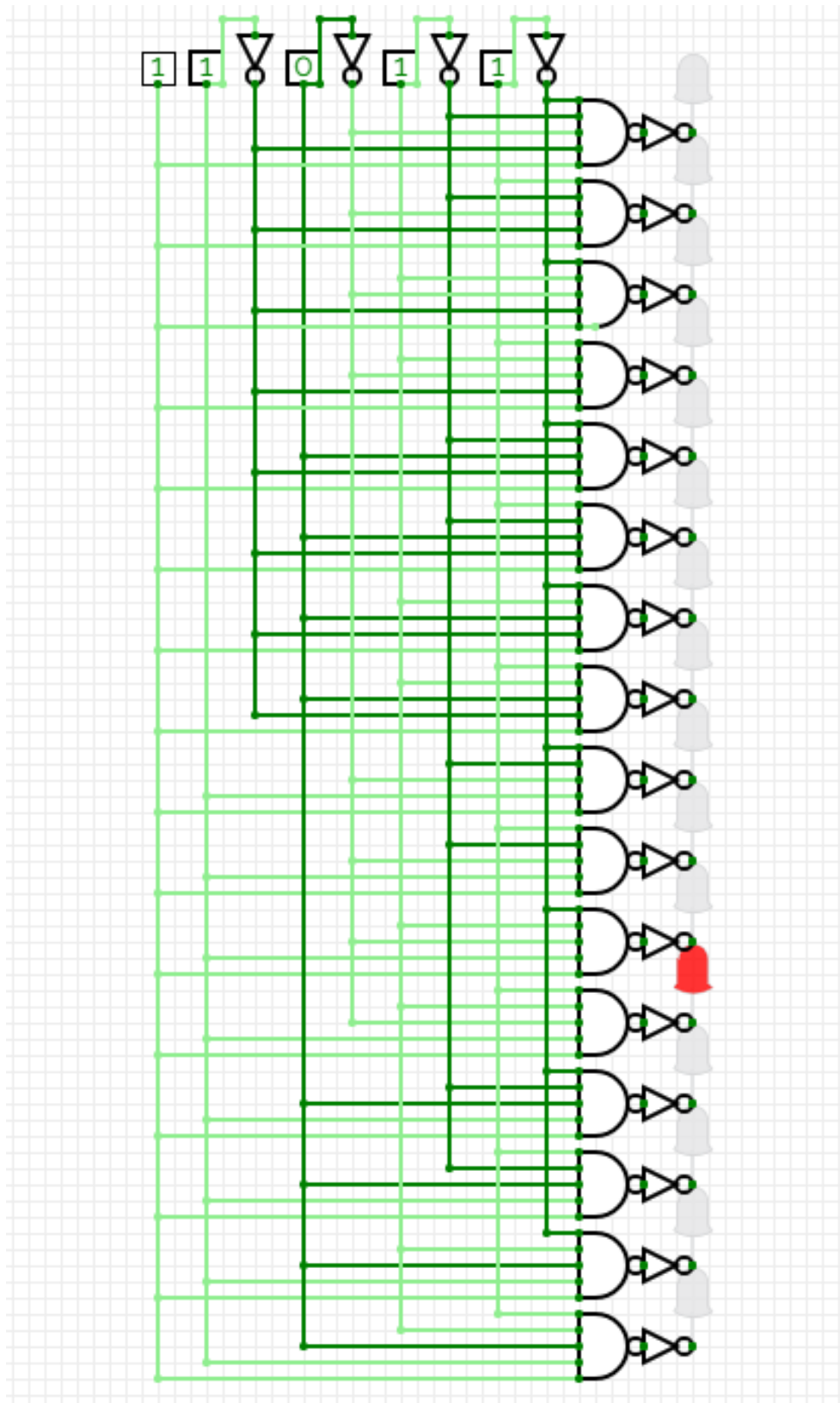**Proof of Task I (SOP) implemented using Decoder Active High logic in simulator using snipping tool**



**Verilog code for 2:4 Decoder (BL, DFL)**

```

module decoder2to4(e, x, f);
    input e;
    input [0:1]x;
    output [0:3]f;
    assign f[0] = ~(~e & ~x[0] & ~x[1]);
    assign f[1] = ~(~e & ~x[0] & x[1]);
    assign f[2] = ~(~e & x[0] & ~x[1]);
    assign f[3] = ~(~e & x[0] & x[1]);
endmodule

```

**Verilog code of 3:8 Decoder (BL, DFL)**

```

module decoder3to8(e, x, f);
    input e;
    input [0:2]x;
    output [0:7]f;
    assign f[0] = ~(~e & ~x[0] & ~x[1] & ~x[2]);
    assign f[1] = ~(~e & ~x[0] & ~x[1] & x[2]);
    assign f[2] = ~(~e & ~x[0] & x[1] & ~x[2]);
    assign f[3] = ~(~e & ~x[0] & x[1] & x[2]);
    assign f[4] = ~(~e & x[0] & ~x[1] & ~x[2]);
    assign f[5] = ~(~e & x[0] & ~x[1] & x[2]);
    assign f[6] = ~(~e & x[0] & x[1] & ~x[2]);
    assign f[7] = ~(~e & x[0] & x[1] & x[2]);
endmodule

```

**Verilog code for 2:4 and 3:8 Decoder (SL)**

```

module decoder2to4(e, x, f);
    input e;
    input [0:1]x;
    output [0:3]f;
    assign f[0] = ~(~e & ~x[0] & ~x[1]);
    assign f[1] = ~(~e & ~x[0] & x[1]);
    assign f[2] = ~(~e & x[0] & ~x[1]);
    assign f[3] = ~(~e & x[0] & x[1]);
endmodule

module decoder3to8(e, x, f);
    input e;
    input [0:2]x;
    output [0:7]f;
    decoder2to4 d2t41(x[0], x[1:2], f[0:3]);
    decoder2to4 d2t42(~x[0], x[1:2], f[4:7]);
endmodule


```

**Verilog Test Bench of Decoder**

```

module testdecoder;
    reg e;
    reg [0:2]x;
    wire [0:7]f;
    decoder3to8 d1(e, x, f);
    initial begin
        e = 0;
        x = 3'b000;
        #100
        x = 3'b001;
        #100
        x = 3'b010;
        #100
        x = 3'b011;
        #100
        x = 3'b100;
        #100
        x = 3'b101;
        #100
        x = 3'b110;
        #100
        x = 3'b111;
        #100
        x = 2'b00;
    end
endmodule

```

 **Snip of Verilog code output with links**

Note: To revert to EPWave opening in a new browser window, set that option on your user page.

[https://www.edaplayground.com/x/kG\\_r](https://www.edaplayground.com/x/kG_r)

**Result and Inference**

The circuit above has been created to decode any input with an active low input enabled.