

21BDS0340

Abhinav Dinesh Srivatsa

Electronics Lab

Task 2


Exercise No.: 1

Date: 10/03/22

Half wave and Full wave rectifier

Half Wave Rectifier

Circuit Diagram

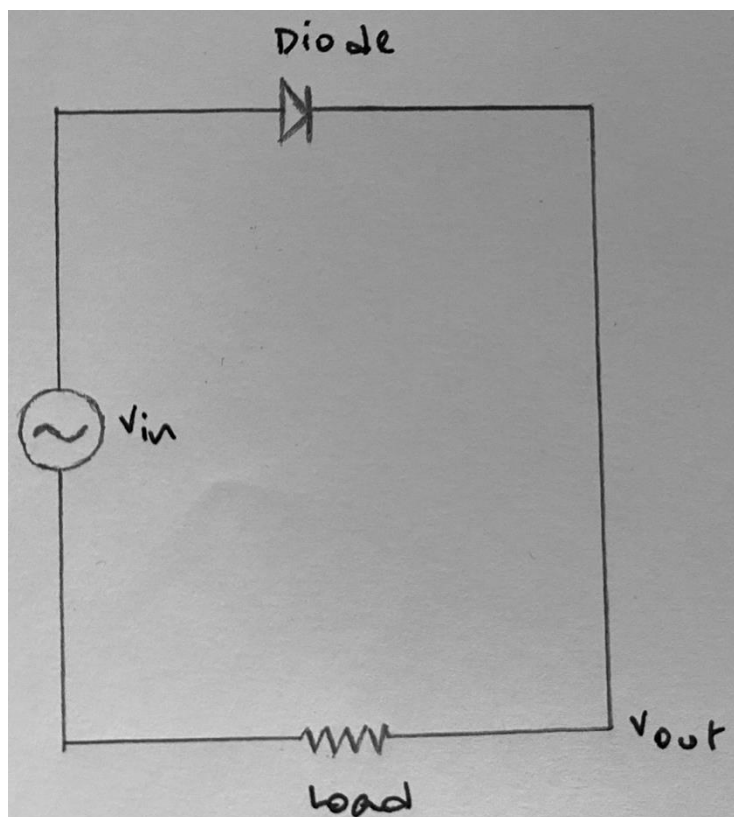


Components Required

Basic – Resistors


Sources – Power Sources – AC_Power, Ground

Simulate – Instruments – Oscilloscope

Simulated Circuit Diagram

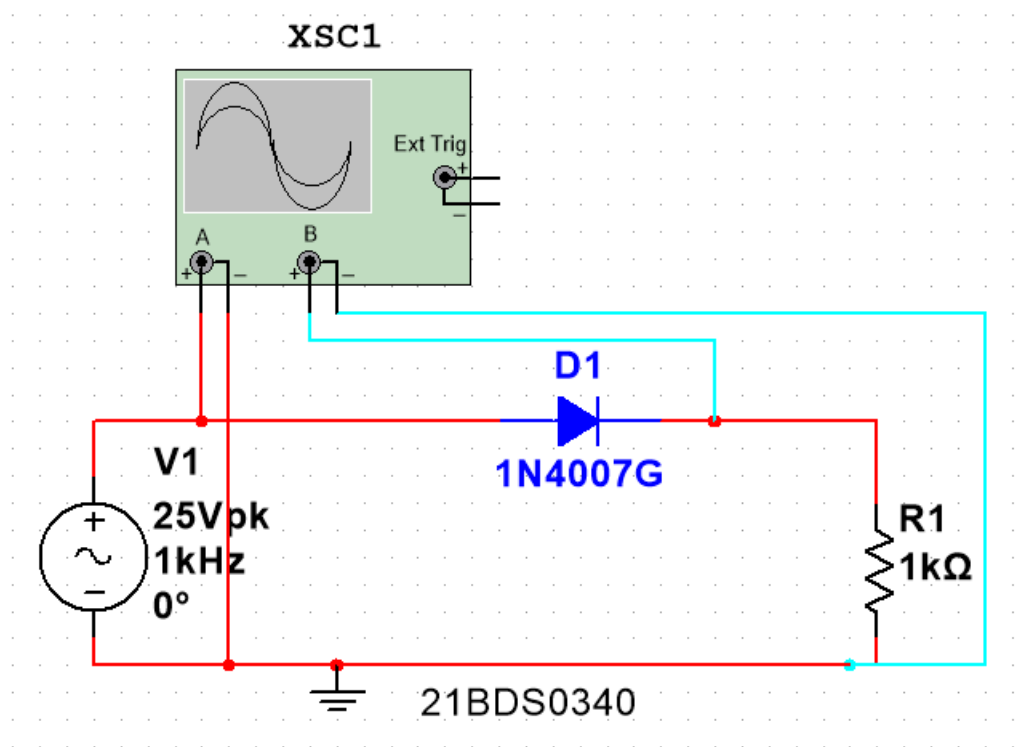

Simulation Output

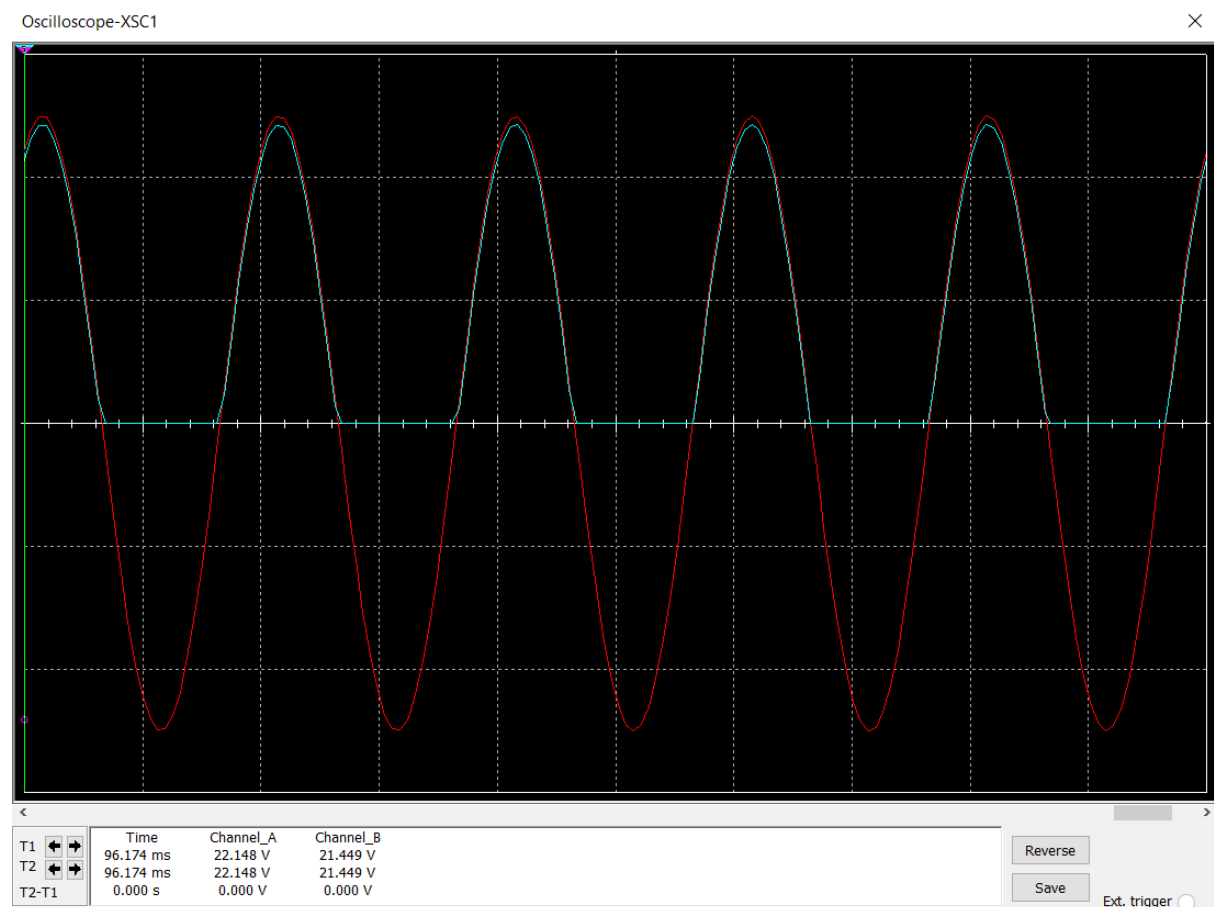

Calculations

$$\text{RMS voltage } V_{rms} = \frac{V_m}{2} = \frac{24.253 \text{ V}}{2} \\ = \underline{12.126 \text{ V}}$$

$$\text{DC / Average voltage } V_{dc} = \frac{V_m}{\pi} = \underline{7.72 \text{ V}}$$

$$\text{Ripple factor } r = \left(\left(\frac{V_{rms}}{V_{dc}} \right)^2 - 1 \right)^{1/2} = \underline{1.21}$$

$$\text{Efficiency } \eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc}^2}{V_{ac}^2} = \frac{V_{dc}^2}{V_{rms}^2} = \frac{4}{\pi^2} = \underline{40.6\%}$$


$$\text{Form factor } F.F = \frac{V_{rms}}{V_{dc}} = \frac{\pi}{2} = \underline{1.57}$$

$$\text{Peak factor } P.F = \frac{V_m}{V_{rms}} = \underline{2}$$

S. No.	Parameter	Value
1	Peak voltage (V_m)	24.25 V
2	RMS voltage (V_{rms})	12.13 V
3	DC voltage (V_{dc})	7.72 V
4	Ripple factor (r)	1.21
5	Efficiency (η)	40.6%
6	Form Factor (F.F.)	1.57
7	Peak Factor (P.F.)	2

Half Wave Rectifier (With Smoothing Capacitor)

Circuit Diagram

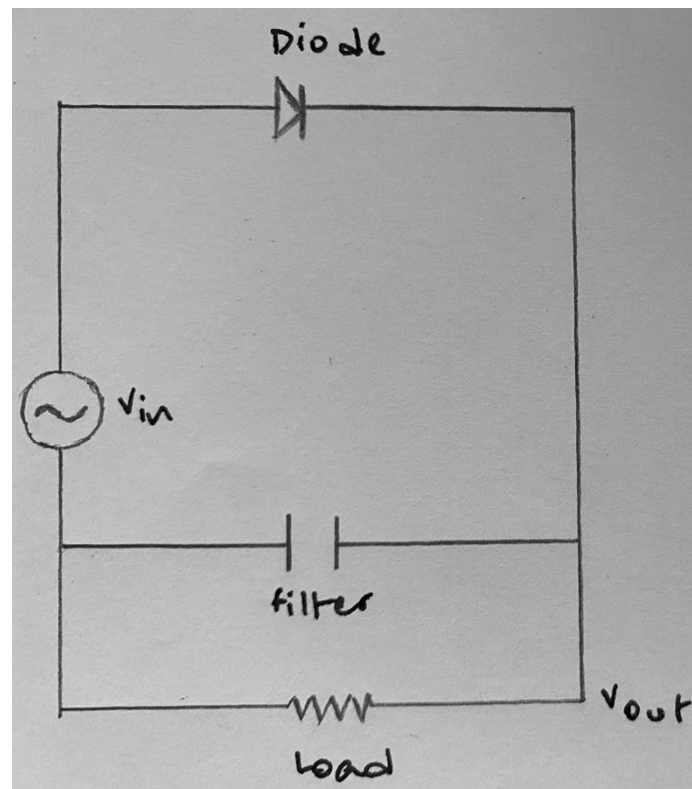


Components Required

Basic – Resistors, Capacitors


Sources – Power Sources – AC_Power, Ground

Simulate – Instruments – Oscilloscope

Simulated Circuit Diagram

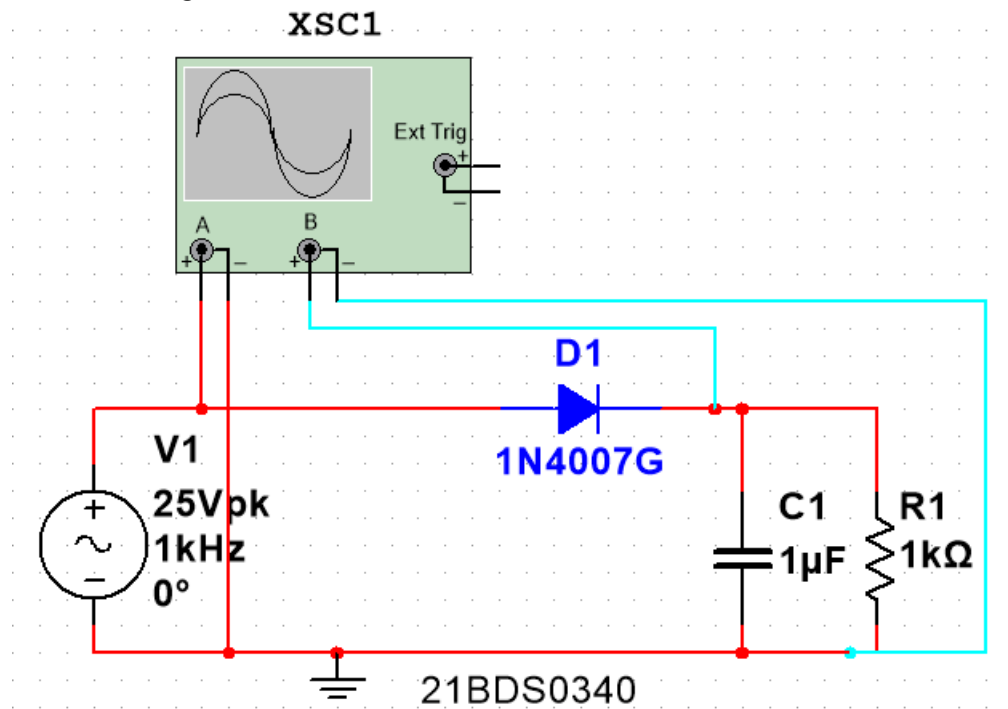

Simulation Output

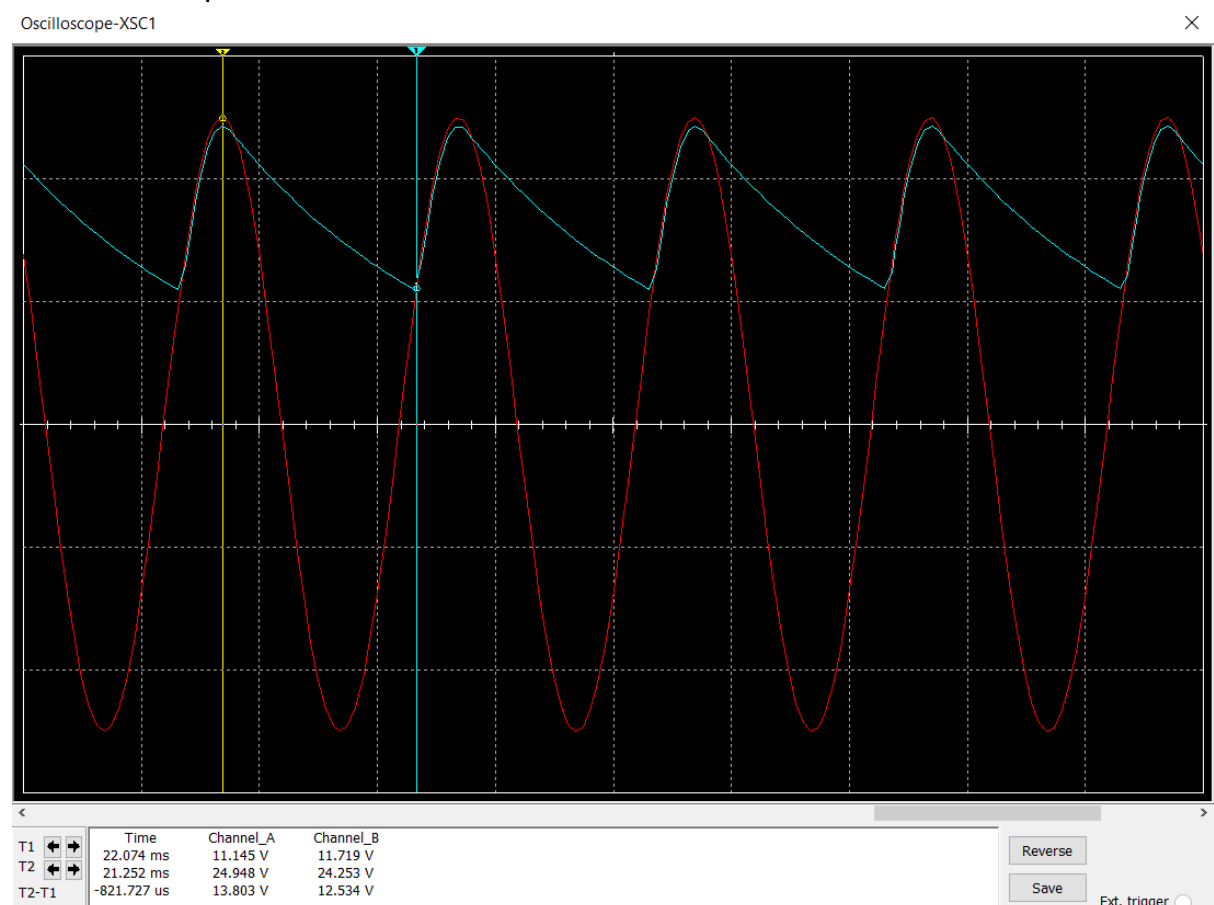

Calculations

$$V_{r,rms} = \frac{V_{rpp}}{2\sqrt{3}} = \frac{12.534}{2\sqrt{3}} \\ = \underline{3.62 \text{ V}}$$

$$\text{DC voltage } V_{dc} = V_m - \frac{V_{rpp}}{2} \\ = \underline{17.99 \text{ V}}$$


$$\text{Ripple Factor } r = \frac{V_{r,rms}}{V_{dc}} \\ = \underline{0.201}$$

$$\text{Also } r = \frac{1}{2\sqrt{3} f R_L C}$$

S. NO.	Parameter	Value
1	RMS voltage $V_{r,rms}$	3.62 V
2	DC voltage V_{dc}	17.99 V
3	Ripple factor r	0.201

Full Wave Rectifier

Circuit Diagram

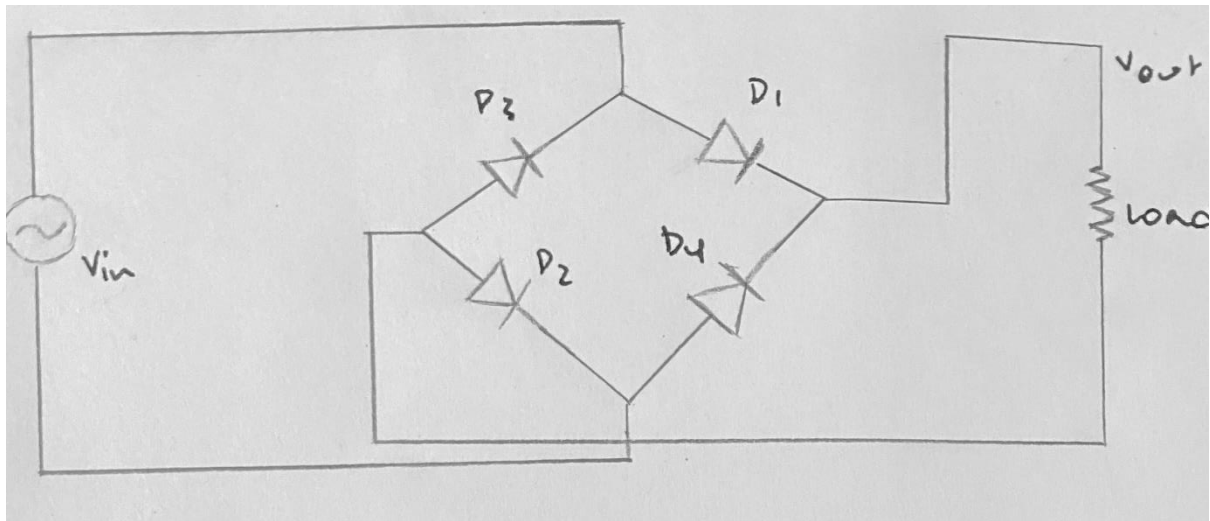


Components Required

Basic – Resistors


Sources – Power Sources – AC_Power, Ground

Simulate – Instruments – Oscilloscope

Simulated Circuit Diagram

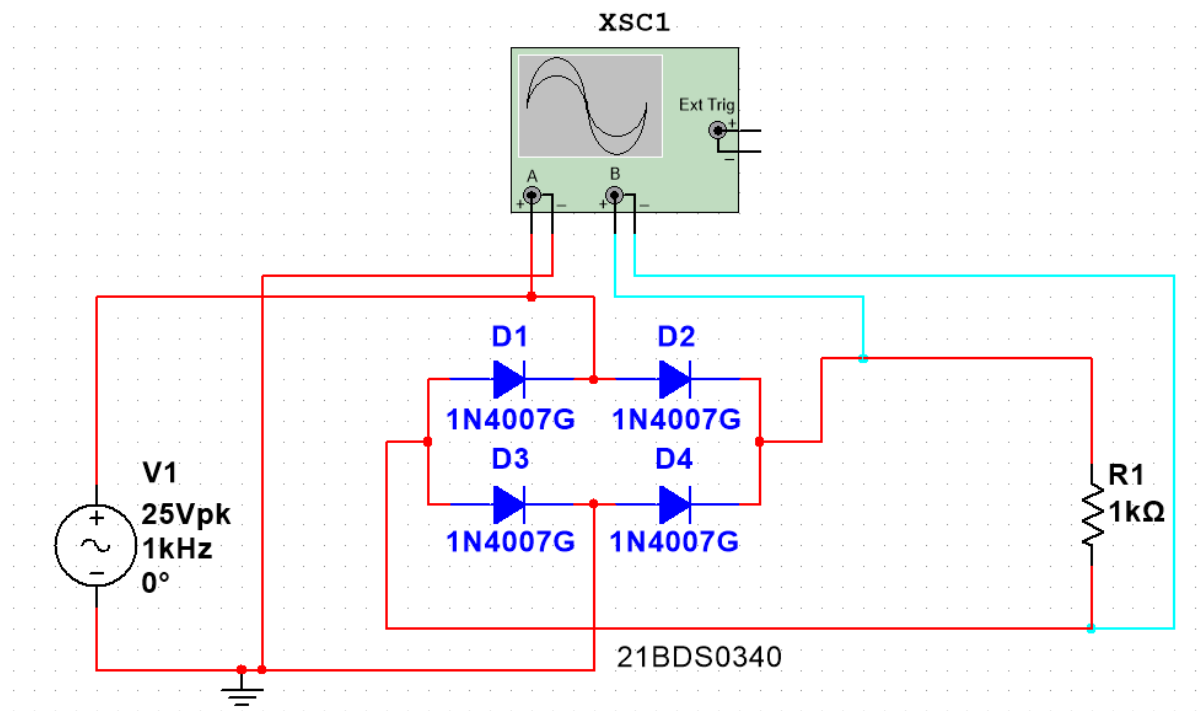

Simulation Output

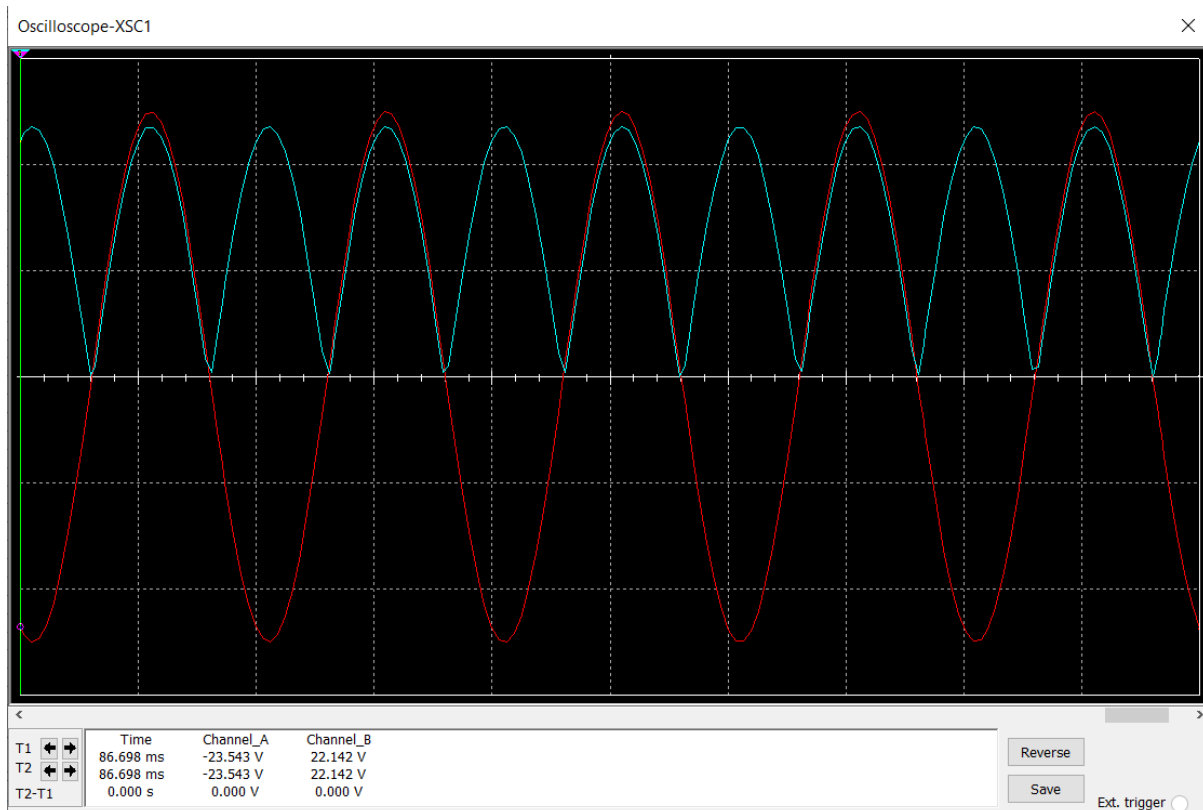

Calculations

$$\begin{aligned}\text{RMS voltage } V_{\text{rms}} &= \frac{V_m}{\sqrt{2}} \\ &= \underline{16.62 \text{ V}}\end{aligned}$$

$$\begin{aligned}\text{DC/Average voltage } V_{\text{dc}} &= \frac{2V_m}{\pi} \\ &= \underline{14.97 \text{ V}}\end{aligned}$$

$$\begin{aligned}\text{Ripple Factor } r &= \left(\left(\frac{V_{\text{rms}}}{V_{\text{dc}}} \right)^2 - 1 \right)^{1/2} \\ &= \underline{0.482}\end{aligned}$$

$$\text{Efficiency } \eta = \frac{4}{\pi^2} = \underline{81.2\%}$$


$$\text{Form Factor} = \frac{V_{\text{rms}}}{V_{\text{dc}}} = \frac{\pi}{2\sqrt{2}} = \underline{1.11}$$

$$\text{Peak Factor} = \frac{V_m}{V_{\text{rms}}} = \underline{\sqrt{2}}$$

S. No.	Parameter	Value
1	V_m	23.51 V
2	RMS voltage V_{rms}	16.62 V
3	DC voltage V_{dc}	14.97 V
4	Ripple Factor r	0.482
5	Efficiency η	81.2%
6	Form Factor	1.11
7	Peak Factor	$\sqrt{2}$

Full Wave Rectifier (With Smoothing Capacitor)

Circuit Diagram

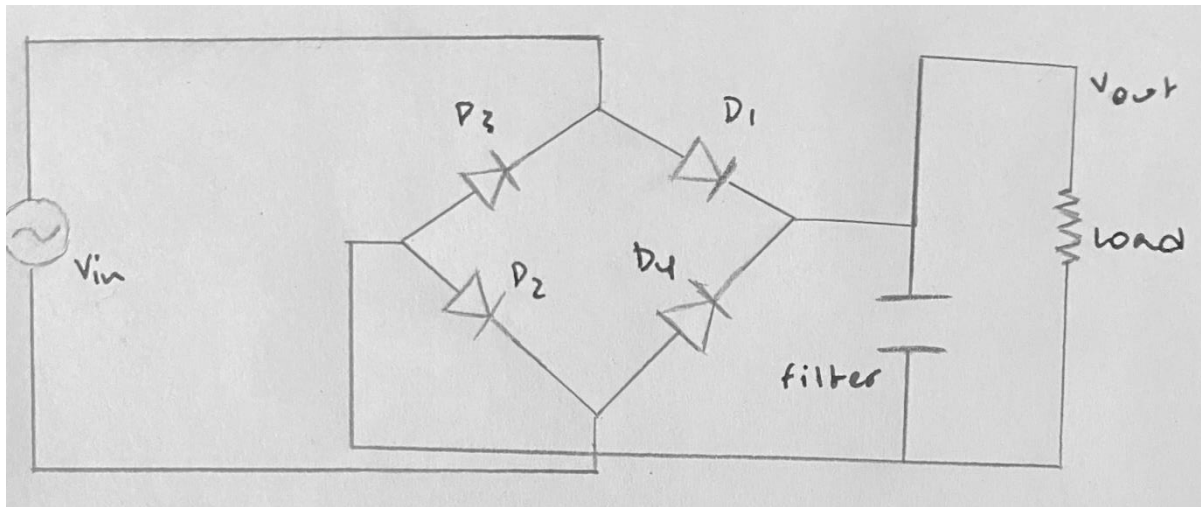


Components Required

Basic – Resistors, Capacitors


Sources – Power Sources – AC_Power, Ground

Simulate – Instruments – Oscilloscope

Simulated Circuit Diagram

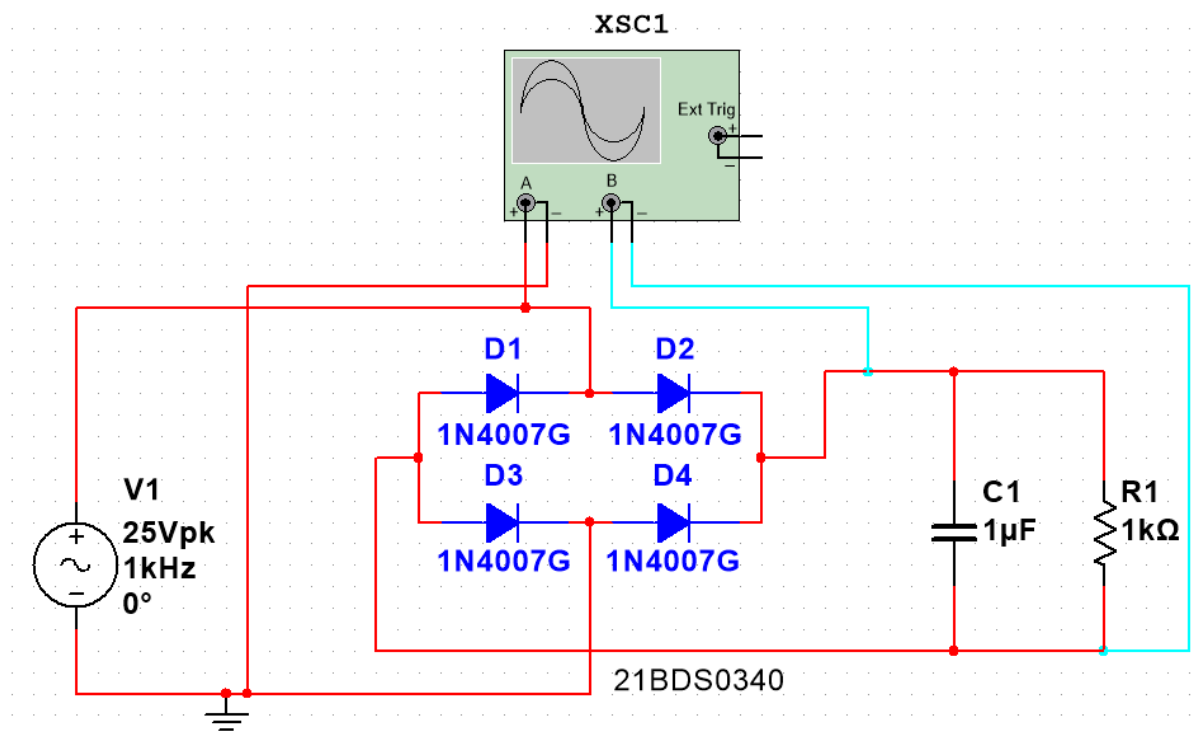

Simulation Output

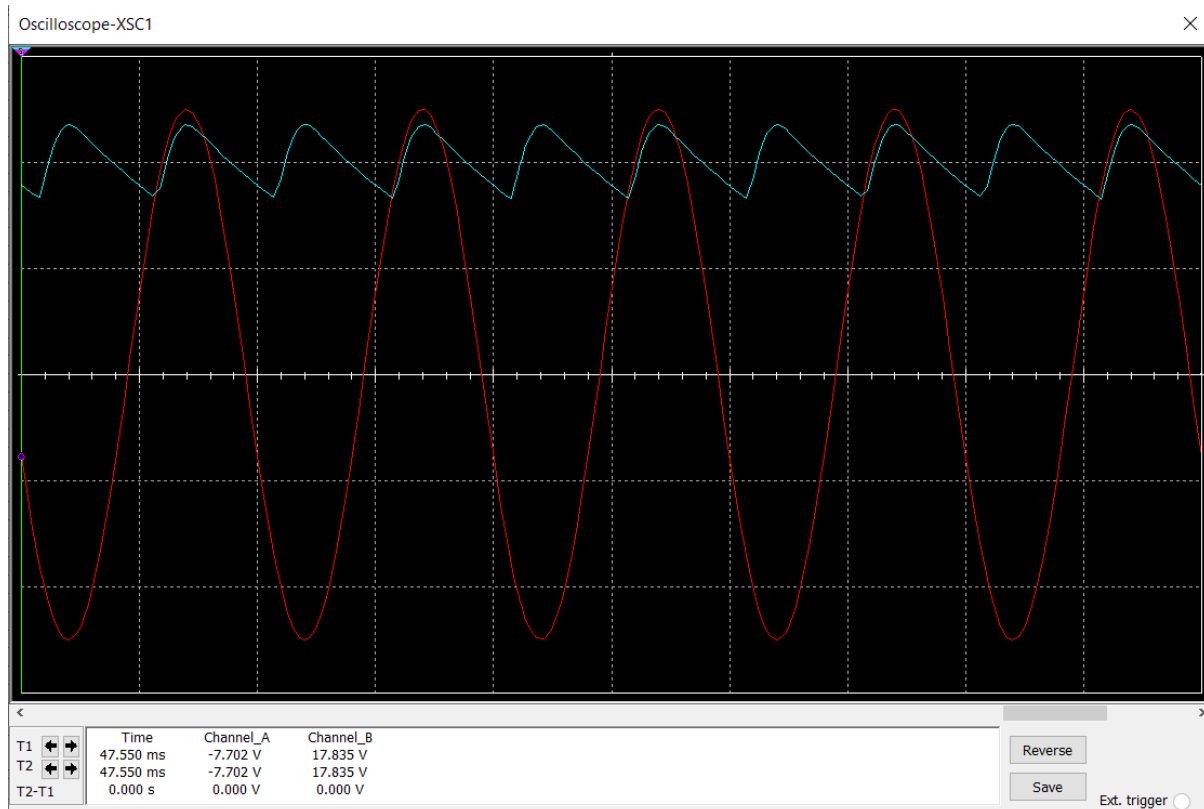

Calculations

$$\begin{aligned}\text{RMS voltage } V_{r,rms} &= \frac{V_{rpp}}{\sqrt{3}} \\ &= \underline{2.01 \text{ V}}\end{aligned}$$

$$\begin{aligned}\text{DC voltage } V_{dc} &= V_m - \left(\frac{V_{rpp}}{2} \right) \\ &= \underline{20.03 \text{ V}}\end{aligned}$$

$$\begin{aligned}\text{Ripple Factor } r &= \frac{V_{r,rms}}{V_{dc}} \\ &= \underline{0.1}\end{aligned}$$

S. No.	Parameter	Value
1	RMS voltage $V_{r,rms}$	2.01 V
2	DC voltage V_{dc}	20.03 V
3	Ripple Factor r	0.1

Verification Message




Exercise No.: 2

Date: 17/03/22

Zener Diode as a Voltage Regulator

Line Regulation

Circuit Diagram

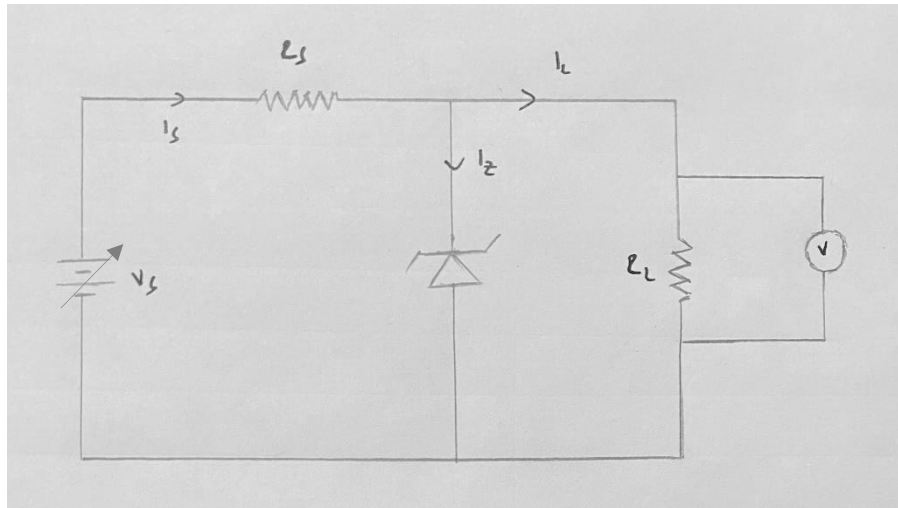

Components Required


Basic – Resistors

Sources – Power Sources – Variable DC Power, Ground

Diodes – Zener – 1N4733A

Toolbars – Measurement Components – Ammeter, Voltmeter

Simulated Circuit Diagram

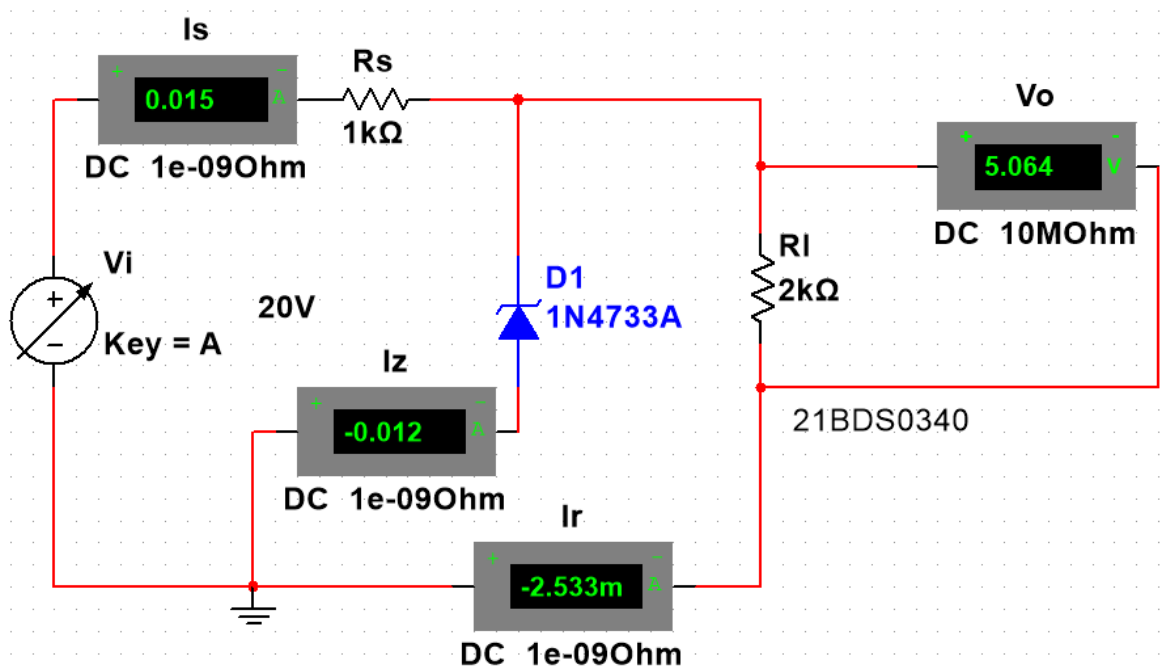

Calculations

In line regulation, load resistance is constant and input voltage varies. V_s must be sufficiently large to turn the Zener diode on.

$$V_L = V_Z = \frac{V_{\min} \times R_L}{(R_S + R_L)}$$

So, the minimum turn-on voltage V_{\min} is:

$$V_{\min} = \frac{V_Z \cdot (R_S + R_L)}{R_L}$$

Taking:

$$V_Z = 5.1 \text{ V}$$


$$R_S = 1000 \text{ ohm}$$

$$R_L = 2000 \text{ ohm}$$

$$\therefore V_{\min} = \frac{5.1 \times 3000}{2000}$$


$$= \underline{7.65 \text{ V}}$$

Graph

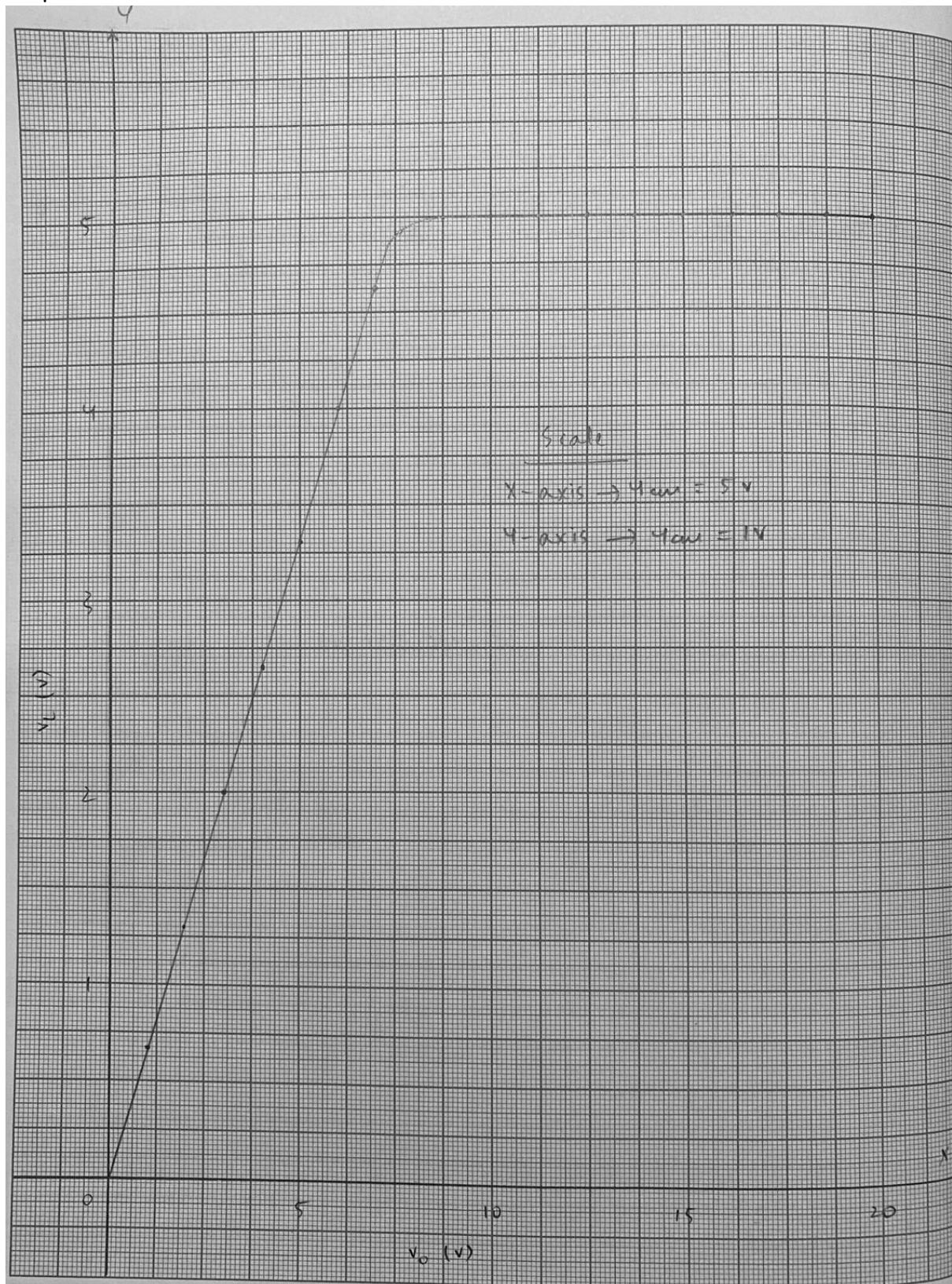

Load Regulation

Circuit Diagram

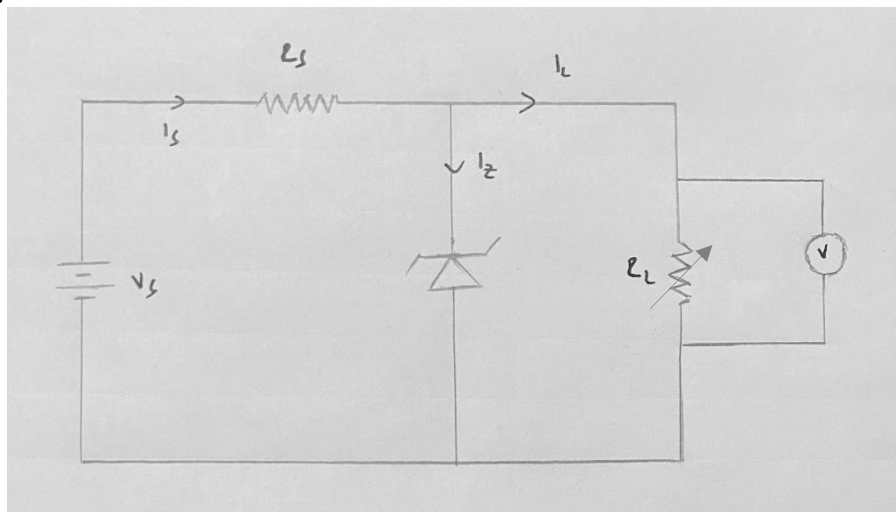

Components Required


Basic – Resistor, Variable Resistor

Sources – Power Sources –DC Power, Ground

Diodes – Zener – 1N4733A

Toolbars – Measurement Components – Ammeter, Voltmeter

Simulated Circuit Diagram

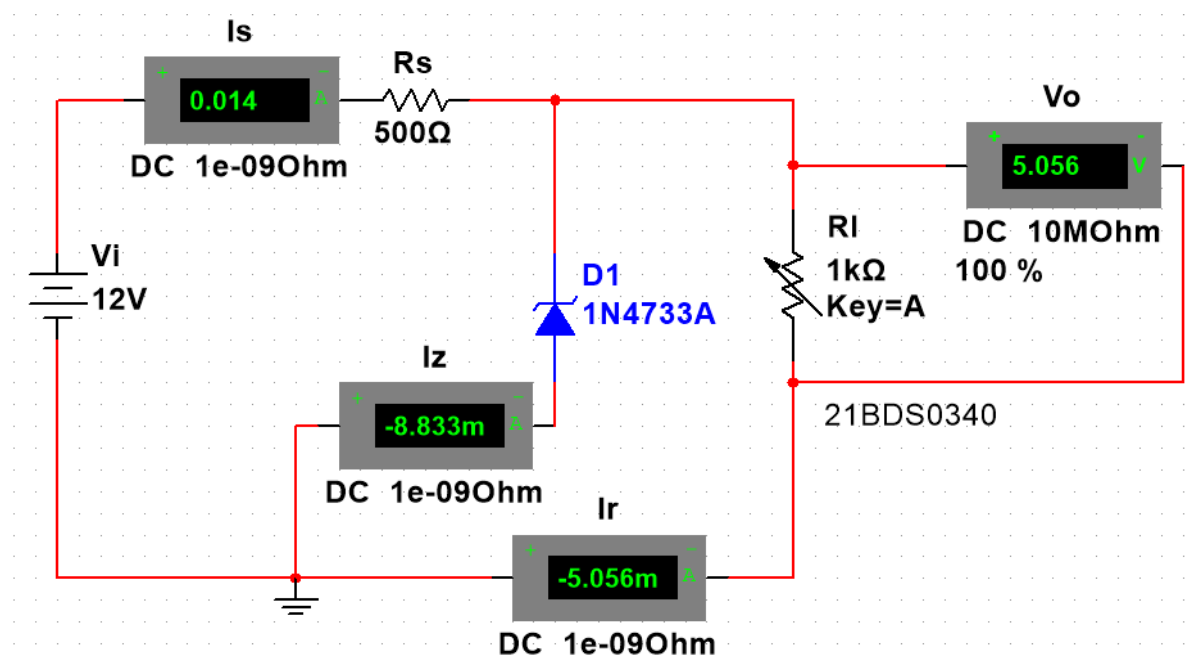

Calculations

In load regulation, input voltage is constant and load resistance varies. Too small a load, will result in making the zener diode off.

$$V_L = V_Z = \frac{V_1 \times R_{Lmin}}{(R_S + R_{Lmin})}$$

So the minimum load resistance R_L :

$$R_{Lmin} = \frac{V_Z \times R_S}{V_1 - V_Z}$$

Taking:


$$V_Z = 5.1 \text{ V}$$

$$R_S = 500 \text{ ohm}$$

$$V_1 = 12 \text{ V}$$

$$\begin{aligned} \therefore R_{Lmin} &= \frac{5.1 \times 500}{12 - 5.1} \\ &= \underline{369.57 \text{ ohm}} \end{aligned}$$

Graph

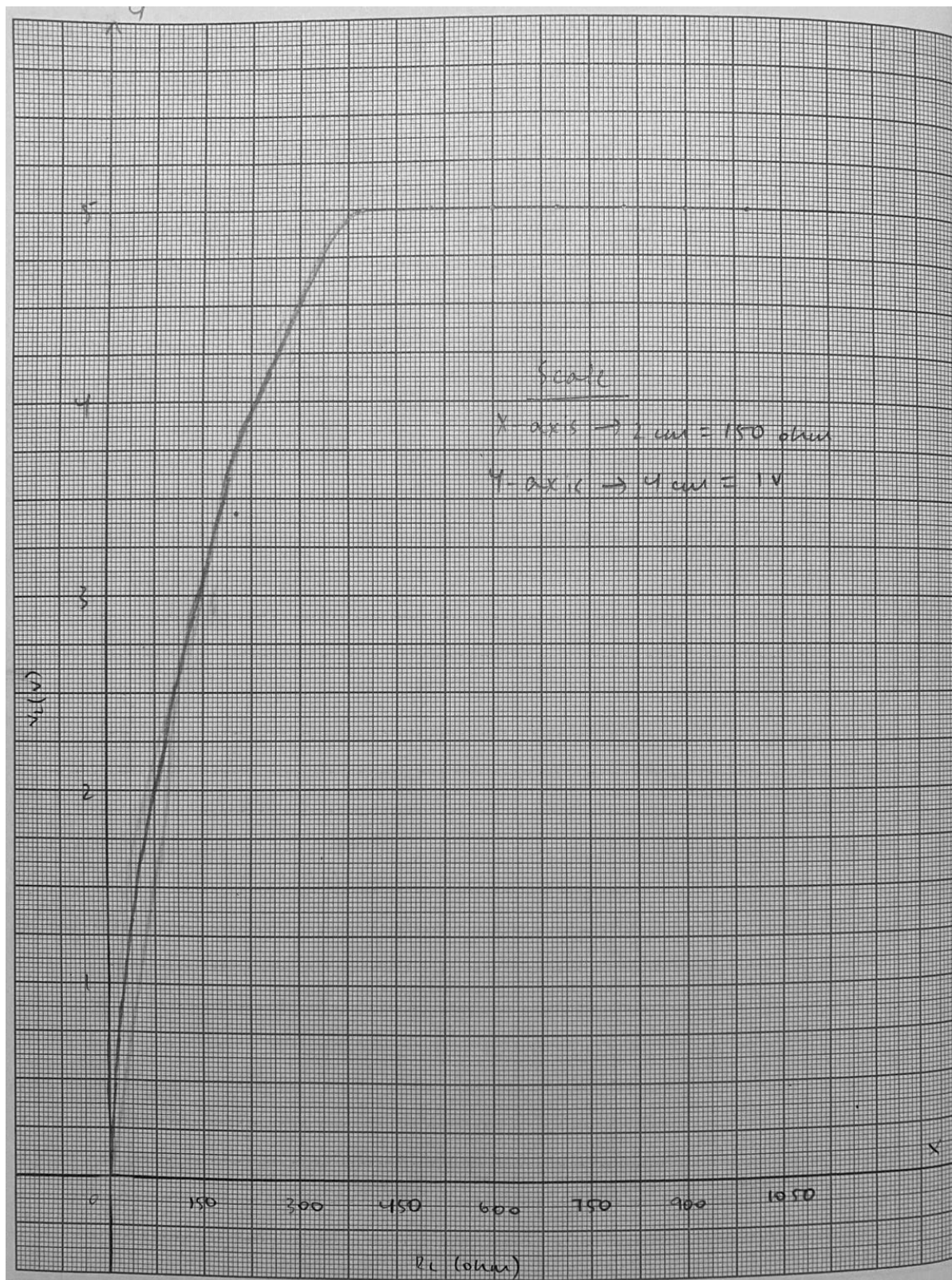

Verification Message



KRISHNA CHAITHANYA MUNTHA 14:25
21BDS0340-Exp 4 verified